

PRVI KOLOKVIJUM IZ ELEKTROTEHNIKE


16. april 2014.

GRUPA 1

1. Veoma velika, ravnomerno naelektrisana površ, površinske gustine naelektrisanja $\sigma_1 = \sigma > 0$ i tačkasto naelektrisanje $Q_2 = -Q < 0$ nalaze se u dielektriku relativne dielektrične konstante ϵ_{r1} kao na Slici 1.

a) Odrediti i **skicirati** vektor elektičnog polja u tački A. (3 poena)


b) Odrediti i **skicirati** vektor sile kojom površ deluje na tačkasto naelektrisanje. (2 poena)

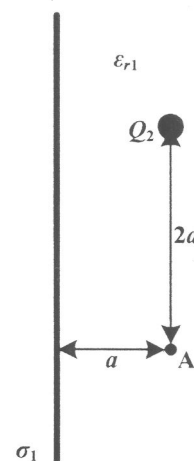


Slika 1

2. Na Slici 2 je prikazana mreža sa kondenzatorima koji su pre povezivanja bili neopterećeni. Odrediti količinu naelektrisanja i napon na svakom kondenzatoru, kao i energiju elektrostatičkog polja kondenzatora C_3 . Obavezno naznačiti referentne smerove naelektrisanja i napona svih kondenzatora. Poznato je: $C_1 = 2\mu\text{F}$, $C_2 = 4\mu\text{F}$, $C_3 = 8\mu\text{F}$, $E = 12\text{V}$.

(5 poena)

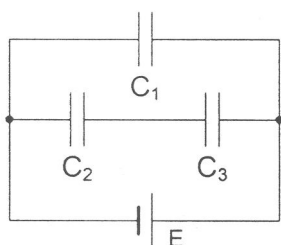


Slika 2

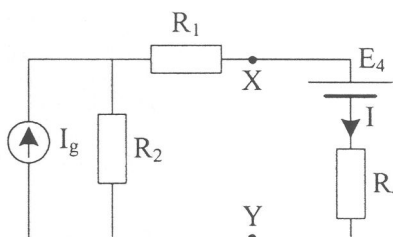


Slika 3

3. U kolu prikazanom na Slici 3, primenom Tevenenove teoreme odrediti intenzitet struje I. Poznato je: $E_4 = 15\text{V}$, $I_g = 2\text{A}$, $R_1 = 10\Omega$, $R_2 = 20\Omega$, $R_4 = 20\Omega$. (5 poena)


4. Primenom metode superpozicije naći napon U_{AB} . Poznato je: $R_1 = 15\Omega$, $R_2 = 25\Omega$, $R_3 = 10\Omega$, $E_1 = 10\text{V}$, $I_g = 1\text{A}$. (5 poena)

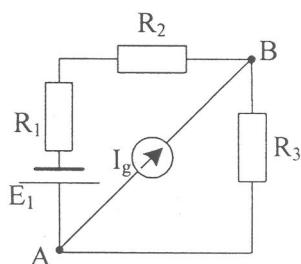

Slika 4

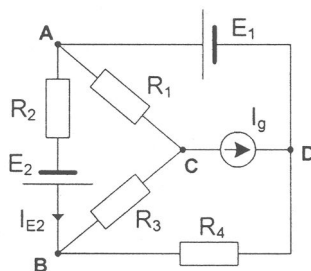

Slika 5

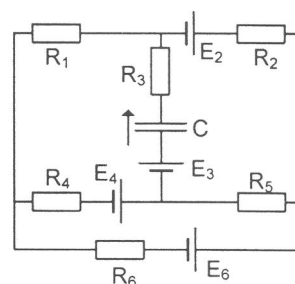


Slika 6

5. U kolu na Slici 5, primenom metode konturnih struja ili napona između čvorova odrediti struju I_{E2} i napon U_{DC} . Poznato je: $E_1 = 40\text{V}$, $E_2 = 30\text{V}$, $I_g = 2\text{A}$, $R_1 = R_2 = R_3 = R_4 = 10\Omega$. (5 poena)

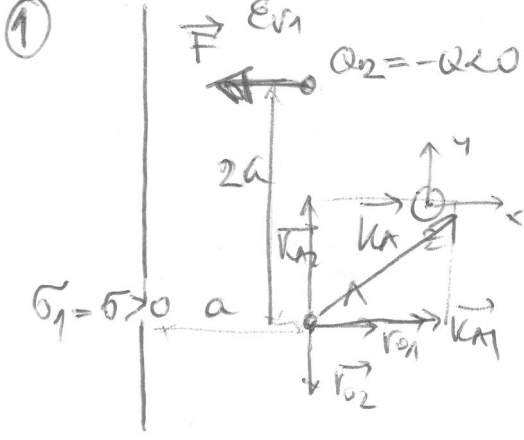6. U kolu prikazanom na Slici 6 uspostavljeno je stacionarno stanje. Odrediti količinu naelektrisanja kondenzatora u smeru naznačenom na slici. Poznato je: $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 10\Omega$, $E_2 = 10\text{V}$, $E_3 = 5\text{V}$, $E_4 = 10\text{V}$, $E_6 = 50\text{V}$, $C = 3\mu\text{F}$. (5 poena)

Izrada kolokvijuma traje 90 minuta. Na vežbanci napisati broj grupe zadataka. Papir sa tekstom zadataka predaje se u vežbanci tj. ne sme se izneti.



a) $\vec{K}_A = \vec{K}_{A1} + \vec{K}_{A2}$

$$\vec{K}_{A1} = \frac{\sigma_1}{2\epsilon_0\epsilon_{r1}} \vec{r}_{01} = \frac{\sigma}{2\epsilon_0\epsilon_{r1}} \vec{r}$$


$$\vec{K}_{A2} = \frac{Q_2}{4\pi\epsilon_0\epsilon_{r3}(2a)^2} \vec{r}_{02} = \frac{-Q}{16\pi\epsilon_0\epsilon_{r3}a^2} (\vec{r})$$

$$= \frac{Q}{16\pi\epsilon_0\epsilon_{r3}a^2} \vec{r}$$

$$\vec{K}_A = \frac{\sigma}{2\epsilon_0\epsilon_{r1}} \vec{r} + \frac{Q}{16\pi\epsilon_0\epsilon_{r3}a^2} \vec{r}$$

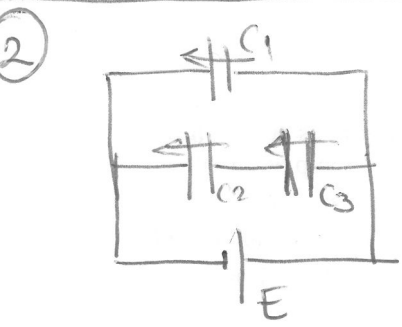b) $\vec{F} = Q_2 \vec{K}$

$$\vec{K} = \frac{\sigma}{2\epsilon_0\epsilon_{r1}} \vec{r} \quad \left\{ \vec{F} = \frac{-Q\sigma}{2\epsilon_0\epsilon_{r1}} \vec{r} \right.$$





$U_1 = E = 12V$ $Q_1 = U_1 \cdot C_1 = 12V \cdot 2\mu F = 24\mu C$

$Q_2 = Q_3 = Q_{23} = C_{23} \cdot E = \frac{C_2 C_3}{C_2 + C_3} E = \frac{4\mu F \cdot 8\mu F}{12\mu F} \cdot 12V = 32\mu C$

$Q_2 = 32\mu C$ $U_2 = \frac{Q_2}{C_2} = \frac{32\mu C}{4\mu F} = 8V$

$Q_3 = 32\mu C$ $U_3 = \frac{Q_3}{C_3} = \frac{32\mu C}{8\mu F} = 4V$




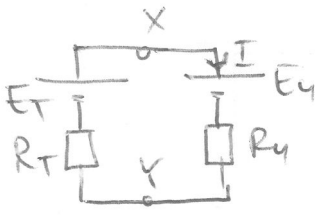
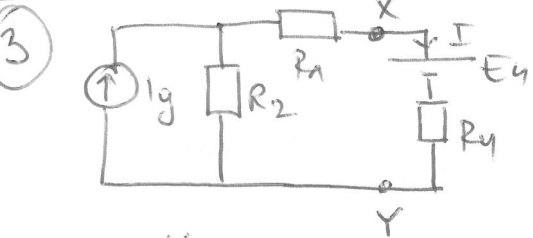
$W_{C3} = \frac{1}{2} Q_3 U_3 = \frac{1}{2} C_3 U_3^2 = \frac{1}{2} \frac{Q_3^2}{C_3} = \frac{1}{2} 32\mu C \cdot 4V = 64\mu J$



$R_T = R_1 + R_2 = 30\Omega$

$E_T = R_2 I_g = 20\Omega \cdot 2A = 40V$

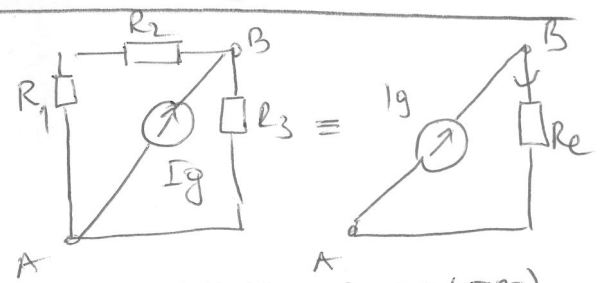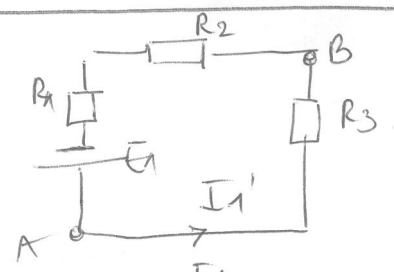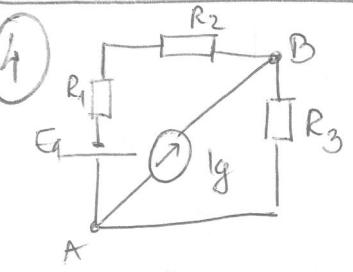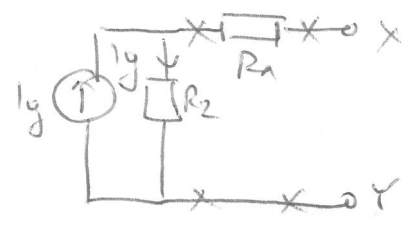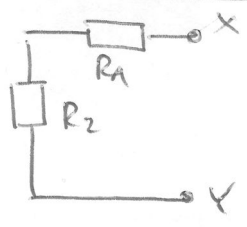$I = \frac{E_T - E_4}{R_T + R_4} = \frac{40 - 15}{30 + 20} = \frac{25}{50} = 0,5A$



$U_{AB} = U_{AB}^I + U_{AB}^{II}$

$= 2 - 8$

$U_{AB} = -6V$

$I_1' = \frac{E_1}{R_1 + R_2 + R_3}$


$U_{AB}^I = R_3 I_1' = \frac{R_3}{R_1 + R_2 + R_3} E_1$

$U_{AB}^I = \frac{10}{50} 10 = 2V$

$R_e = R_3 \parallel (R_1 + R_2) = 10 \parallel (15 + 25)$

$= \frac{10 \cdot 40}{50} = 8\Omega$

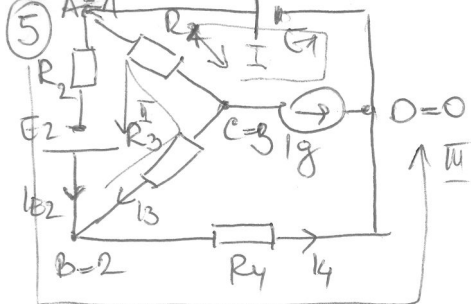$U_{AB}^{II} = -R_e I_g = -8 \cdot 1 = -8V$



$$I_I = I_g$$

$$-R_1 I_I + (R_2 + R_3 + R_4) I_{II} + R_2 I_{III} = E_2$$

$$0 \cdot I_I + R_2 I_{II} + (R_2 + R_4) I_{III} = E_1 + E_2$$

$$3R I_{II} + R_2 I_{III} = E_2 + R I_g$$

$$R I_{II} + 2R I_{III} = E_1 + E_2$$

$$30 I_{II} + 10 I_{III} = 30 + 20 = 50$$

$$10 I_{II} + 20 I_{III} = 40 + 30 = 70$$

$$3 I_{II} + I_{III} = 5 \quad | -2$$

$$I_{II} + 2 I_{III} = 7 \quad | +$$

$$3 I_{II} + I_{III} = 5$$

$$-6 I_{II} + I_{III} = -10 + 7$$

$$I_{III} = 5 - 3 I_{II}$$

$$-5 I_{II} = -3$$

$$\Rightarrow \begin{cases} I_{II} = \frac{3}{5} = 0,6 \text{ A} \\ I_{III} = 5 - 3 \cdot \frac{3}{5} = 5 - \frac{9}{5} = \frac{25-9}{5} = \frac{16}{5} \end{cases}$$

$$I_{III} = 3,2 \text{ A}$$

$$|E_2 = I_{II} + I_{III} = 0,6 + 3,2$$

$$|E_2 = 3,8 \text{ A}|$$

$$I_4 = I_{III} = 3,2 \text{ A} \quad I_3 = -I_{II} = -0,6 \text{ A}$$

$$U_{CO} = R_3 I_3 + R_4 I_4$$

$$= -6 + 32 = 26 \text{ V}$$

$$U_{CO} = 26 \text{ V}$$

НАПОНИМА: $U_{10} = U_{A0} = E_1 = 40$

$$-\frac{1}{R_2} U_{10} + U_{20} \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) - \frac{1}{R_3} U_{30} = \frac{E_2}{R_2}$$

$$-\frac{1}{R_1} U_{10} - \frac{1}{R_3} U_{20} + \left(\frac{1}{R_1} + \frac{1}{R_3} \right) U_{30} = -I_g$$

$$\frac{3}{R} U_{20} - \frac{1}{R} U_{30} = \frac{E_2}{R} + \frac{E_1}{R}$$

$$-\frac{1}{R} U_{20} + \frac{2}{R} U_{30} = -I_g + \frac{E_1}{R}$$

$$3U_{20} - U_{30} = E_1 + E_2 = 70$$

$$-U_{20} + U_{30} = -I_g R + E_1 = 20$$

↓

$$U_{20} = 32 \text{ V} \quad U_{30} = 26 \text{ V}$$


$$U_{CO} = U_{30} = 26 \text{ V}$$

$$U_{BA} = U_{21} = U_{20} - U_{10} = 32 - 40$$

$$U_{BA} = -8 = E_2 - R_2 I_{E2}$$

$$I_{E2} = \frac{E_2 - U_{BA}}{R_2} = \frac{30 - (-8)}{10} = \frac{38}{10}$$

$$I_{E2} = 3,8 \text{ A}$$

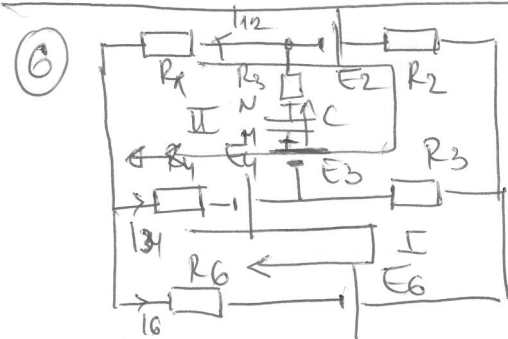

$$(R_4 + R_3 + R_6) I_I - (R_3 + R_4) I_{II} = E_4 - E_6$$

$$-(R_3 + R_4) I_I + (R_1 + R_2 + R_3 + R_4) I_{II} = -E_4 + E_2$$

$$3R I_I - 2R I_{II} = 10 - 50 = -40$$

$$-2R I_I + 4R I_{II} = -10 + 10$$

$$R = 10 \Omega$$

$$30 I_I - 20 I_{II} = -40$$

$$-2 I_I + 4 I_{II} = 0$$

$$3 I_I - 2 I_{II} = -4$$

$$-I_I + 2 I_{II} = 0$$

$$2 I_I = -4 \Rightarrow I_I = -2 \text{ A}$$

$$2 I_{II} = I_I \Rightarrow I_{II} = -1 \text{ A}$$

$$I_{12} = -I_{II} = 1 \text{ A}$$

$$I_{34} = I_I - I_{II} = -2 + 1 = -1 \text{ A}$$

$$U_C = U_{MN} = -R_1 I_{12} - R_4 I_{34} + E_4 + E_3$$

$$= -10 \cdot 1 - 10 \cdot (-1) + 10 + 5$$

$$= -10 + 10 + 15 = 15 \text{ V}$$

$$U_C = 15 \text{ V}$$

$$Q_C = U_C \cdot C = 15 \text{ V} \cdot 3 \mu\text{F}$$

$$Q_C = 45 \mu\text{C}$$