

1. Kondenzator kapaciteta  $C = 100 \mu\text{F}$ , otpornici otpornosti  $R_1$  i  $R_2$  i idealni naponski generator ems  $E = 10 \text{ V}$  su povezani u kolo kao na slici.


U položaju (0) prekidača  $\Pi$  izmeren je napon na kondenzatoru

$U_{C0} = 1 \text{ V}$ , zatim se prekidač prebacuje u položaj (1) u kome ostaje sve do uspostavljanja novog stacionarnog stanja.


a) Izračunati koliko se promenilo opterećenje kondenzatora

$\Delta Q = Q_1 - Q_0$  do uspostavljanja novog stacionarnog stanja gde je  $Q_0$  početno naelektrisanje kondenzatora a  $Q_1$  naelektrisanje u stacionarnom stanju pri položaju (1) prekidača.

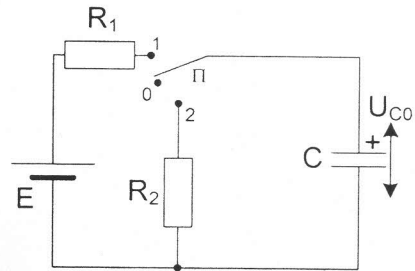
b) Odrediti vrednost otpornosti otpornika  $R_1$  ako je vremenska konstanta u procesu opterećivanja kondenzatora  $\tau_o = 0.05 \text{ s}$ .



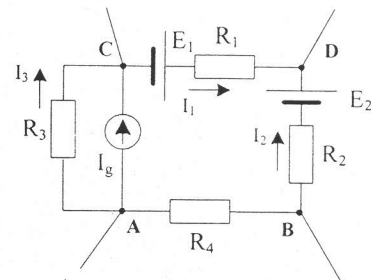
2. U delu složenog kola jednosmerne struje sa slike poznate su sve vrednosti elemenata i intenziteti struja  $I_1$ ,  $I_2$  i  $I_3$ . Odrediti izraz za napon  $U_{AB}$ .



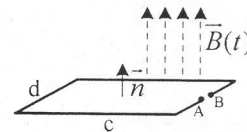
3. Kroz ravno kolo na slici magnetna indukcija se menja po zakonu  $B(t) = 0.2 \cdot \sin(314t) \text{ T}$ . Odrediti izraz za magnetni fluks kroz konturu. Odrediti trenutnu vrednost indukovane elektromotorne sile između tačaka A i B. Poznato je:  $d = 20 \text{ cm}$  i  $c = 50 \text{ cm}$ .



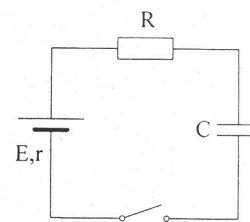4. U RC kolu sa slike vremenska konstanta prelaznog procesa uključenja kondenzatora na izvor realne elektromotorne sile je  $\tau = 0.01 \text{ s}$ . Poznate su vrednosti  $R = 97 \Omega$  i  $C = 100 \mu\text{F}$ . Izračunati unutrašnju otpornost  $r$ .




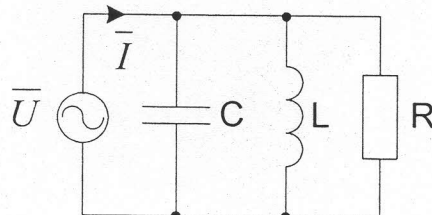5. U kolu naizmjenične struje sa slike poznato je:  $\bar{U} = 100 \sqrt{-\frac{\pi}{6}} \text{ V}$ ,  $X_L = X_C = 10 \Omega$  i  $R = 10 \Omega$ . Odrediti struju  $\bar{I}$  u kompleksnom obliku.



①  $\pi \rightarrow 0 \quad U_{C0} = 1V \Rightarrow Q_0 = U_{C0} \cdot C = 100 \mu C$


a)  $\pi \rightarrow 1$

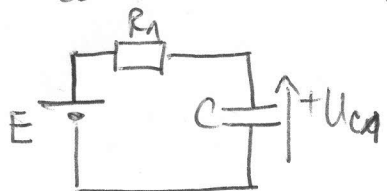


$U_{C1} = E \Rightarrow Q_1 = U_{C1} \cdot C = 1000 \mu C$

$\Delta Q = Q_1 - Q_0 = 900 \mu C$

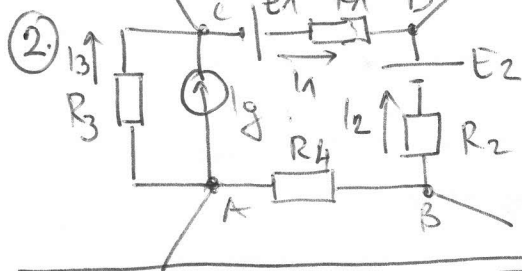b)  $\tau_0 = R_1 C \Rightarrow R_1 = \frac{\tau_0}{C} = \frac{0,05 S}{100 \mu F} = 500 \Omega$



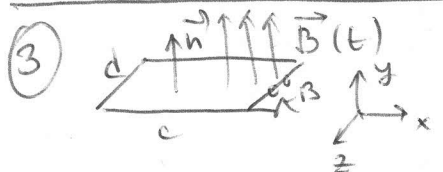$U_{AB} = -R_2 I_2 + E_2 + R_1 I_1 - E_1 + R_3 I_3$




$\Phi(t) = \vec{B} \cdot \vec{S} = B(t) \vec{j} \cdot c d \cdot \vec{j} = B(t) \cdot c d = 20 \cdot 10^{-2} \cdot 50 \cdot 10^{-2} \cdot 0,2 \sin(314t)$

$\Phi(t) = 20 \cdot 10^{-3} \sin(314t) \text{ [Wb]}$

$e_{ind} = -\frac{d\Phi(t)}{dt} = -20 \cdot 10^{-3} \cos(314t) \cdot 314$

$= -6,28 \cos(314t) \text{ [V]}$

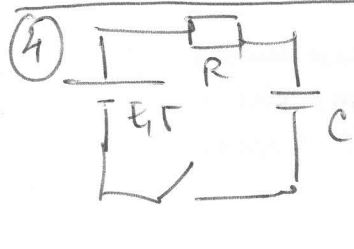

$\tau = C(R+r) \Rightarrow r = \frac{\tau}{C} - R = \frac{0,01}{100 \cdot 10^{-6}} - 97$


$r = 100 - 97 = 3 \Omega$

$r = 3 \Omega$

⑤  $\bar{U} = 100 e^{j\omega t/6}$

$X_L = X_C = 10 \Omega$

$R = 10 \Omega$

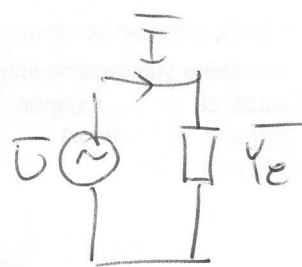

$\bar{Z}_L = jX_L = j10 \Omega \Rightarrow \bar{Y}_L = \frac{1}{j10} = -j0,1 S$

$\bar{Z}_C = -jX_C = -j10 \Omega \quad \bar{Y}_C = \frac{1}{j10} = +j0,1 S$

$\bar{Z}_R = 10 \Omega \quad \bar{Y}_R = \frac{1}{10} = 0,1 S$

$\bar{Y}_e = \bar{Y}_C + \bar{Y}_L + \bar{Y}_R = -j0,1 + j0,1 + 0,1 = 0,1 S$

$I = \frac{\bar{U}}{\bar{Z}_e} = \bar{U} \bar{Y}_e = 100 e^{j\omega t/6} \cdot 0,1 = 10 e^{j\omega t/6} \text{ A}$