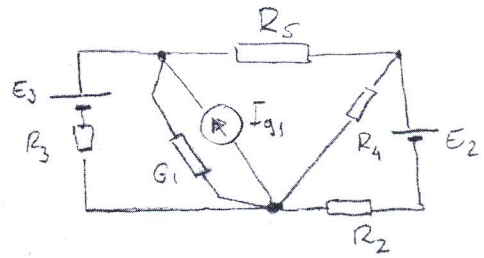



**Elektrotehnika, 5.2.2015.**  
**grupa 2**

1. a) Složeno električno kolo jednosmerne struje čine otpornici, realni naponski generatori i realni strujni generatori. Kolo ima  $N_g=5$  grana i  $N_č=3$  čvorova. Za ovakav slučaj postaviti opšti sistem jednačina po metodi napona između čvorova. Šta su nepoznate veličine u ovom sistemu i kako se određuju? Šta su koeficijenti uz nepoznate veličine i kako se oni dobijaju? Šta su slobodni koeficijenti u sistemu jednačina i kao se oni određuju?




b) U kolu na slici označiti na pogodan način čvorove i napisati odgovarajući sistem jednačina po metodi napona između čvorova.

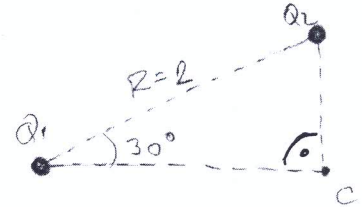
2. Dva tačkasta naelektrisanja  $Q_1$  i  $Q_2$  nalaze se na rastojanju  $R=2$  [cm]. Potencijal  $V_C$  tačke C koja se nalazi u temenu pravouglog trougla čija je jedna hipotenuza duž koja spaja naelektrisanja  $Q_1$  i  $Q_2$  je nula. Odrediti količnik  $\frac{Q_1}{Q_2}$ .



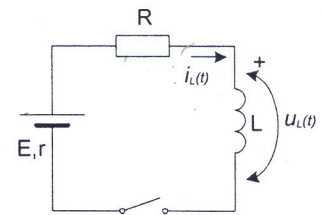3. U kolu na slici prelazni proces započinje uključanjem prekidača. Odrediti vremensku konstantu prelaznog procesa i energiju kalema kada se prelazni proces završi. Poznato je:  $E, r, R, L$ .



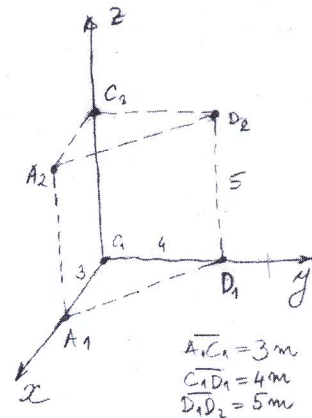4. Odrediti fluks magnetnog polja kroz svaku stranu trostrane prizme prikazane na slici kao i ukupni fluks kroz zatvorenu površ koju čine bočne strane i osnove prizme. Vektor magnetne indukcije ima intenzitet  $B=1$ T a usmeren je u pravcu i smeru y ose. Podaci o ivicama prizme prikazani su na slici.




5. Kroz namotaj koji ima  $N=20$  navojaka magnetni fluks se menja u vremenu po zakonu  $\Phi(t) = \sin\left(1000t + \frac{\pi}{4}\right)$  Wb. Odrediti indukovanu elektromotornu silu na krajevima namotaja.

6. Tri generatora naizmeničnog napona  $e_a, e_b, e_c$  imaju istu efektivnu vrednost elektromotorne sile  $E_a = E_b = E_c = 100$  [V], a faze su  $\varphi_a = 0, \varphi_b = 120^\circ, \varphi_c = 240^\circ$ . Generatori su spregnuti u zvezdu i napajaju trofazni potrošač koji sačinjavaju tri jednake impedanse  $\bar{Z} = 10e^{j\frac{\pi}{6}}$  [ $\Omega$ ], vezane u zvezdu. Odrediti struje i napone u fazama potrošača kao i u linijskim provodnicima koji povezuju trofazni generator sa potrošačem.

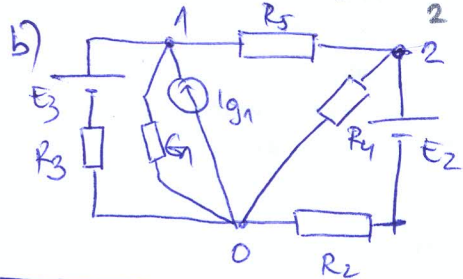
1. a)  $N_c = 3 \Rightarrow$  Broj napona  $N_c - 1 = 2$

$$\begin{cases} G_{11}U_{10} - G_{12}U_{20} = \sum_1 I_g \\ -G_{21}U_{10} + G_{22}U_{20} = \sum_2 I_g \end{cases} \quad \left. \begin{array}{l} \text{ZA DETALJE POGLEDATI U DZBENIK} \\ \text{NA STRANI 53.} \end{array} \right\}$$



$$\begin{aligned} \left(\frac{1}{R_3} + G_1 + \frac{1}{R_5}\right)U_{10} - \frac{1}{R_5}U_{20} &= \frac{E_3}{R_3} + I_{g1} \\ -\frac{1}{R_5}U_{10} + \left(\frac{1}{R_5} + \frac{1}{R_4} + \frac{1}{R_2}\right)U_{20} &= \frac{E_2}{R_2} \end{aligned}$$

2

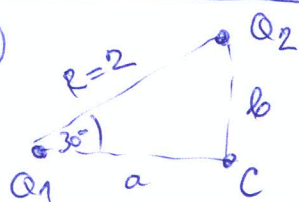


$$a = R \cos 30^\circ = \frac{R\sqrt{3}}{2}, \quad b = R \sin 30^\circ = \frac{R}{2}$$

$$V_c = V_{c1} + V_{c2} = 0$$

$$V_c = \frac{Q_1}{4\pi\epsilon_0 a} + \frac{Q_2}{4\pi\epsilon_0 b} = \frac{Q_1}{2\sqrt{3}\epsilon_0 R} + \frac{Q_2}{2\epsilon_0 R} = 0$$

$$\boxed{\frac{Q_1}{Q_2} = -\sqrt{3}}$$

3

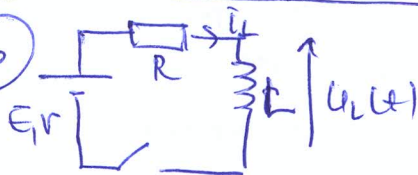


$$i_L(t) = \frac{E}{v+R} (1 - e^{-t/\tau}), \quad \tau = \frac{L}{v+R}$$

$$W_L(t) = \frac{1}{2} L i^2(t)$$

$$W_{L\infty} = \frac{1}{2} L \left(\frac{E}{v+R}\right)^2 = \frac{LE^2}{2(v+R)^2}$$

4

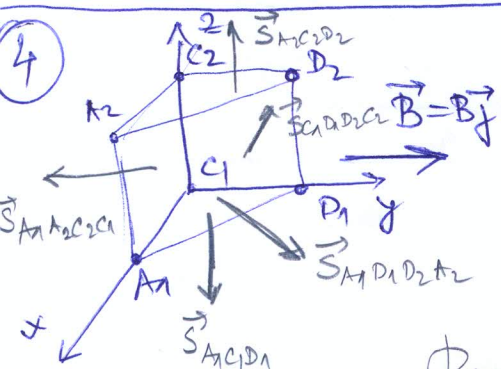


$$\begin{aligned} \Phi_{A_2D_2C_2} &= \vec{B} \cdot \vec{S}_{A_2D_2C_2} = B S_{A_2D_2C_2} \cos \angle(\vec{B}, \vec{S}_{A_2D_2C_2}) \\ &= B S_{A_2D_2C_2} \cos 90^\circ = 0 \end{aligned}$$

$$\begin{aligned} \Phi_{A_1D_1C_1} &= \vec{B} \cdot \vec{S}_{A_1D_1C_1} = B S_{A_1D_1C_1} \cos \angle(\vec{B}, \vec{S}_{A_1D_1C_1}) \\ &= B S_{A_1D_1C_1} \cos 90^\circ = 0 \end{aligned}$$

$$\begin{aligned} \Phi_{C_1D_1D_2C_2} &= \vec{B} \cdot \vec{S}_{C_1D_1D_2C_2} = B S_{C_1D_1D_2C_2} \cos \angle(\vec{B}, \vec{S}_{C_1D_1D_2C_2}) \\ &= B S_{C_1D_1D_2C_2} \cos 90^\circ = 0 \end{aligned}$$

$$\begin{aligned} \Phi_{A_1A_2C_2C_1} &= \vec{B} \cdot \vec{S}_{A_1A_2C_2C_1} = B S_{A_1A_2C_2C_1} \cos \angle(\vec{B}, \vec{S}_{A_1A_2C_2C_1}) = B \cdot \overline{A_1C_1} \cdot \overline{A_1A_2} \cos 180^\circ \\ &= -15 \cdot 10^{-4} \text{ Wb} \end{aligned}$$
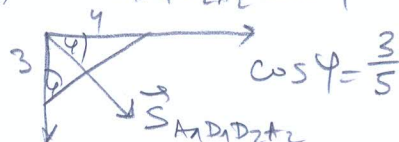
$$\begin{aligned} \Phi_{A_1D_1D_2A_2} &= \vec{B} \cdot \vec{S}_{A_1D_1D_2A_2} = B S_{A_1D_1D_2A_2} \cos \angle(\vec{B}, \vec{S}_{A_1D_1D_2A_2}) = B S_{A_1D_1D_2A_2} \cos \varphi \\ &= B \cdot \overline{A_1D_1} \cdot \overline{D_1D_2} \cos \varphi = 15 \cdot 10^{-4} \text{ Wb} \end{aligned}$$






⑤  $N=20 \quad \phi(t) = \sin(1000t + \frac{\pi}{4}) \text{ Wb}$

$$e_{ind} = -N \frac{d\phi}{dt} = -20 \frac{d}{dt} (\sin(1000t + \frac{\pi}{4})) = -20 \cdot \cos(1000t + \frac{\pi}{4}) \cdot 1000$$

$$e_{ind} = -20000 \cos(1000t + \frac{\pi}{4}) \text{ [V]} = -20 \cos(1000t + \frac{\pi}{4}) \text{ [kV]}$$

⑥

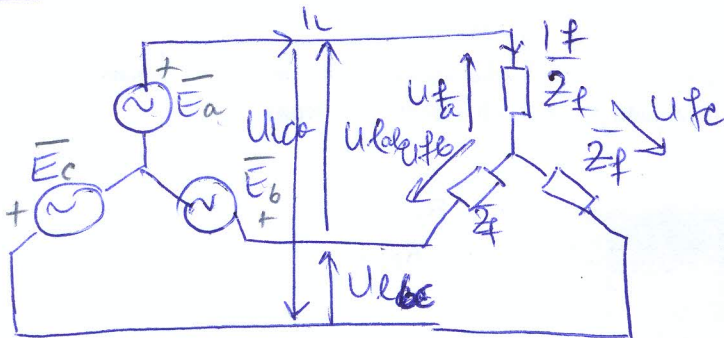

$$E_a = E_b = E_c = 100 \text{ V}$$

$$\varphi_a = 0$$

$$\varphi_b = 120^\circ = \frac{2\pi}{3}$$

$$\varphi_c = 240^\circ = \frac{4\pi}{3}$$

$$\bar{Z}_f = 10 e^{j\frac{\pi}{6}}$$

$$U_L = \sqrt{3} U_f = E \sqrt{3} = 100 \sqrt{3} \text{ V}$$

$$U_f = E = 100 \text{ V}$$

$$Z_f = 10 \Omega$$

$$I_f = \frac{U_f}{Z_f} = \frac{100}{10} = 10 \text{ A}$$

$$I_L = I_f = 10 \text{ A}$$

$$\varphi_a = \varphi_a - \theta = 0 - \frac{\pi}{6} = -\frac{\pi}{6} \Rightarrow$$

$$\bar{I}_{La} = \bar{I}_{Fa} = 10 e^{-j\frac{\pi}{6}}$$

$$\varphi_b = \varphi_b - \theta = \frac{2\pi}{3} - \frac{\pi}{6} = \frac{3\pi}{6} - \frac{\pi}{6} = \frac{2\pi}{6} = \frac{\pi}{3} \Rightarrow$$

$$\bar{I}_{Lb} = \bar{I}_{Fb} = 10 e^{j\frac{\pi}{3}}$$

$$\varphi_c = \varphi_c - \theta = \frac{4\pi}{3} - \frac{\pi}{6} = \frac{8\pi}{6} - \frac{\pi}{6} = \frac{7\pi}{6} \Rightarrow$$

$$\bar{I}_{Lc} = \bar{I}_{Fc} = 10 e^{j\frac{7\pi}{6}}$$

$$\bar{E}_a = \bar{U}_{Fa} = 100 e^{j0}$$

$$\bar{E}_b = \bar{U}_{Fb} = 100 e^{j\frac{2\pi}{3}}$$

$$\bar{E}_c = \bar{U}_{Fc} = 100 e^{j\frac{4\pi}{3}}$$

$$\bar{U}_{Lab} = \bar{U}_{Fa} - \bar{U}_{Fb} = 100 e^{j0} - 100 e^{j\frac{2\pi}{3}}$$

$$= 100 e^{j\frac{\pi}{3}} (e^{-j\frac{\pi}{3}} - e^{j\frac{\pi}{3}}) = 100 e^{j\frac{\pi}{3}} (2j \sin \frac{\pi}{3})$$

$$= 100 e^{j\frac{\pi}{3}} \cdot 2 \sin \frac{\pi}{3} e^{-j\frac{\pi}{2}} = 100 \cdot \frac{\sqrt{3}}{2} e^{j(\frac{\pi}{3} - \frac{\pi}{2})}$$

$$\bar{U}_{Lab} = 100 \sqrt{3} e^{-j\frac{\pi}{6}}$$

$$\bar{U}_{Lbc} = \bar{U}_{Fb} - \bar{U}_{Fc} = 100 e^{j\frac{2\pi}{3}} - 100 e^{j\frac{4\pi}{3}} = 100 e^{j\frac{2\pi}{3}} (1 - e^{j\frac{2\pi}{3}})$$

$$= 100 e^{j\frac{2\pi}{3}} e^{j\frac{\pi}{3}} (e^{-j\frac{\pi}{3}} - e^{j\frac{\pi}{3}}) = 100 e^{j\pi} (-2j \sin \frac{\pi}{3})$$

$$= 100 e^{j\pi} \cdot 2 e^{-j\frac{\pi}{2}} \cdot \frac{\sqrt{3}}{2} = 100 \sqrt{3} e^{j\frac{\pi}{2}} = \bar{U}_{Lbc}$$

$$\bar{U}_{Lca} = \bar{U}_{Fc} - \bar{U}_{Fa} = 100 e^{j\frac{4\pi}{3}} - 100 = 100 e^{j\frac{2\pi}{3}} (e^{j\frac{2\pi}{3}} - e^{-j\frac{2\pi}{3}}) = 100 e^{j\frac{2\pi}{3}} (2j \sin \frac{2\pi}{3})$$

$$= 100 \cdot e^{j\frac{2\pi}{3}} \cdot 2 \cdot \frac{\sqrt{3}}{2} e^{j\frac{\pi}{2}} = 100 \sqrt{3} e^{j\frac{7\pi}{6}} = \bar{U}_{Lca}$$