


Elektrotehnika

06. jul 2016.


1. a) Pločasti kondenzator nepoznate kapacitivnosti C_1 optrećen je količinom naelektrisanja $Q_{10} = 10 \text{ pC}$. Ploče kondenzatora su oblika kvadrata stranice $a = 1 \text{ cm}$, a rastojanje između njih iznosi $d = 1 \text{ mm}$. Dielektrična konstanta dielektrika između ploča kondenzatora je $\epsilon = 5 \cdot 10^{-11} \text{ F/m}$. Odrediti:

- nepoznatu kapacitivnost kondenzatora, C_1 ; (3 poena)
- napon na krajevima kondenzatora; (2 poena)
- intenzitet vektora električnog polja u dielektriku; (2 poena)
- intenzitet sile kojom se privlače ploče. (3 poena)


- b) Ako se kondenzator iz tačke a) poveže u kolo na Slici 1, sa neopterećenim kondenzatorom kapacitivnosti $C_2 = 20 \text{ pF}$ i generatorom elektromotorne sile $E = 12 \text{ V}$, odrediti kolika će količina naelektrisanja proteći kroz kolo u naznačenom smeru nakon zatvaranja prekidača. (10 poena)

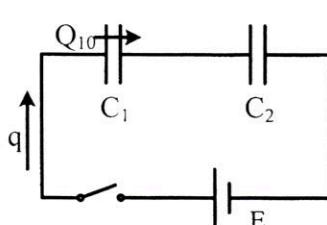

Slika 1

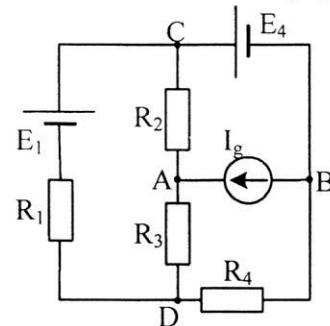

Slika 2

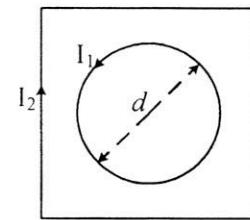


Slika 3

2. U kolu na Slici 2 poznate su vrednosti $R_1 = R_2 = R_3 = 3 \Omega$, $R_4 = 8 \Omega$, $I_g = 1 \text{ A}$, $E_1 = 6 \text{ V}$, $E_4 = 8 \text{ V}$. Primenom Tevenenove teoreme odrediti napon U_{DB} i snagu otpornika R_4 . (25 poena)


3. Kružna kontura prečnika $d = 4 \text{ cm}$ sa strujom intenziteta $I_1 = 1 \text{ A}$ i kvadratna kontura stranice $a = 3 \text{ cm}$ sa strujom intenziteta $I_2 = 4 \text{ A}$ nalaze se u istoj ravni u vazduhu (Slika 3). Odrediti i nacrtati vektor jačine magnetnog polja u centru kružne konture. (15 poena)

4. U kolu na Slici 4 poznate su vrednosti elemenata: $E = 60 \text{ V}$, $R = 2 \Omega$, $L = 24 \mu\text{H}$. Prekidač je otvoren i u kolu je uspostavljeno stacionarno stanje. U trenutku $t = 0$, prekidač se zatvara. a) Odrediti izraze za struju i napon kalema nakon zatvaranja prekidača (12 p) i nacrtati odgovarajuće vremenske dijagrame (4 p). b) Odrediti energiju magnetnog polja kalema u trenutku $t_1 = 12 \mu\text{s}$. (4 p)

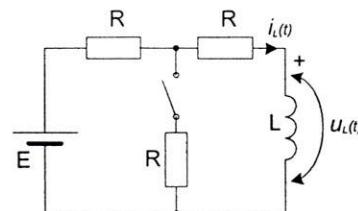

Slika 4


5. Na Slici 5 prikazan je trofazni sistem generator potrošač. Efektivna vrednost elektromotornih sila iznosi $E = 100 \text{ V}$, aktivna snaga potrošača $P = 27 \text{ W}$, a reaktivna snaga $Q = -36 \text{ var}$. Odrediti: efektivnu vrednost linijske struje, faktor snage potrošača i kompleksnu impedansu potrošača. (20 poena)

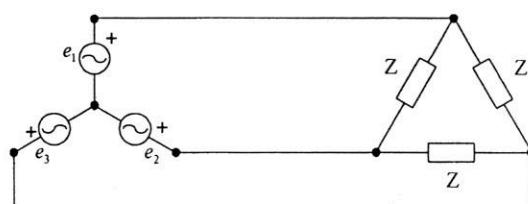

Slika 5

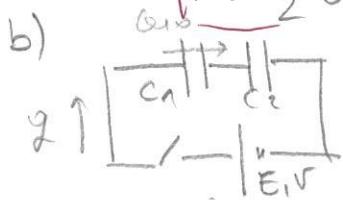(1) a)

- $C_1 = \epsilon \frac{S}{d} = 5 \cdot 10^{-11} \frac{10^{-4}}{10^{-3}} = 5 \cdot 10^{-12} = 5 \text{ pF}$
- $U = \frac{Q_{10}}{C_1} = 2 \text{ V}$
- $K = \frac{U}{d} = 2 \frac{\text{kV}}{\mu\text{m}}$
- $F = \frac{1}{2} Q_{10} K = \frac{Q_{10}^2}{2 \epsilon S} = 10^{-8} \text{ N}$



$$Q_1 = Q_{10} + q$$

$$Q_2 = q$$

$$E - U_{C_1} - U_{C_2} = 0$$

$$E - \frac{Q_{10} + q}{C_1} - \frac{q}{C_2} = 0$$

$$q = \frac{E - \frac{Q_{10}}{C_1}}{\frac{1}{C_1} + \frac{1}{C_2}}$$

$$q = 40 \text{ pC}$$

(2)

$$E_T = U_{BD}^{(0V)} = R_3 I_3 + R_2 I_2 + E_4$$

$$I_I = I_2$$


$$I_{II} (R_1 + R_2 + R_3) + R_2 I_5 = -E_1$$

$$I_{III} = \frac{-E_1 - R_2 I_2}{R_1 + R_2 + R_3} = \frac{-6 - 3 \cdot 3}{3 + 3 + 3} = \frac{-9}{9} = -1 \text{ A}$$

$$| E_T = 5 \text{ V} |$$

$$I_3 = I_{II} = -1 \text{ A} \quad I_2 = I_I + I_{III} = 0$$
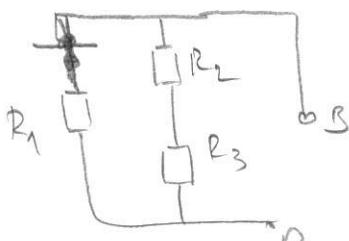
$$E_T = 3 \cdot (-1) + 3 \cdot 0 + 8 = 8 - 3 = 5 \text{ V}$$




$$E_T = 5 \text{ V}$$

$$R_T = 2 \Omega$$

$$P_{R_2} = 2 \text{ W}$$
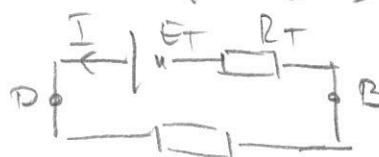
$$R_T = R_1 \parallel (R_2 + R_3) = 3 \parallel (3 + 3) = 3 \parallel 6 = \frac{3 \cdot 6}{9} = 2 \Omega$$



$$I = \frac{E_T}{R_T + R_4} = \frac{5}{8 + 2} = \frac{1}{2} \text{ A}$$

$$U_{DB} = R_4 I = 8 \cdot \frac{1}{2} = 4 \text{ V}$$

$$P_{R_4} = R_4 I^2 = 8 \left(\frac{1}{2}\right)^2 = 2 \text{ W}$$

(3)

$$\vec{B}_0 = \vec{B}_{01} + \vec{B}_{02}$$

$$\vec{B}_{01} = \frac{\mu_0 I_1}{2 \cdot d/2} \vec{k} = \frac{\mu_0 I_1}{d} \vec{k}$$

$$\vec{B}_{02} = \mu_0 \frac{I_2}{4 \cdot \frac{\pi a}{2}} (\cos 45^\circ + i \sin 45^\circ) (\vec{k}) = -2 \frac{\mu_0 I_2}{\pi a} \left(\frac{J_2}{2} + \frac{S_2}{2} \right) \vec{k}$$


$$= -2 \frac{\mu_0 I_2 \sqrt{2}}{\pi a} \vec{k}$$

$$\vec{B}_0 = \mu_0 \left(\frac{I_1}{d} - 2 \frac{I_2 \sqrt{2}}{\pi a} \right) \vec{k}$$

$$| H_0 = \frac{\vec{B}_0}{\mu_0} = \left(\frac{I_1}{d} - 2 \frac{I_2 \sqrt{2}}{\pi a} \right) \vec{k} = -95,59 \frac{\text{A}}{\text{m}} \vec{k} |$$


$$(4) \text{ S.S. } I_{L0} = \frac{E}{2R} = \frac{60}{2 \cdot 2} = 15 \text{ A} \quad U_0 = 0$$

P.P.

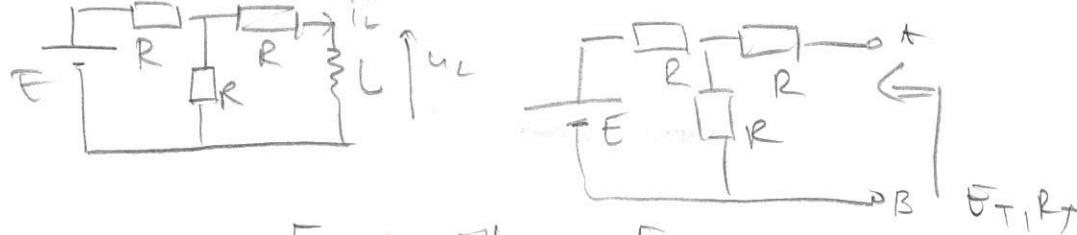

$$E_T = U_{AB} = R \cdot \frac{E}{2R} = \frac{E}{2} = 30 \text{ V}$$

$$R_T = R + (R || R) = R + \frac{R}{2} = \frac{3R}{2} = 3\Omega$$

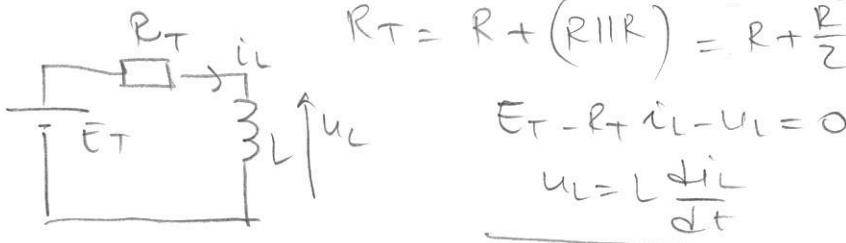

$$E_T - R_T i_L - U_L = 0$$

$$U_L = L \frac{di_L}{dt}$$

$$E_T - R_T i_L - L \frac{di_L}{dt} = 0$$

$$\tau = \frac{L}{R_T} = \frac{24 \mu H}{3\Omega} = 8 \mu s$$

$$\frac{di_L}{dt} + \frac{i_L}{L/R_T} = \left(\frac{E_T}{L} \right) = K$$


$$K = \frac{E_T}{L}$$

$$B = K \tau = \frac{E_T}{R_T} = 10 \text{ A}$$

$$A + B = I_{L0} \Rightarrow$$

$$A = I_{L0} - B = 5 \text{ A}$$

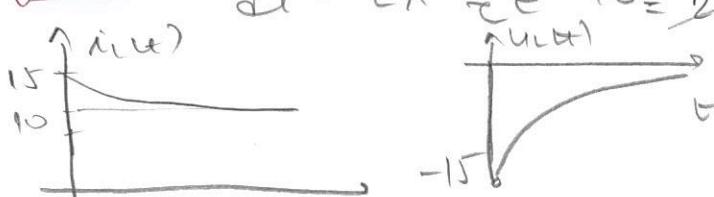
$$i_L(t) = Ae^{-t/\tau} + B = (5e^{-t/8} + 10) \text{ A}$$



$$b) W_m | t_1 = 12 \mu s = \left[\frac{1}{2} L i_L^2 | t_1 = 12 \mu s \right] + \frac{1}{2} \cdot 24 \mu H (5e^{-\frac{12}{8}} + 10)^2 = 12 (10 + 5e^{-1.5})^2 \mu J$$

$$W_m | t_1 = 12 \mu s = 1482,69 \mu J = 1,48 \text{ mJ}$$

(5)

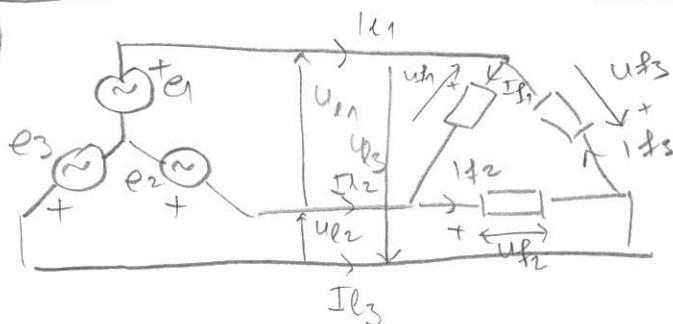

$$U_L = U_f = E\sqrt{3} = 100\sqrt{3} \text{ V}$$

$$\begin{aligned} P &= 27 \text{ W} \\ Q &= -36 \text{ VA} \end{aligned} \Rightarrow S = \sqrt{P^2 + Q^2} = 45 \text{ VA}$$

$$S = 3U_f I_f \Rightarrow I_f = \frac{S}{3U_f} = \frac{45}{300\sqrt{3}} = \frac{150\sqrt{3}}{3} \text{ mA}$$

$$I_f = \frac{150\sqrt{3}}{3} \text{ mA} = 50\sqrt{3} \text{ mA}$$

$$I_L = I_f \sqrt{3} = 150 \text{ mA}$$

$$\cos \varphi = \frac{P}{S} = \frac{27}{45} = 0,6$$

$$\sin \varphi = \frac{Q}{S} = -0,8$$

$$Z_f = \frac{U_f}{I_f} = \frac{100\sqrt{3} \text{ V}}{50\sqrt{3} \text{ mA}} = 2 \text{ k}\Omega$$

$$Z_f = 27 \cos \varphi + j 27 \sin \varphi = 2(0,6 - j0,8) \text{ k}\Omega$$

$$Z_f = (112 - j116) \text{ k}\Omega = (1200 - j1600) \text{ }\Omega$$