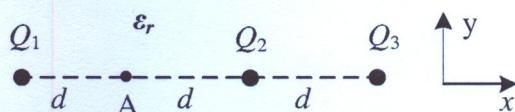


Elektrotehnika


31. januar 2024.

1. Na Slici 1 su prikazana tri tačkasta nanelektrisanaja $Q_1=Q$, $Q_2=-2Q$ i $Q_3=3Q$ koja se nalaze u dielektriku relativne dielektrične konstante ϵ_r . Odrediti i nacrtati vektor električnog polja u tački A. (15 poena)

2. U kolu na Slici 2 poznate su vrednosti $R_1 = 2R = 10\Omega$, $R_2 = 3R = 15\Omega$, $R_3 = R_4 = R_5 = R = 5\Omega$, $I_g = 1A$, $E_1 = 10V$, $E_4 = 40V$. Primenom Tevenenove teoreme odrediti intenzitet struje kroz otpornik R_2 u smeru označenom na slici, kao i snagu na ovom otporniku. (25 poena)



Slika 1

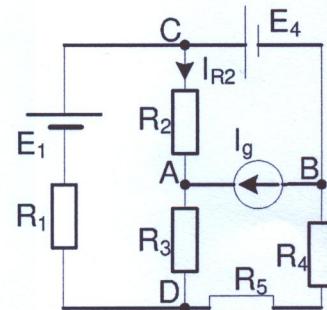


Slika 2

3. Na Slici 3 je prikazano magnetno kolo, sa poznatim parametrima jezgra: dužina srednje linije l_1 , površina poprečnog preseka A , magnetna permeabilnost μ_1 , i debljina vazdušnog procepa l_0 . Na jezgro su namotana dva namotaja, jedan sa N_2 navojaka kroz koji protiče struja konstantnog intenziteta I , i drugi otvorenih krajeva, sa N_1 navojaka.

a) Odrediti intenzitet vektora magnetne indukcije u vazdušnom procepu. (8 poena)


b) Odrediti međusobnu induktivnost namotaja. (6 poena)

c) Odrediti indukovani elektromotornu silu na krajevima namotaja čiji su krajevi otvoreni. (6 poena)

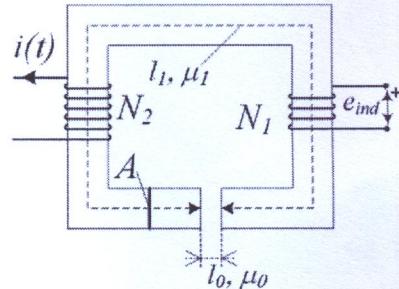

Slika 3

4. U kolu na Slici 4 poznate su vrednosti elemenata: $E = 30V$, $R_1 = R = 5\Omega$, $R_2 = 2R$ i $L = 20\mu H$. Prekidač Π je zatvoren i u kolu je uspostavljeno stacionarno stanje. U trenutku $t = 0$, prekidač se otvara. Odrediti izraz za struju i napon kalema nakon otvaranja prekidača i nacrtati odgovarajuće vremenske dijagrame. Odrediti snagu otpornika R_1 u trenutku $t_1 = 12\mu s$. (20 poena)

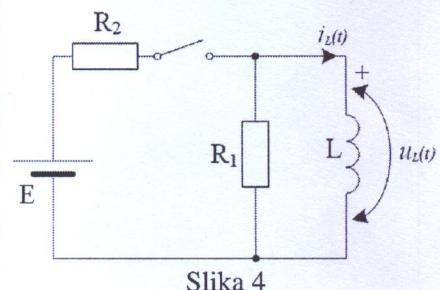

Slika 4


5. Na potrošaču nepoznate impedanse poznate su trenutne vrednosti napona $u(t) = 20\sqrt{2} \sin(1000t + \pi)V$ i struje $i(t) = 10\sin(1000t + 3\pi/4)A$.

a) Odrediti kompleksnu impedansu potrošača. (5 poena)

b) Odrediti aktivnu, reaktivnu i prividnu snagu potrošača. (5 poena)

c) Nacrtati fazorski dijagram struje i napona na impedansi. (5 poena)

d) Ako se paralelno potrošaču priključi kondenzator kapacitivnosti $C = 250\mu F$ odrediti faktor snage celokupnog potrošača. (5 poena)

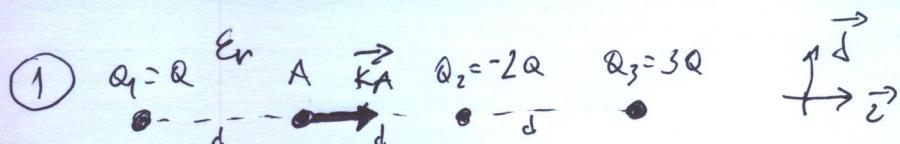
(1) 

$$\vec{K}_A = \vec{K}_{A1} + \vec{K}_{A2} + \vec{K}_{A3} = \frac{Q_1}{4\pi\epsilon_0\epsilon_r d^2} \vec{i} + \frac{Q_2}{4\pi\epsilon_0\epsilon_r d^2} (-\vec{i}) + \frac{Q_3}{4\pi\epsilon_0\epsilon_r d^2} (-\vec{i})$$

$$\vec{K}_A = \frac{Q}{4\pi\epsilon_0\epsilon_r d^2} \vec{i} + \frac{2Q}{4\pi\epsilon_0\epsilon_r d^2} \vec{i} - \frac{3Q}{4\pi\epsilon_0\epsilon_r d^2} \vec{i}$$

$$\vec{K}_A = \frac{Q}{4\pi\epsilon_0\epsilon_r d^2} \vec{i} \left(1 + 2 - \frac{3}{4}\right) \vec{i}$$

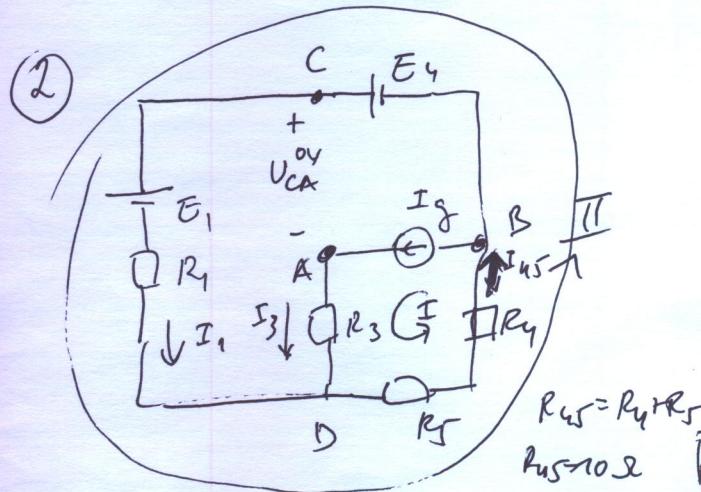$\boxed{\vec{K}_A = \frac{9Q}{16\pi\epsilon_0\epsilon_r d^2} \vec{i}}$



$$I_I = I_g = 1 \text{ A}$$

$$R_{45} I_I + (R_1 + R_{45}) I_{II} = E_4 - E_1$$

$$I_{II} = \frac{E_4 - E_1 - (R_4 + R_5) I_g}{R_1 + R_4 + R_5}$$


$$I_{II} = \frac{40 - 10 - (5+5) \cdot 1}{10 + 5 + 5} = \frac{20}{20} = 1 \text{ A}$$

$I_{45} = I_C + I_{II} = 2 \text{ A}$
 $I_I = I_{II} = 1 \text{ A}$
 $I_3 = I_I = I_g = 1 \text{ A}$

$$E_T = U_{CA}^{ov} = E_4 - R_{45} I_{45} - R_3 I_3$$

$E_T = 40 - 10 \cdot 2 = 5$


$E_T = 15 \text{ V}$

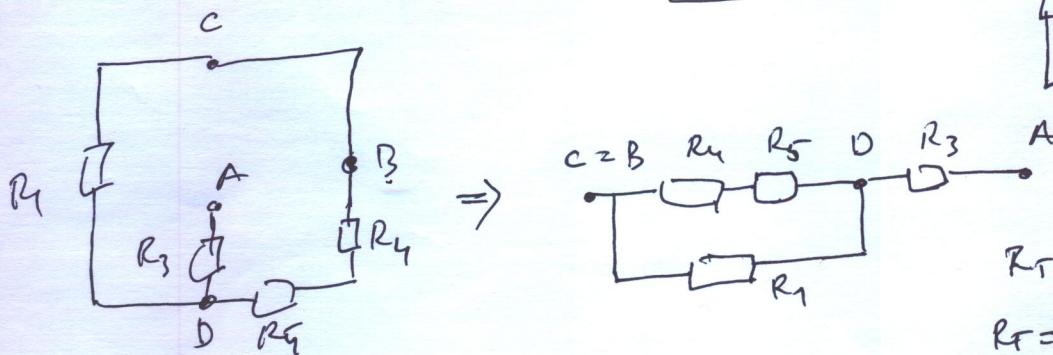

$$R_T = (R_4 + R_5) // R_1 + R_3$$

$$R_T = 2R // 2R + R = R + R = 2R$$


$R_T = 10 \Omega$

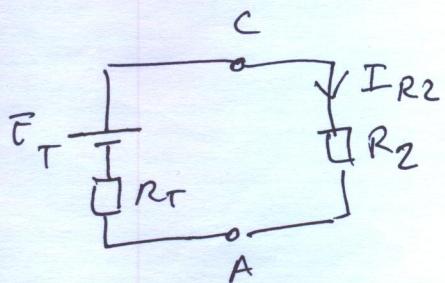

$$I_{R2} = \frac{E_T}{R_T + R_2} = \frac{15}{10 + 15} = \frac{15}{25} = \frac{3}{5} = 0,6 \text{ A}$$

$I_{R2} = 0,6 \text{ A}$

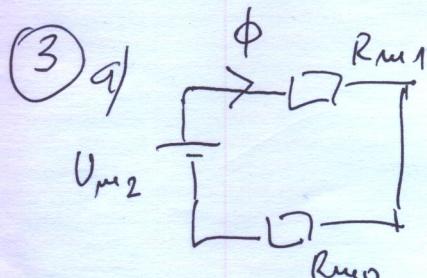$P_{R2} = R_2 I_{R2}^2 = 15 \cdot 0,6^2 = 5,4 \text{ W}$



$$U_{m2} = N_2 I$$

$$R_{m1} = \frac{l_1}{\mu_1 \cdot A}$$

$$R_{mo} = \frac{l_0}{\mu_0 \cdot A}$$


$$\phi = \frac{U_{m2}}{R_{m1} + R_{mo}} = \frac{N_2 I}{\frac{l_1}{\mu_1 \cdot A} + \frac{l_0}{\mu_0 \cdot A}}$$

$$(B_1 - B_0) = \frac{\phi}{A} = \frac{N_2 I}{\frac{l_1}{\mu_1} + \frac{l_0}{\mu_0}}$$

$$b) L_{12} = L_{21} = \frac{N_1 N_2}{R_{m1} + R_{m0}} = \frac{N_1 N_2 A}{l_1/\mu_1 + l_0/\mu_0}$$


$$c) \Psi_1 = N_1 \cdot \Phi = \frac{N_1 N_2 I A}{l_1/\mu_1 + l_0/\mu_0} = \text{const}$$
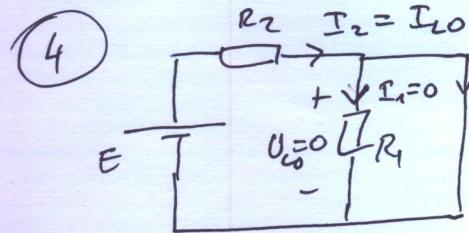
$$\mathcal{E}_{ind} = - \frac{d\Psi_1}{dt} = 0 \text{ V}$$



$$U_{c0} = 0 \Rightarrow I_1 = 0 \Rightarrow I_2 = I_{L0} = \frac{E}{R_2} = \frac{\bar{E}}{2R}$$

$$I_{L0} = 3 \text{ A}$$

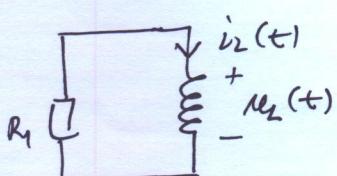

$$R i_L + u_L = 0$$

$$R i_L + L \frac{di_L}{dt} = 0$$

$$\boxed{\frac{di_L}{dt} + \frac{R}{L} i_L = 0}$$

$$\Rightarrow K=0, \alpha = \frac{R}{L}, T = \frac{L}{R} = 4 \mu\text{s}$$


$$i_L(t) = A e^{-\frac{t}{T}} + B$$

$$B = K \cdot \tau = 0$$

$$A = i_L(0) - B = I_{L0} = \frac{E}{2R}$$

$$i_L(t) = \frac{E}{2R} e^{-\frac{R}{L} t}$$
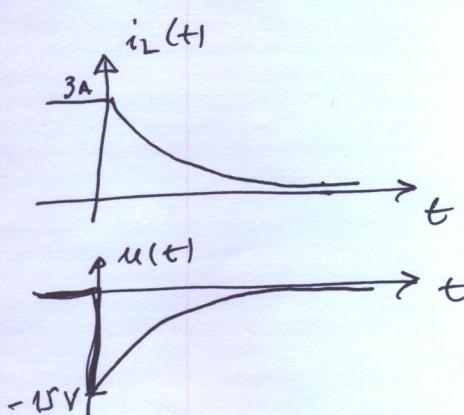
$$i_L(t) = 3 e^{-\frac{t}{4 \mu\text{s}}} \text{ A}$$



$$u_L(t) = L \frac{di_L}{dt} = L \frac{E}{2R} e^{-\frac{R}{L} t} \cdot \left(-\frac{R}{L}\right)$$

$$\boxed{u_L(t) = -\frac{E}{2} e^{-\frac{R}{L} t} = -15 e^{-\frac{t}{4 \mu\text{s}}} \text{ V}}$$

$$P_{R1}(t_1) = R_1 \cdot i_L^2(t_1) = \frac{E^2}{4R} e^{-2 \frac{R}{L} t_1} = 45 e^{-\frac{2 \cdot 12 \mu\text{s}}{4 \mu\text{s}}} = \underline{45 e^{-6} \text{ W}}$$

(5)

a) $U(t) = 20\sqrt{2} \sin(1000t + \bar{\alpha}) \Rightarrow \bar{U} = 20 e^{j\bar{\alpha}} \text{ V} = -20 \text{ V}$


$i(t) = 10 \sin(1000t + 3\bar{\alpha}/4) \Rightarrow \bar{i} = \frac{10}{\sqrt{2}} e^{j\frac{3\bar{\alpha}}{4}} \text{ A} = 5\sqrt{2} \left(\cos\frac{3\bar{\alpha}}{4} + j \sin\frac{3\bar{\alpha}}{4}\right) = -5 + j5\sqrt{2} \text{ A}$

$\bar{Z} = \frac{\bar{U}}{\bar{i}} = \frac{+20 e^{j\bar{\alpha}}}{5\sqrt{2} e^{j\frac{3\bar{\alpha}}{4}}} = \frac{4}{\sqrt{2}} e^{j(\bar{\alpha} - \frac{3\bar{\alpha}}{4})} = 2\sqrt{2} e^{j\bar{\alpha}/4} = 2\sqrt{2} \left(\cos\frac{\bar{\alpha}}{4} + j \sin\frac{\bar{\alpha}}{4}\right) = 2 + j2\sqrt{2}$

$\boxed{\bar{Z} = 2\sqrt{2} e^{j\bar{\alpha}/4} \Omega = 2 + j2\sqrt{2} \Omega}$

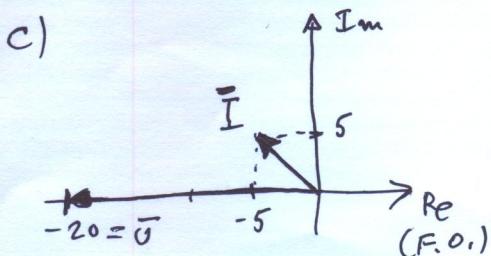b) $\bar{S} = \bar{U} \bar{i}^* = \bar{Z} \bar{i}^2 = 2\sqrt{2} e^{j\bar{\alpha}/4} \cdot (5\sqrt{2})^2 = 100\sqrt{2} e^{j\bar{\alpha}/4} = 100\sqrt{2} (\cos\bar{\alpha}/4 + j \sin\bar{\alpha}/4)$

$\bar{S} = 100\sqrt{2} e^{j\bar{\alpha}/4} \text{ VA} = 100 + j100 \text{ VA} \Rightarrow \underline{P = 100 \text{ W}, Q = 100 \text{ VAR}, S = 100\sqrt{2} \text{ VA}}$



d)

$\bar{Z}_C = -j \frac{1}{\omega C} = -j \frac{1}{1000 \cdot 250 \cdot 10^{-6}} = -j4 \Omega$

$\bar{Z}_L = \frac{\bar{Z}_C \cdot \bar{Z}}{\bar{Z}_C + \bar{Z}} = \frac{-j4(2+j2)}{-j4+2+j2} = \frac{8-j8}{2-j2} = 4 \Omega$

$\bar{Z}_e = R + jX_e = 4 + j0 \Omega \Rightarrow \cos\varphi = \frac{R_e}{Z_e} = \frac{4}{4} = 1$

$$Z_e = |Z_e| = 4 \Omega$$

d) alternativ no prevo snage:

$$P_e = P_Z + \overset{P_C}{\cancel{P}}^0 = P_Z = 100W$$

$$Q_C = -wCU^2 = -1000 \cdot 250 \cdot 10^{-6} \cdot (20)^2 = -100 \text{ VAR}$$

$$Q_e = Q_Z + Q_C = 100 - 100 = 0 \text{ VAR}$$

$$S_e = \sqrt{P_e^2 + Q_e^2} = 100 \text{ VA}$$

$$\cos \varphi = \frac{P_e}{S_e} = \frac{100}{100} = 1$$