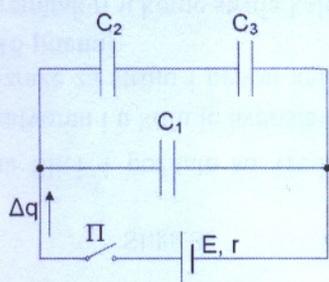



Elektrotehnika

20. februar 2023.

1. U kolu na Slici 1 poznate su kapacitivnosti kondenzatora $C_1 = 2C$, $C_2 = C_3 = C$, kao i elektromotorna sila E . Svi kondenzatori su neopterećeni, prekidač je otvoren, a u kolu je uspostavljeno stacionarno stanje.
- a) Odrediti količinu naelektrisanja, Δq , koja će proteći kroz granu sa naponskim izvorom nakon zatvaranja prekidača Π . (8 poena)
- b) Odrediti naelektrisanja, napone i elektrostatičku energiju svakog kondenzatora po uspostavljanju novog stacionarnog stanja (pri zatvorenom prekidaču). (12 poena)



Slika 1

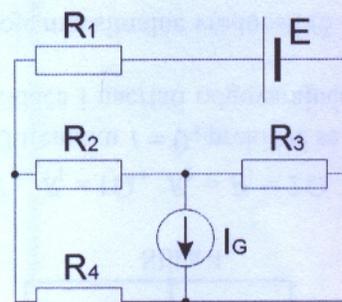


Slika 2


2. U kolu na Slici 2 poznato je: $R_1 = 10 \Omega$, $R_2 = 5 \Omega$, $R_3 = 5 \Omega$, $R_4 = 20 \Omega$, $E = 50 \text{ V}$, $I_G = 20 \text{ A}$. Odrediti struju u grani sa otpornikom R_4 primenom Thevenenove teoreme. (20 poena)

3. Na torus magnetne permeabilnosti μ_{Fe} , dužine srednje linije l_{Fe} i površine poprečnog preseka S , namotan je provodnik sa N navojaka, kao što je prikazano na Slici 3. Poznata je induktivnost namotaja L .
- a) Odrediti debljinu vazdušnog procepa l_0 . (10 poena)

- b) Ako kroz namotaj protiče struja intenziteta I , skicirati vektor jačine magnetnog polja u vazdušnom procepu i odrediti njegov intenzitet. (10 poena)

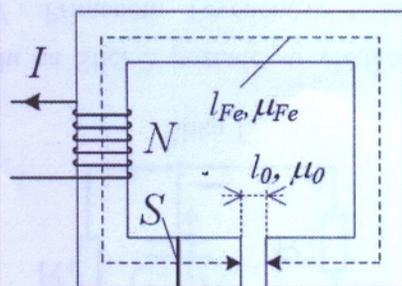

Slika 3

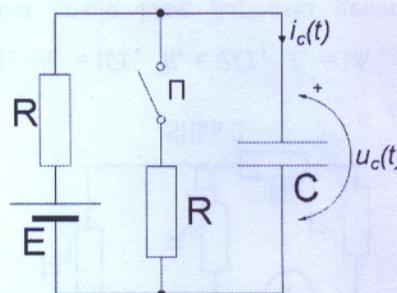

Slika 4


4. U kolu na Slici 4, poznate su vrednosti elemenata: E , R , C . Prekidač Π je otvoren i u kolu je uspostavljeno stacionarno stanje. U trenutku $t = 0$, prekidač se zatvara.

- a) Odrediti izraze za napon i struju kondenzatora nakon zatvaranja prekidača i nacrtati odgovarajuće vremenske dijagrame. (15 poena)
- b) Odrediti trenutak t_1 u kome napon kondenzatora dostiže 75% svoje maksimalne vrednosti. (5 poena)

5. U kolu naizmenične struje (Slika 5), potrošač kompleksne impedanse $\bar{Z} = (1 + j)\Omega$ priključen je na naponski izvor $u(t) = 100 \cdot \sin(100 \cdot t) \text{ V}$.


- a) Odrediti kapacitivnost kondenzatora koji je potrebno priključiti paralelno potrošaču da bi se faktor snage popravio na vrednost $\cos \varphi = 1$. (10 poena)

- b) Nacrtati fazorski dijagram za sve električne veličine označene na slici, u situaciji nakon priključenja kondenzatora. (10 poena)

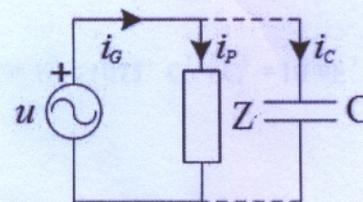

Slika 5

1

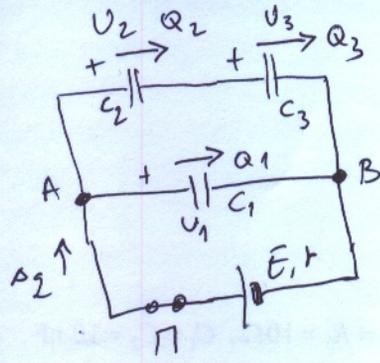

a) $C_{23} = \frac{C_2 C_3}{C_2 + C_3} = \frac{C \cdot C}{2C} = \frac{C}{2}$
 $C_1 = 2C$
 $C_{AB} = C_{123} = C_1 + C_{23} = 2C + \frac{1}{2}C = \frac{5}{2}C$


$U_{AB} = E$
 $\Delta Q_2 = Q_{AB} = U_{AB} \cdot C_{AB} = \frac{5}{2}CE$

b) $Q_1 = C_1 \cdot U_1 = 2CE$
 $U_1 = U_{AB} = E$
 $W_1 = \frac{1}{2} Q_1 U_1 = 2CE^2$


$Q_2 = Q_3 = Q_{23} = C_{23} \cdot U_{AB} = \frac{C}{2} \cdot E$

$Q_2 = Q_3 = \frac{1}{2}CE$
 $U_2 = \frac{Q_2}{C_2} = \frac{1}{2}E$
 $U_3 = \frac{Q_3}{C_3} = \frac{1}{2}E$
 $W_2 = \frac{1}{2} Q_2 U_2 = \frac{1}{8}CE^2$
 $W_3 = \frac{1}{2} Q_3 U_3 = \frac{1}{8}CE^2$


2

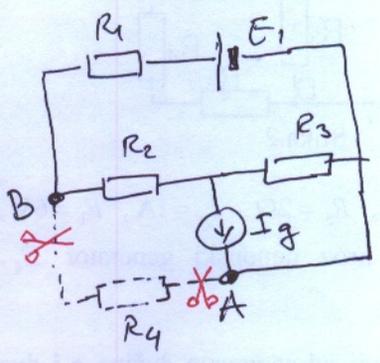

\Rightarrow

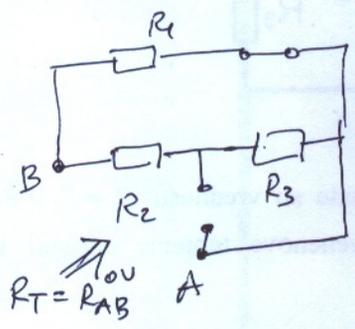


\Rightarrow

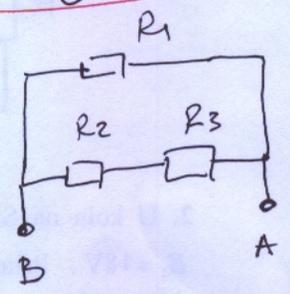

$R_T = R_1 \parallel (R_2 + R_3)$
 $R_T = \frac{R_1 \cdot (R_2 + R_3)}{R_1 + R_2 + R_3} = 5\Omega$


\Downarrow ET

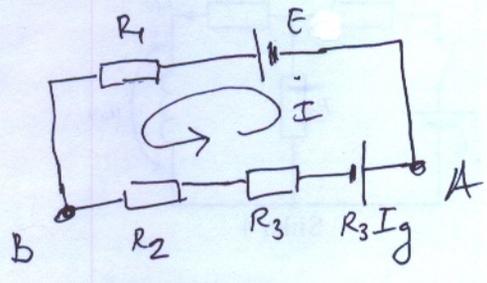

$E_T = U_{AB}^{ov}$
 $I = \frac{E + R_3 I_g}{R_1 + R_2 + R_3} = \frac{50 + 100}{20} = 7,5A$

$U_{AB}^{ov} = R_1 I - E = 75 - 50 = 25V$

$E_T = U_{AB}^{ov} = 25V$

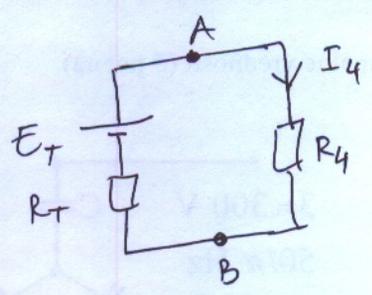

$I_4 = \frac{E_T}{R_T + R_4} = \frac{25}{20 + 5} = 1A$

3) a) $L = \frac{N^2}{R_{m0} + R_m} = \frac{N^2}{\frac{l_0}{\mu_0 S} + \frac{l_{fe}}{\mu_{fe} S}}$

$\frac{l_0}{\mu_0 S} + \frac{l_{fe}}{\mu_{fe} S} = \frac{N^2}{L}$
 $\frac{l_0}{\mu_0} = \frac{N^2 S}{L} - \frac{l_{fe}}{\mu_{fe}}$

$l_0 = \frac{\mu_0 N^2 S}{L} - \frac{\mu_0 l_{fe}}{\mu_{fe}}$


ALTERNATIVO 2:
 b) $\phi = \frac{\Psi}{N} = \frac{LI}{N}$
 $B = \frac{\phi}{S} = \frac{LI}{NS}$
 $H_0 = \frac{B}{\mu_0} = \frac{LI}{\mu_0 NS}$

b) $H_0 l_0 + H_{fe} l_{fe} = NI$
 $\frac{B l_0}{\mu_0} + \frac{B l_{fe}}{\mu_{fe}} = NI$



$B = \frac{NI}{\frac{l_0}{\mu_0} + \frac{l_{fe}}{\mu_{fe}}}$

$H_0 = \frac{B}{\mu_0} = \frac{NI}{l_0 + \frac{\mu_0 l_{fe}}{\mu_{fe}}}$

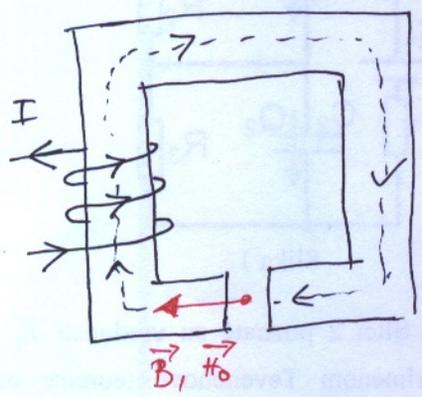
$H_0 = \frac{NI}{\frac{\mu_0 N^2 S}{L} - \frac{\mu_0 l_{fe}}{\mu_{fe}} + \frac{\mu_0 l_{fe}}{\mu_{fe}}} = \frac{NIL}{\mu_0 N^2 S} = H_0$



4) $U_{c0} = U_c(0) = E$

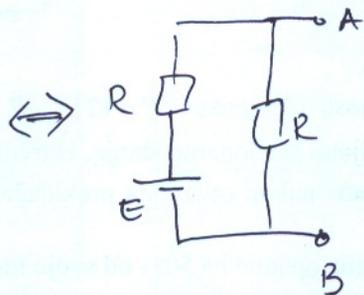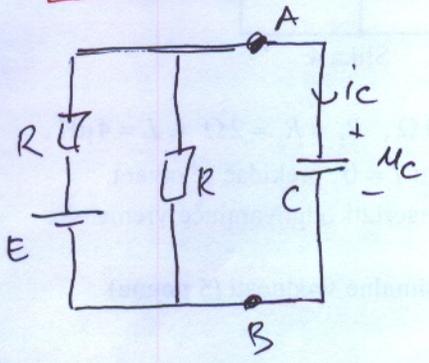

$E_T = U_{AB}^{ov} = \frac{E}{2}$
 $R_T = R_{AB}^{ov} = R || R = \frac{R}{2}$

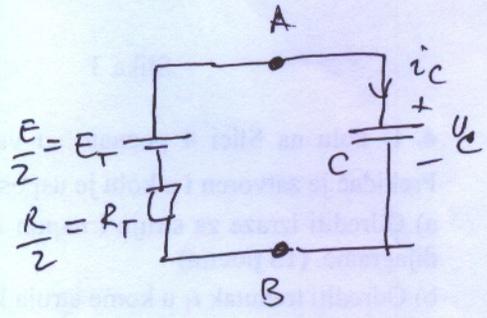

$E_T - R_T i_c - U_c = 0$
 $\frac{E}{2} i_c + U_c = \frac{E}{2}$

$\frac{RC}{2} \frac{dU_c}{dt} + U_c = \frac{E}{2} \cdot \frac{2}{RC}$


$\frac{dU_c}{dt} + \frac{U_c}{\frac{RC}{2}} = \frac{E}{RC}$

$$u_c(t) = A e^{-\frac{t}{\tau}} + B, \quad B = kE = \frac{E}{2}, \quad U_{\infty} = A + B \Rightarrow A = U_{\infty} - B = E - \frac{E}{2} = \frac{E}{2}$$

$$u_c(t) = \frac{E}{2} e^{-\frac{t}{RC/2}} + \frac{E}{2}$$

$$i_c(t) = C \frac{du_c}{dt} = C \cdot \frac{E}{2} \cdot \left(-\frac{2}{RC}\right) \cdot e^{-t/(RC/2)}$$
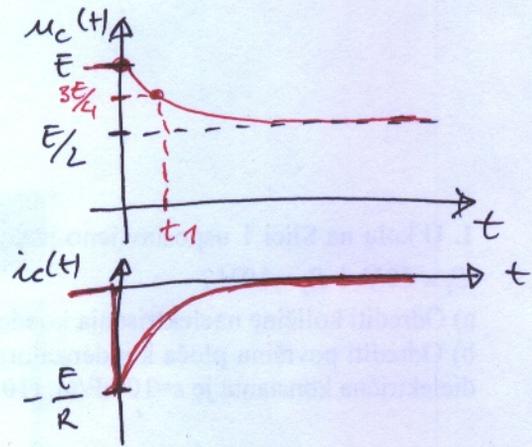
$$i_c(t) = -\frac{E}{R} e^{-\frac{t}{RC/2}}$$



$$b) \text{FSY } U_{cmax} = \text{FSY} \cdot E = \frac{3}{4} E$$

$$u_c(t_1) = \frac{E}{2} e^{-\frac{t_1}{RC/2}} + \frac{E}{2} = \frac{3}{4} E$$

$$\frac{E}{2} e^{-\frac{t_1}{RC/2}} = \frac{3}{4} E - \frac{1}{2} E = \frac{1}{4} E \quad | \cdot \left(\frac{2}{E}\right)$$

$$e^{-\frac{t_1}{RC/2}} = \frac{1}{2} \quad | \ln(\cdot)$$

$$-t_1 = \frac{RC}{2} \ln\left(\frac{1}{2}\right)$$

$$t_1 = \frac{RC}{2} \ln(2)$$

ALTERNATIVNO:

$$\begin{aligned} a) \quad \bar{Y} &= \frac{1}{Z} = \frac{1}{1+j} \cdot \frac{1-j}{1-j} = \frac{1-j}{2} \text{ S} \\ \bar{Y}_C &= j\omega C \\ \bar{Y} &= \bar{Y} + \bar{Y}_C = \frac{1}{2} + j\left(\omega C - \frac{1}{2}\right) \text{ S} \\ \cos \varphi &= 1 \Rightarrow \varphi = 0 \Rightarrow \omega C = \frac{1}{2} \\ C &= \frac{1}{2\omega} = 5 \text{ mF} \end{aligned}$$

$$5) a) U_{Um} = 100 \text{ V} \Rightarrow U = \frac{U_{Um}}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 50\sqrt{2} \text{ V}$$

$$\bar{Z} = (1+j) \Omega$$

$$\bar{S} = \frac{U^2}{\bar{Z}^*} = \frac{(50\sqrt{2})^2}{1-j} \cdot \frac{1+j}{1+j} = \frac{2500 \cdot 2}{2} (1+j) = \frac{2500}{P} + j \frac{2500}{Q} \text{ VA}$$

$$P = 2500 \text{ W}, \quad Q = 2500 \text{ VAR}$$

$$\bar{S}' = P' + jQ' \Rightarrow \cos \varphi = \frac{P'}{S'} = 1 \Rightarrow S' = P', \quad Q' = 0$$

$$P' = P + P_C \stackrel{0}{=} P = 2500 \text{ W}$$

$$0 = Q' = Q + Q_C \Rightarrow Q_C = -Q = -2500 \text{ VAR}$$

$$Q_C = -\omega C U^2 \Rightarrow C = \frac{-Q_C}{\omega U^2} = \frac{2500}{100 \cdot (50\sqrt{2})^2} = \frac{2500}{100 \cdot 2500 \cdot 2} = 5 \text{ mF}$$

$$b) \bar{U} = U = 50\sqrt{2} \text{ V}$$

$$\bar{I}_P = \frac{\bar{U}}{\bar{Z}} = \frac{50\sqrt{2}}{1+j} = \frac{1-j}{1+j} = 25\sqrt{2}(1-j) \text{ A} = \bar{I}_P$$

$$\bar{Z}_C = -j \frac{1}{\omega C} = -j 2 \Omega \Rightarrow \bar{I}_C = \frac{\bar{U}}{\bar{Z}_C} = \frac{50\sqrt{2}}{-j 2} = j 25\sqrt{2} \text{ A} = \bar{I}_C$$

$$\bar{I}_G = \bar{I}_P + \bar{I}_C = 25\sqrt{2} \text{ A}$$

