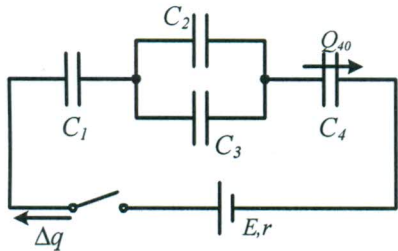



Elektrotehnika

19. februar 2021.


1. Odrediti količinu naelektrisanja Δq koja će proteći, nakon zatvaranja prekidača, kroz granu u kojoj se nalazi naponski generator (Slika 1). Pre povezivanja, kondenzatori C_1 , C_2 i C_3 su bili neopterećeni, dok je početno naelektrisanje kondenzatora C_4 poznato i iznosi Q_{40} . Poznate su kapacitivnosti kondenzatora: $C_1 = 4C$, $C_2 = C$, $C_3 = 3C$, $C_4 = 2C$, kao i elektromotorna sila naponskog generatora E . Odrediti napone i količine naelektrisanja na kondenzatorima C_1 i C_4 nakon protoka naelektrisanja Δq . (20 poena)



Slika 1

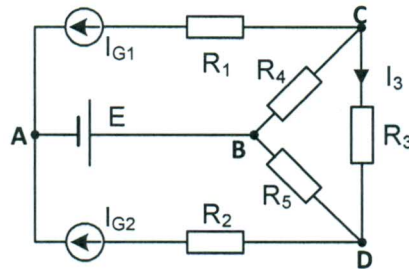

Slika 2

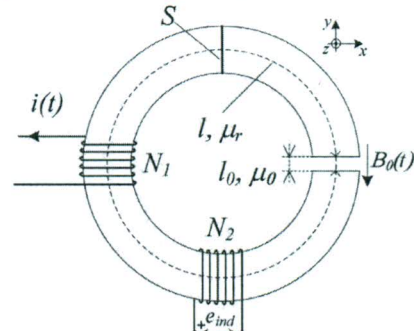

Slika 3

3. Na Slici 3 prikazano je magnetno kolo, koje se sastoji od jezgra, relativne magnetne permeabilnosti $\mu_r = 400$, dužine srednje linije $l = 40\text{cm}$, sa vazдушnim procepom debljine $l_0 = 1\text{mm}$. Poprečni presek jezgra iznosi $S = 10\text{cm}^2$. Namotaj sa $N_2 = 100$ navojaka je otvorenih krajeva, a kroz namotaj sa $N_1 = 200$ navojaka protiče struja nepoznatog intenziteta. Poznato je da se u vazдушnom procepu intenzitet vektora magnetne indukcije $\vec{B}_0(t)$ menja u vremenu po formuli $B_0(t) = B_{0m} \cos \omega t$, gde je $B_{0m} = 16\pi \text{mT}$ i $\omega = 1000 \text{rad/s}$. ($\mu_0 = 4\pi \cdot 10^{-7} \text{H/m}$)


a) Odrediti trenutnu vrednost struje $i(t)$. (10 poena)

b) Odrediti efektivnu vrednost indukovane ems (E_{ind}) u namotaju čiji su krajevi otvoreni. (10 poena)

4. U kolu na Slici 4 poznati su parametri elemenata: E , $R_1 = R_2 = 2R$, $R_3 = R$ i L . Prekidač Π je zatvoren i u kolu je uspostavljeno stacionarno stanje. U trenutku $t = 0$, prekidač se otvara.


a) Odrediti izraz za struju i napon kabela nakon otvaranja prekidača (12 p) i nacrtati odgovarajuće vremenske dijagrame (4 p).

b) Odrediti snagu generatora E u trenutku $t_1 = L/R$. (4 p)

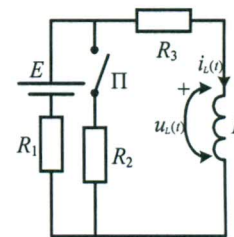


Slika 4

5. Na Slici 5 prikazana je grupa od šest elemenata kola naizmernične struje. Poznato je: $R_1 = R_2 = 10\Omega$, $X_{L1} = 20\Omega$, $X_{L2} = 10\Omega$, $X_{C1} = -10\Omega$ i $X_{C2} = -20\Omega$. Odrediti ekvivalentnu kompleksnu impedansu između tačaka E i D. (20 poena)

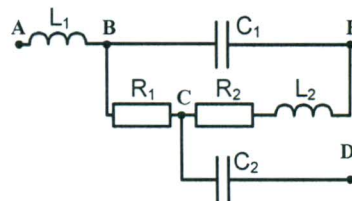


Slika 5

6. Trofazni simetrični generator, spregnut u trougao, napaja trofazni simetrični potrošač, spregnut u trougao, preko električnih vodova čija je impedansa $\bar{Z}_v = 1 + j1\Omega$, kao što je prikazano na Slici 6. Poznati su linijski napon generatora $U_l = 450 \text{V}$ i impedansa faze potrošača $\bar{Z}_\Delta = 9 + j6\Omega$. Izračunati kompleksnu prividnu, aktivnu i reaktivnu snagu generatora. (20 poena)

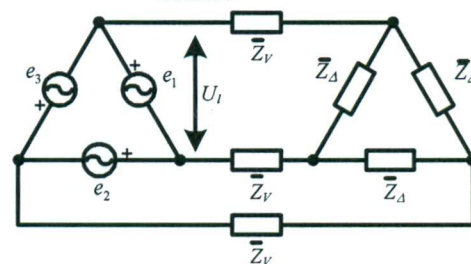

Slika 6

①

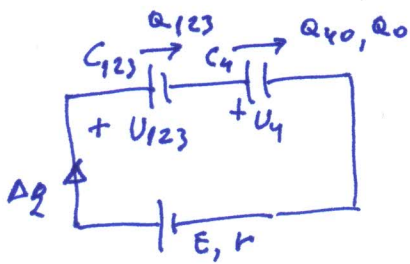

$$C_{123} = \frac{C_1(C_2+C_3)}{C_1+C_2+C_3} = \frac{4C(C+3C)}{4C+C+3C} = 2C$$

$$U_{123} + U_4 = E$$

$$\frac{Q_{123}}{C_{123}} + \frac{Q_4}{C_4} = E$$

$$\frac{\Delta q}{2C} + \frac{\Delta q + Q_{40}}{2C} = E$$


$$2\Delta q + Q_{40} = 2CE$$

$$\Delta q = CE - \frac{1}{2}Q_{40}$$

$$Q_1 = \Delta q = CE - \frac{1}{2}Q_{40}$$

$$U_1 = \frac{Q_1}{C_1} = \frac{CE - \frac{1}{2}Q_{40}}{4C}$$


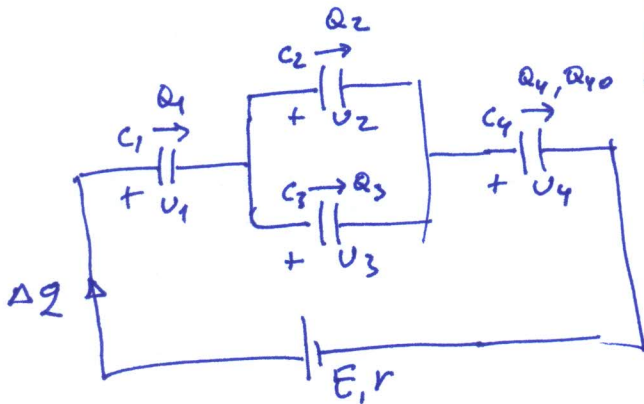
$$U_1 = \frac{E}{4} - \frac{Q_{40}}{8C}$$



$$Q_4 = \Delta q + Q_{40} = CE + \frac{1}{2}Q_{40}$$

$$U_4 = \frac{Q_4}{C_4} = \frac{CE + \frac{1}{2}Q_{40}}{2C} = \frac{E}{2} + \frac{Q_{40}}{4C} = U_4$$

② 1) Deluje samo I_{G1}

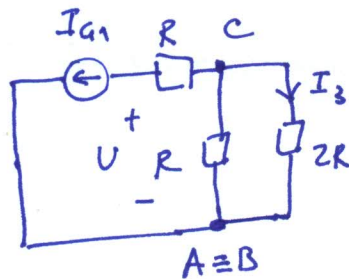
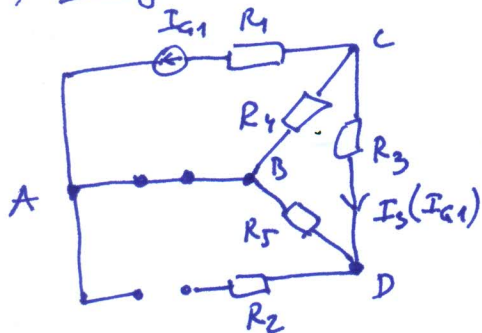


$$U = -I_{G1} \cdot (R \parallel 2R)$$

$$U = -I_{G1} \cdot \frac{R \cdot 2R}{R+2R} = -\frac{2R}{3} I_{G1}$$

$$I_3(I_{G1}) = \frac{U}{2R} = -\frac{1}{3} I_{G1} = -1A$$

2) Deluje samo I_{G2}

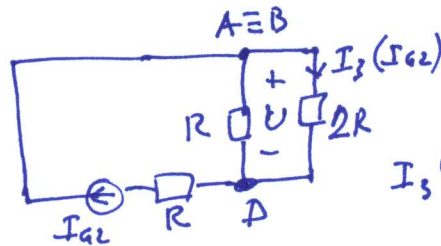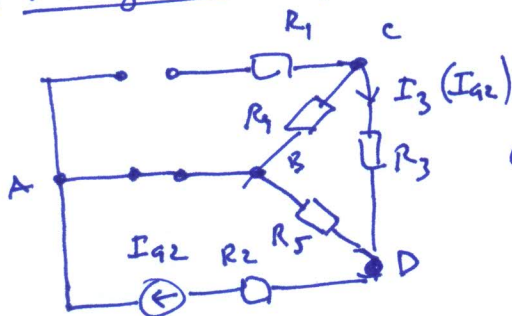


$$U = I_{G2} \cdot (R \parallel 2R)$$

$$U = I_{G2} \cdot \frac{2R}{3}$$

$$I_3(I_{G2}) = \frac{U}{2R} = \frac{1}{3} I_{G2} = 3A$$


3) Deluje samo E

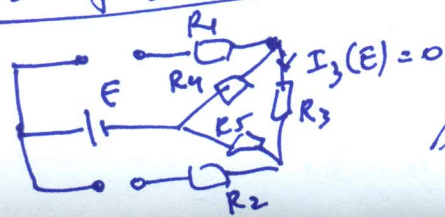

$$I_3 = I_3(I_{G1}) + I_3(I_{G2}) + I_3(E)$$

$$I_3 = -1 + 3 + 0 = 2A$$

3

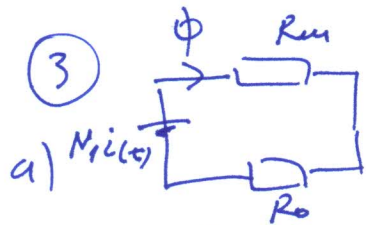

$$R_m = \frac{l}{\mu_0 \mu_r S}$$

$$R_o = \frac{l_0}{\mu_0 S}$$

$$\Phi(t) = \frac{N_1 i(t)}{R_m + R_o} = \frac{N_1}{\frac{l}{\mu_0 \mu_r S} + \frac{l_0}{\mu_0 S}} i(t)$$

$$B_o(t) = \frac{\Phi(t)}{S} = \frac{\mu_0 N_1}{l/\mu_r + l_0} i(t)$$

$$B_o(t) = B_{om} \cos(\omega t)$$

$$i(t) = \frac{B_{om} (l_0 + l/\mu_r)}{\mu_0 N_1} \cos(\omega t)$$

$$i(t) = 0,4 \cos(1000t) \text{ A}$$

b)

$$e_{ind}(t) = - \frac{d\psi_2(t)}{dt} = - \frac{d}{dt} [N_2 \cdot \Phi(t)] = - \frac{d}{dt} [N_2 S \cdot B_o(t)] = - N_2 S B_{om} \frac{d}{dt} [\cos(\omega t)]$$


$$e_{ind}(t) = N_2 S B_{om} \omega \sin(\omega t) = E_{indm} \sin(\omega t)$$

$$E_{indm} = N_2 S B_{om} \omega = 1,6 \sqrt{2} \text{ V}$$


$$E_{ind} = \frac{E_{indm}}{\sqrt{2}} = \frac{1,6 \sqrt{2}}{\sqrt{2}} \text{ V}$$

4

a) Stacionarno stanje

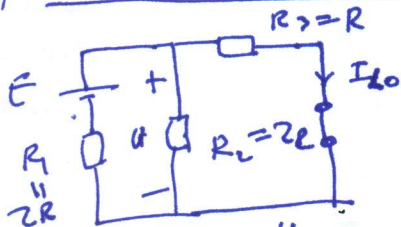
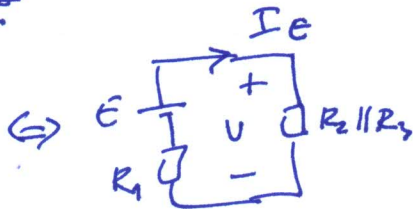
$$I_{L0} = \frac{U}{R_3} = \frac{E/4}{R} = \frac{E}{4R}$$




$$I_E = \frac{E}{R_1 + R_2 \parallel R_3}$$

$$I_E = \frac{E}{2R + \frac{2R \cdot R}{2R + R}} = \frac{3E}{8R}$$

$$U = I_E \cdot R_2 \parallel R_3 = \frac{3E}{8R} \cdot \frac{2R}{3} = \frac{E}{4}$$

PRELAZNI PROCES

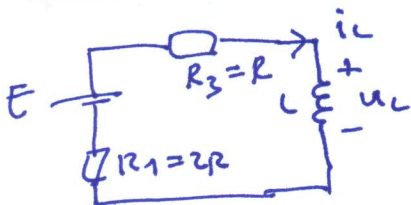

$$E - R_3 i_L - R_1 i_L - u_L = 0$$

$$3R i_L + u_L = E, \quad u_L = L \frac{di_L}{dt}$$

$$3R i_L + L \frac{di_L}{dt} = E \quad /: L$$

$$\frac{di_L}{dt} + \left(\frac{3R}{L}\right) i_L = \left(\frac{E}{L}\right) \quad \text{POČETNI USLOV: } I_{L0} = \frac{E}{4R}$$

$$i_L(t) = A e^{-t/\tau} + B$$

$$\tau = \frac{L}{3R}, \quad B = K\tau = \frac{E}{L} \cdot \frac{L}{3R} = \frac{E}{3R}$$


$$I_{L0} = A + B \Rightarrow A = I_{L0} - B = \frac{E}{4R} - \frac{E}{3R} = \frac{3E - 4E}{12R} = -\frac{E}{12R}$$

$$i_L(t) = -\frac{E}{12R} e^{-\frac{3R}{L}t} + \frac{E}{3R}$$

$$u_L(t) = L \frac{di_L}{dt} = L \cdot \left(-\frac{E}{12R}\right) \cdot \left(-\frac{3R}{L}\right) e^{-\frac{3R}{L}t} = \frac{E}{4} e^{-\frac{3R}{L}t} = u_L(t)$$

$$i_L(0) = I_{L0} = \frac{E}{4R}$$


$$i_L(\infty) = \frac{E}{3R}$$

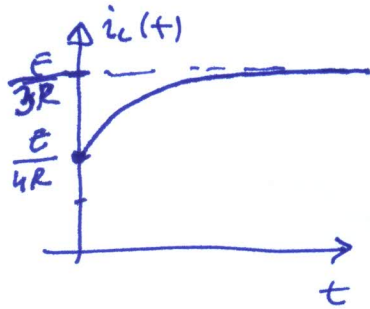

$$u_L(0^-) = 0$$

$$u_L(0^+) = \frac{E}{4}$$


$$u_L(\infty) = 0$$

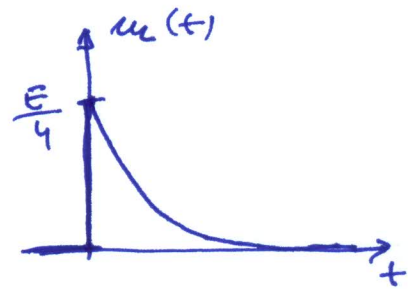

$$b) P_E(t_1) = E \cdot i_E(t_1) = E i_L(t_1) = -\frac{E^2}{12R} e^{-\frac{3R}{L} t_1} + \frac{E^2}{3R}$$

$$P_E(t_1 = \frac{L}{R}) = \frac{E^2}{3R} - \frac{E^2}{12R e^3}$$

5

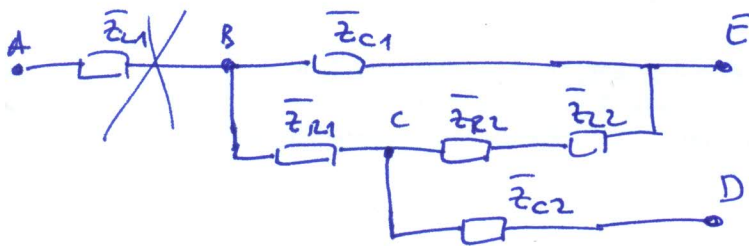

$$\bar{z}_{C1} = -j10 \Omega$$

$$\bar{z}_{C2} = -j20 \Omega$$




$$\bar{z}_{L2} = j10 \Omega$$

$$\bar{z}_{R1} = \bar{z}_{R2} = 10 \Omega$$

$$\bar{z}_{DE} = \bar{z}_{C2} + (\bar{z}_{R1} + \bar{z}_{C1}) \parallel (\bar{z}_{R2} + \bar{z}_{L2}) = -j20 + (10 - j10) \parallel (10 + j10)$$

$$\bar{z}_{DE} = -j20 \frac{(10 - j10)(10 + j10)}{10 - j10 + 10 + j10} = -j20 + \frac{100 - j^2 100}{20} = -j20 + \frac{200}{20} = 10 - j20 \Omega$$

6

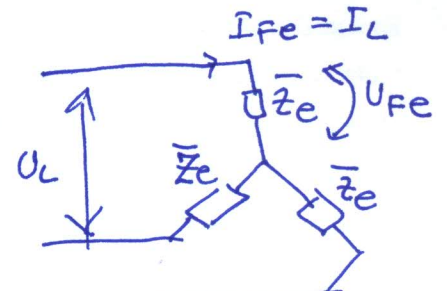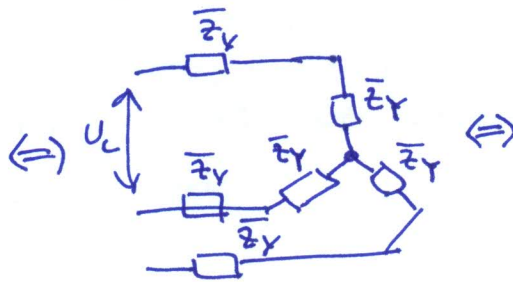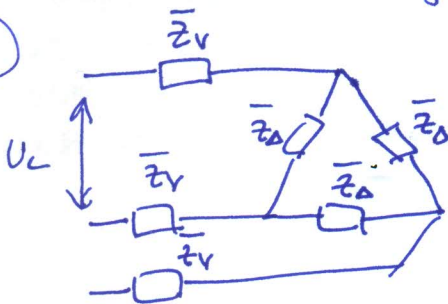

$$\bar{z}_Y = \frac{\bar{z}_D}{3} = 3 + j2 \Omega$$

$$\bar{z}_e = \bar{z}_V + \bar{z}_Y = 4 + j3 \Omega$$

SNAGE GENERATORA:

$$P_e = P_{Fe} = 3 \cdot R_e \cdot I_{Fe}^2 = 3 \cdot 4 \cdot \left(\frac{90}{\sqrt{3}}\right)^2 = 32,4 \text{ kW (AKTIVNA)}$$

$$Q_e = Q_{Fe} = 3 X_e \cdot I_{Fe}^2 = 3 \cdot 3 \cdot \left(\frac{90}{\sqrt{3}}\right)^2 = 24,3 \text{ kVAR (REAKTIVNA)}$$

$$\bar{S}_e = P_e + jQ_e = (32,4 + j24,3) \text{ kVA (KOMPLEKSNJA PRIVIDNA)}$$

$$U_{Fe} = \frac{U_L}{\sqrt{3}} = \frac{450}{\sqrt{3}} \text{ V}$$

$$z_e = \sqrt{4^2 + 3^2} = 5 \Omega$$

$$I_{Fe} = \frac{U_{Fe}}{z_e} = \frac{90}{\sqrt{3}} \text{ A}$$

$$R_e = 4 \Omega$$

$$X_e = 3 \Omega$$