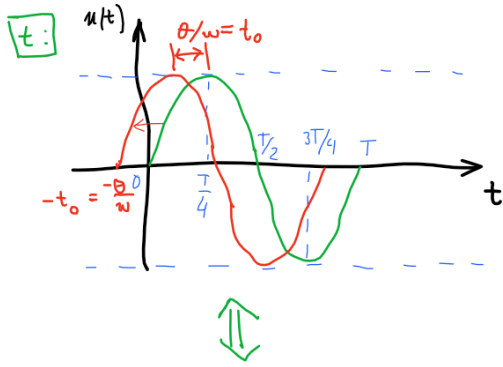


NAIZMENIČNE STRUJE



$$u(t) = \frac{U_m}{1) \quad 2) \quad 3)} \sin(\omega t + \theta)$$

1) U_m - amplituda [V]

$U = \frac{U_m}{\sqrt{2}}$ - efektivna vrednost

2) ω - kružna učestanost [rad/s]

$f = \frac{\omega}{2\pi}$ - učestanost (frekvencija) [Hz = 1/s]

$T = \frac{1}{f}$ - perioda [s]

3) $\alpha = \omega t + \theta$ - faza [rad]

$t=0: \alpha = \theta$ - početna faza [rad]


$$\begin{pmatrix} \omega t_0 = \theta \\ t_0 = \frac{\theta}{\omega} \end{pmatrix}$$

w: $\bar{U} = U e^{j\theta} = U \cos\theta + j U \sin\theta$

$U = \frac{U_m}{\sqrt{2}}$ - efektivna vrednost

θ - početna faza

ω - vektor rotiranja

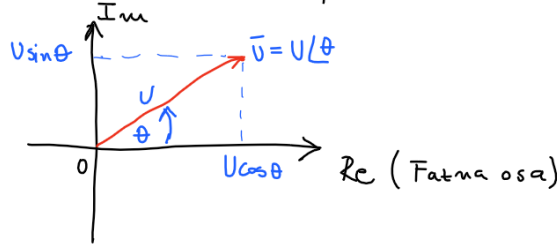

PRIMER 1:

$$u(t) = 10 \sin(314t + \frac{\pi}{4}) \text{ [V]}$$

$$U_m = 10 \text{ V}$$

$$U = \frac{10}{\sqrt{2}} = 5\sqrt{2} \text{ V}$$

$$\omega = 314 \frac{\text{rad}}{\text{s}} \Rightarrow f = \frac{314}{2 \cdot 3.14} = 50 \text{ Hz}$$


$$T = \frac{1}{f} = 20 \text{ ms}$$

$$\theta = \frac{\pi}{4} \text{ rad}$$

$$\bar{U} = U e^{j\theta} = 5\sqrt{2} e^{j\pi/4}$$


$$\bar{U} = 5\sqrt{2} \left(\cos\left(\frac{\pi}{4}\right) + j \sin\left(\frac{\pi}{4}\right) \right)$$

$$\bar{U} = 5 + j5 \text{ [V]}$$

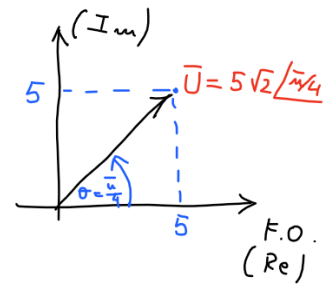

PRIMER 2:
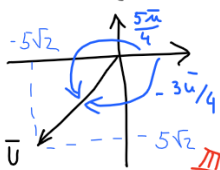
$$\bar{U} = -5\sqrt{2} - j5\sqrt{2}, \quad f = 100 \text{ Hz}$$



$$U = |\bar{U}| = \sqrt{(-5\sqrt{2})^2 + (-5\sqrt{2})^2} = 10 \text{ V}$$

$$\theta = \arg\{\bar{U}\} = \arctg \frac{-5\sqrt{2}}{-5\sqrt{2}} + k\pi$$

$$\theta = \arctg(1) + k\pi = \frac{\pi}{4} + k\pi$$

ili: $\theta = \frac{\pi}{4} + \pi = \frac{5\pi}{4}$

$$\Leftrightarrow \bar{U} = 10 e^{-j3\pi/4} \text{ V}$$

1) $U_m = U\sqrt{2} = 10\sqrt{2} \text{ V}$

2) $\omega = 2\pi f = 628 \frac{\text{rad}}{\text{s}}$

3) $\theta = -3\pi/4 \text{ rad}$


$$u(t) = \frac{10\sqrt{2}}{1) \quad 2) \quad 3)} \sin(628t - \frac{3\pi}{4}) \text{ V}$$

KORISTIMO SINUS!

PRIMER 3:

$$\bar{I} = -10\sqrt{3} + j10 \text{ A}$$
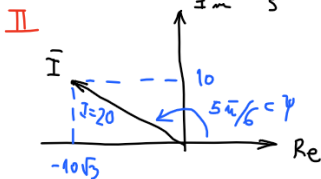
$$\omega = 314 \frac{\text{rad}}{\text{s}}$$




$$I = |\bar{I}| = \sqrt{(-10\sqrt{3})^2 + 10^2} = \sqrt{10^2 \cdot (3+1)} = \sqrt{10^2 \cdot 2^2} = 20 \text{ A} \Rightarrow I_m = 20\sqrt{2} \text{ A}$$

$$\psi = \arctg \frac{10}{-10\sqrt{3}} + k\pi = -\arctg \frac{\sqrt{3}}{3} + k\pi = -\frac{\pi}{6} + k\pi$$

ili: $\psi = -\frac{\pi}{6} + \pi = \frac{5\pi}{6}$
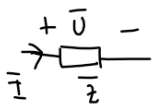
$$i(t) = 20\sqrt{2} \sin(314t + \frac{5\pi}{6}) \text{ A}$$



$$\bar{Z} = Z e^{j\varphi} = R + jX$$

\bar{Z} - kompleksna impedansa [Ω]

Z - impedansa [Ω]


R - rezistansa [Ω]

X - reaktansa [Ω]

$X > 0$ - induktivni

$X < 0$ - kapacitivni

$X = 0$ - rezistivni

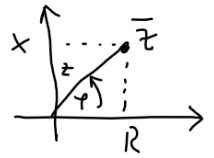

SNAGA: $\bar{S} = S e^{j\varphi} = P + jQ$

\bar{S} - kompleksna prividna snaga [VA]

S - prividna snaga [VA]


P - aktivna snaga [W]

Q - reaktivna snaga [VAR]

$Q > 0$ - induktivni

$Q < 0$ - kapacitivni


$Q = 0$ - rezistivni

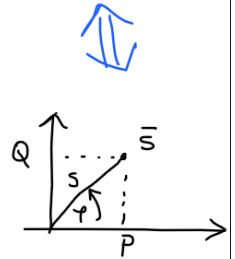

$$\bar{S} = \bar{U} \bar{I}^* = \bar{Z} \cdot \bar{I} \cdot \bar{I}^* = \bar{Z} I^2 = \underbrace{R I^2}_P + j \underbrace{X I^2}_Q$$

$$\bar{S} = \underbrace{Z I^2}_S e^{j\varphi}$$

OTPORNIK:

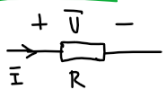

$$u(t) = R i(t)$$


$$\bar{Z}_R = R [\Omega]$$

$$\bar{U} = \bar{Z}_R \bar{I} = R \bar{I}$$


$$U e^{j\theta} = R I e^{j\varphi} \Rightarrow U = R I, \theta = \varphi$$

$$\bar{S}_R = \bar{Z}_R \cdot I^2 = R I^2 \Rightarrow P_R = R I^2 [W]$$

$$Q_R = 0 [VAR]$$

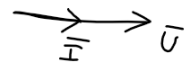

KALEM:

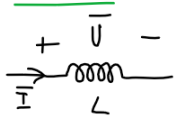

$$u(t) = L \frac{di(t)}{dt}$$

$$X_L = \omega L [\Omega]$$

$$\bar{Z}_L = +jX_L = j\omega L = \omega L e^{j\pi/2}$$


$$\bar{U} = \bar{Z}_L \bar{I}$$

$$U e^{j\theta} = \omega L I e^{j(\varphi + \pi/2)} \Rightarrow U = X_L I, \theta = \varphi + \pi/2$$


$$\bar{S}_L = \bar{Z}_L \cdot I^2 = jX_L I^2 = j\omega L I^2 [VA]$$

$$P_L = 0 W$$

$$Q_L = \omega L I^2 [var] > 0$$

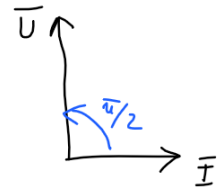

KONDENZATOR:

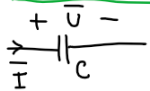

$$i(t) = C \frac{du(t)}{dt}$$

$$X_C = \frac{1}{\omega C} [\Omega]$$


$$\bar{Z}_C = -jX_C = -j \frac{1}{\omega C} = \frac{1}{\omega C} e^{-j\pi/2}$$

$$\bar{U} = \bar{Z}_C \bar{I} = \frac{I}{\omega C} e^{j(\varphi - \pi/2)} \Rightarrow U = X_C I, \theta = \varphi - \pi/2$$

$$\bar{S}_C = \bar{Z}_C I^2 = -jX_C I^2 = -j \frac{I^2}{\omega C} [VA]$$

$$P_C = 0 W$$
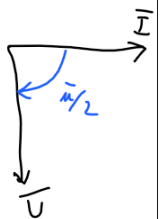
$$Q_C = -X_C I^2 = -\frac{I^2}{\omega C} [VAR] < 0$$



1. Odrediti kompleksnu impedansu \bar{Z} , ako je poznato da je vremenski oblik napona na impedansi $u(t) = 30 \sin(314t - 15^\circ)$ V i struje $i(t) = 15 \sin(314t + \frac{\pi}{12})$ A.

$$\bar{U} = \frac{30}{\sqrt{2}} e^{-j\pi/12} V$$

$$\bar{I} = \frac{15}{\sqrt{2}} e^{+j\pi/12} A$$

$$\bar{Z} = \frac{\bar{U}}{\bar{I}} = \frac{30/\sqrt{2}}{15/\sqrt{2}} e^{-j(\pi/12 + \pi/12)} = 2 e^{-j\pi/6} \Omega$$

$$\bar{Z} = 2 \cos \frac{\pi}{6} - j 2 \sin \frac{\pi}{6} = \sqrt{3} - j \Omega$$



$$\bar{Z} = R - j \frac{1}{\omega C}$$

$$R = \sqrt{3} \Omega$$

$$\frac{1}{\omega C} = 1 \Rightarrow C = \frac{1}{314} = 3,18 \text{ mF}$$