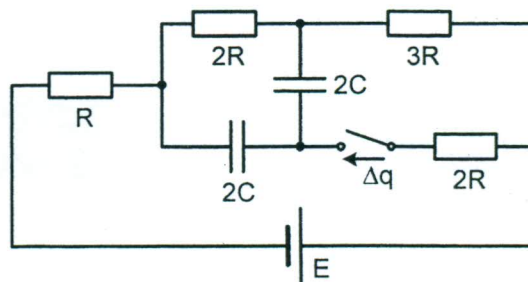


Elektrotehnika


02. februar 2022.

1. U kolu na Slici 1 poznate su vrednosti E , R i C . Kondenzatori su bili neopterećeni pre povezivanja u kolo. Prekidač je otvoren i uspostavljeno je stacionarno stanje. Odrediti količinu naelektrisanja Δq koja će proteći kroz granu sa prekidačem nakon njegovog zatvaranja. (20 poena)




Slika 1

2. U kolu jednosmerne struje sa Slike 2, potrebno je izračunati intenzitete struja koje protiču kroz otpornik R_2 i generator E , primenom metode konturnih struja. Poznato je: $I_G = 2\text{ A}$, $E = 80\text{ V}$, $R_1 = R_2 = R_3 = R_4 = R_5 = 10\ \Omega$. (20 poena)

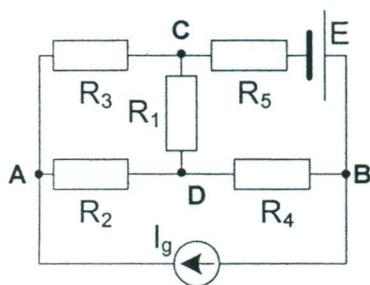

Slika 2

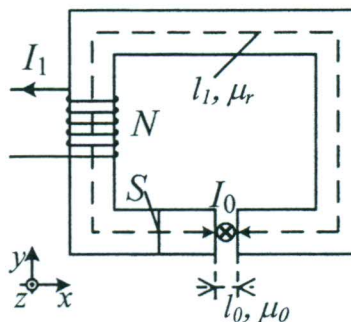


Slika 3

3. Na pravougaonom jezgru od feromagnetnog materijala (Slika 3), relativne magnetne permeabilnosti $\mu_r = 1000$, sa vazдушnim procepom debljine $l_0 = 0.2\text{ mm}$, ravnomerno je namotano $N = 200$ navojaka kroz koje protiče struja intenziteta $I_1 = 5\text{ A}$. Dužina srednje linije magnetnog jezgra je $l_1 = 20\text{ cm}$, a površina poprečnog preseka jezgra, oblika kvadrata, iznosi $S = 4\text{ cm}^2$. Odrediti i skicirati vektor sile koja deluje na tanak pravolinijski provodnik, postavljen u vazдушnom procepu na način prikazan na slici, kroz koji protiče struja intenziteta $I_0 = 1\text{ A}$. ($\mu_0 = 4\pi \cdot 10^{-7}\text{ H/m}$) (20 poena)


4. U kolu na Slici 4, poznate su vrednosti elemenata: $E = 200\text{ V}$, $R = 10\ \Omega$, $C = 2\ \mu\text{F}$. Prekidač je otvoren i u kolu je uspostavljeno stacionarno stanje. U trenutku $t = 0$, prekidač se zatvara.

a) Odrediti izraze za struju i napon kondenzatora nakon zatvaranja prekidača i nacrtati odgovarajuće vremenske dijagrame. (15 poena)

b) Odrediti vrednost energije električnog polja kondenzatora u trenutku $t_1 = 120\ \mu\text{s}$. (5 poena)

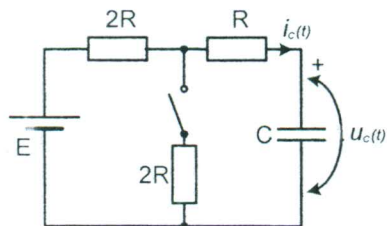

Slika 4

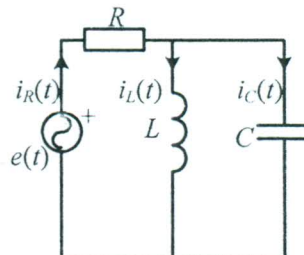


Slika 5

5. U kolu na Slici 5 poznato je: $e(t) = 200\sin(1000t + \pi/4)\text{ V}$, $R = 10\ \Omega$, $L = 10\text{ mH}$, $C = 200\ \mu\text{F}$.

a) Odrediti kompleksne struje u svim granama i kompleksne napone na otporniku, kalemu i kondenzatoru, (10 poena)

b) Odrediti vremenski oblik struje kondenzatora, (4 poena)

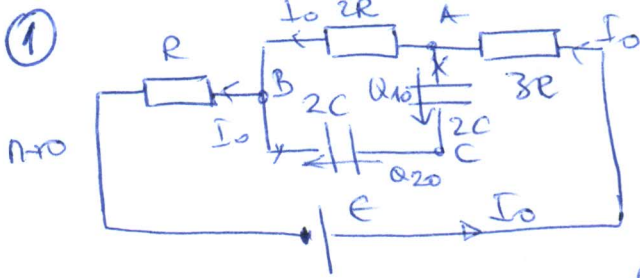c) Odrediti aktivnu, reaktivnu i prividnu snagu celokupnog potrošača. (6 poena)




$$I_0 = \frac{\epsilon}{3R+2R+R} = \frac{\epsilon}{6R}$$

$$U_{AB} = 2R I_0 = \frac{\epsilon}{3}$$

$$U_{AC} = U_{CB} = \frac{U_{AB}}{2} = \frac{\epsilon}{6}$$
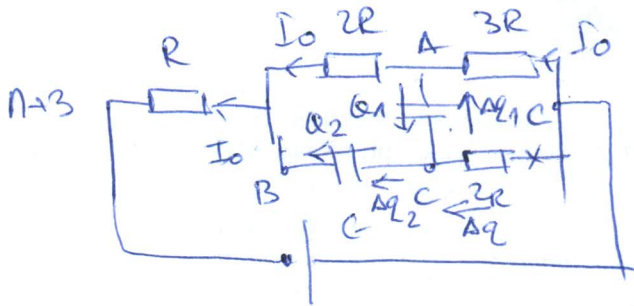
$$Q_{10} = Q_{20} = 2C \cdot U_{AC} = \frac{2C\epsilon}{3}$$



$$I_0 = \frac{\epsilon}{3R+2R+R} = \frac{\epsilon}{6R}$$

$$U_{AC} = -3R I_0 = -\frac{\epsilon}{2}$$

$$U_{CB} = 5R I_0 = \frac{5\epsilon}{6}$$


$$Q_1 = U_{AC} \cdot 2C = -C\epsilon$$

$$Q_2 = U_{CB} \cdot 2C = \frac{5\epsilon C}{3}$$

$$Q_1 = Q_{10} - \Delta Q_1 \Rightarrow \Delta Q_1 = Q_{10} - Q_1 = \frac{4}{3} C\epsilon$$

$$Q_2 = Q_{20} + \Delta Q_2 \Rightarrow \Delta Q_2 = Q_2 - Q_{20} = \frac{4}{3} C\epsilon$$
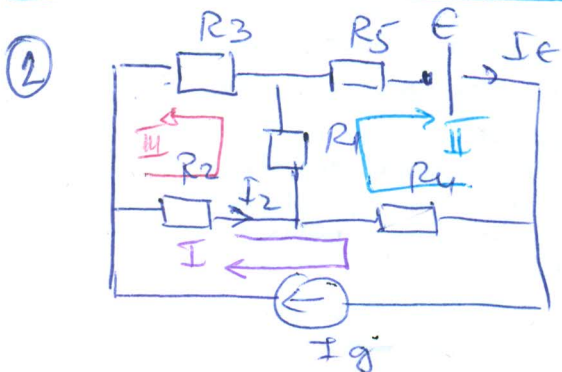
$$\Delta Q = \Delta Q_1 + \Delta Q_2 = \frac{8}{3} C\epsilon$$



$$\bar{I}_I = I_g$$

$$-R_4 I_I + (R_1 + R_4 + R_5) I_{II} + R_1 I_{III} = E$$

$$R_2 I_I + R_1 I_{II} + (R_2 + R_1 + R_3) I_{III} = 0$$

$$-R I_I + 3R I_{II} + R I_{III} = E \quad /: R$$

$$R I_I + R I_{II} + 3R I_{III} = 0 \quad /: R$$

$$I_I = I_g$$

$$3I_{II} + I_{III} = \frac{E}{R} + I_g$$

$$I_{II} + 3I_{III} = -I_g \Rightarrow I_{II} = -3I_{III} - I_g$$

$$3(-3I_{III} - I_g) + I_{III} = \frac{E}{R} + I_g$$

$$I_{II} = -3I_{III} - I_g$$

$$I_{II} = -3I_{III} - I_g$$

$$-9I_{III} - 3I_g + I_{III} = \frac{E}{R} + I_g$$

$$I_{III} = -3I_{III} - I_g$$

$$-8I_{III} = \frac{E}{R} + 4I_g$$


$$I_{III} = \frac{-I_g}{2} - \frac{E}{8R} = \frac{-2}{2} - \frac{80}{80} = -2A$$

$$I_{II} = -3I_{III} - I_g = -3(-2) - 2 = 6 - 2 = 4A$$

$$\bar{I}_2 = I_I + I_{III}$$

$$= 2 + (-2) = 0A$$

$$I_e = I_{II} = 4A$$

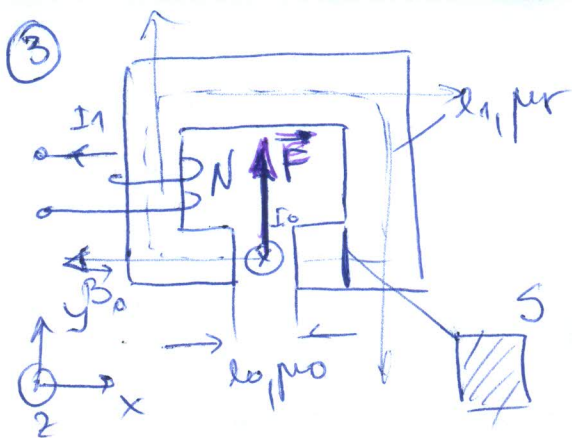

$$\oint \vec{H} \cdot d\vec{l} = \sum I$$

$$H_1 l_1 + H_0 l_0 = N I_1$$

$$\frac{B l_1}{\mu_0 \mu_r} + \frac{B l_0}{\mu_0} = N I_1$$



$$B = \frac{N I_1 \mu_0}{\frac{l_1}{\mu_r} + l_0} = \mu T$$

$$\vec{B}_0 = B \cdot (-\vec{i})$$

$$\vec{F} = I_0 \vec{l} \times \vec{B}_0 = I_0 \sqrt{s} (\vec{k}) \times B_0 (-\vec{i})$$

$$\vec{F} = I_0 B \sqrt{s} \vec{k} \times (-\vec{i}) = I_0 B \sqrt{s} \vec{j}$$
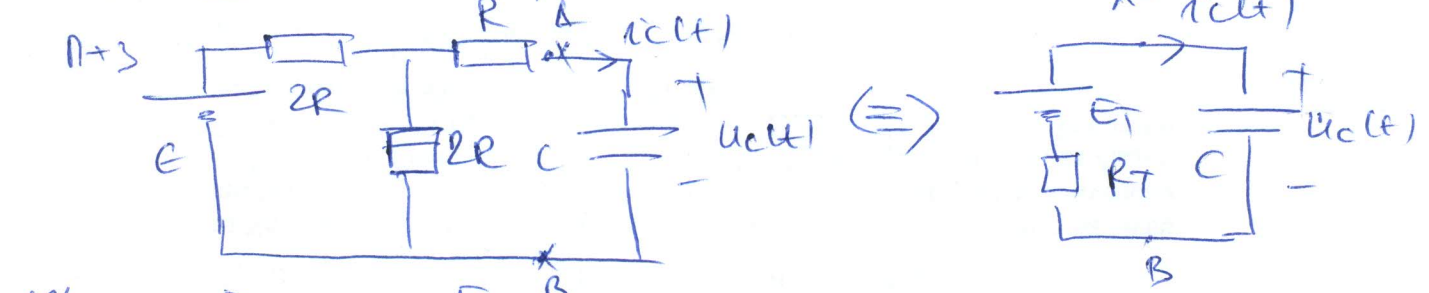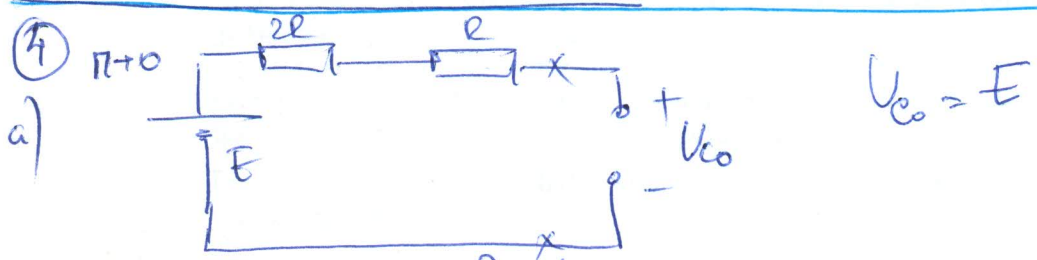
$$\boxed{\vec{F} = 20\pi \vec{j} \mu N = 9.02\pi \vec{j} N}$$



$$U_{AB} = E_T = \frac{E}{2R+2R} \cdot 2R = \frac{E}{2}$$

$$R_T = R + 2R \parallel 2R = R + R = 2R$$

$$i(t) = C \frac{du_c(t)}{dt}$$

$$E_T - R_T i(t) - u_c(t) = 0 \Rightarrow u_c(t) = A e^{-t/\tau} + B$$

$$E_T - R_T C \frac{du_c(t)}{dt} - u_c(t) = 0$$


$$\frac{du_c(t)}{dt} + \frac{u_c(t)}{R_T C} = \frac{E_T}{R_T C}$$

$$\tau = R_T C = 2RC = 40 \mu s$$


$$k = \frac{E_T}{R_T C} = \frac{E}{4RC}$$

$$B = k \cdot \tau = \frac{E}{2}$$
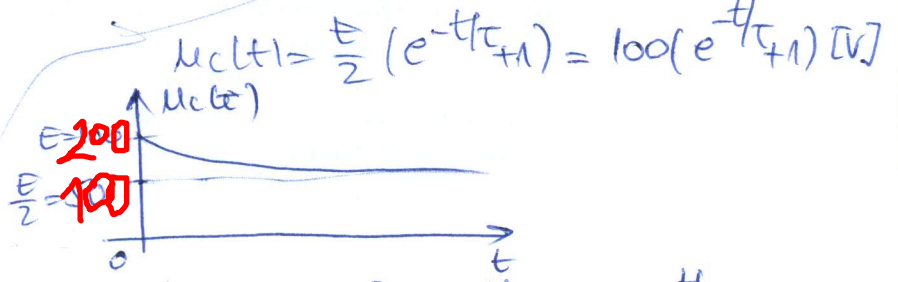
$$A + B = U_{co} = 1 \Rightarrow A = \frac{E}{2}$$


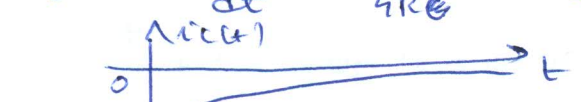
$$u_c(t) = \frac{E}{2} (e^{-t/\tau} + 1) = 100 (e^{-t/40} + 1) [V]$$




$$i(t) = C \frac{du_c(t)}{dt} = -\frac{E}{4RC} e^{-t/\tau} = -5 e^{-t/40} [A]$$

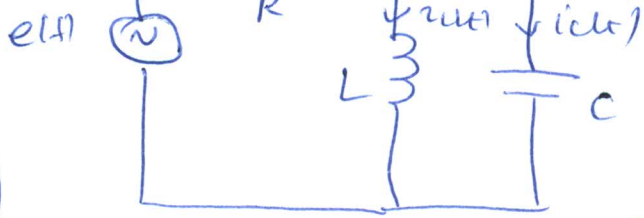b) $t_1 = 120 \mu s$ $\tau = 40 \mu s$

$$W_{el}(t_1) = \frac{1}{2} C u_c^2(t_1) = \frac{1}{2} \cdot 2 \mu \cdot (100 (1 + e^{-3}))^2 = 10^{-6} \cdot 10^4 (1 + e^{-3})^2$$

$$\boxed{W_{el}(t_1) = 10^{-2} (1 + e^{-3})^2 \approx 11.02 \mu J}$$



$$e(t) = 200 \sin(1000t + \frac{\pi}{4}) [V]$$

$$\bar{E} = \frac{200}{\sqrt{2}} e^{j\pi/4} = 100\sqrt{2} e^{j\pi/4} [V]$$

$$R = 10 \Omega \quad L = 10 \text{ mH} \quad C = 200 \mu\text{F}$$

$$\bar{Z}_L = j\omega L = j \cdot 1000 \cdot 10 \cdot 10^{-3} = j10 \Omega$$

$$\bar{Z}_C = \frac{1}{j\omega C} = \frac{1}{j \cdot 10^3 \cdot 200 \cdot 10^{-6}} = -j \frac{10^3}{200} = -j5 \Omega$$

$$\bar{Z}_{LC} = \frac{\bar{Z}_L \cdot \bar{Z}_C}{\bar{Z}_L + \bar{Z}_C} = \frac{j10 \cdot (-j5)}{j10 - j5} = -j10 \Omega$$

$$\bar{Z}_e = R + \bar{Z}_{LC} = 10(1 - j) \Omega = 10\sqrt{2} \left(\frac{\sqrt{2}}{2} - j \frac{\sqrt{2}}{2} \right) = 10\sqrt{2} e^{j\pi/4} \Omega$$

$$\bar{I}_R = \frac{\bar{E}}{\bar{Z}_e} = \frac{100\sqrt{2} e^{j\pi/4}}{10\sqrt{2} e^{-j\pi/4}} = 10 e^{j\pi/2} = \boxed{j10 \text{ A} = I_R}$$

$$\bar{U}_{LC} = \bar{Z}_{LC} \cdot \bar{I}_R = -j10 \cdot j10 = \boxed{100 \text{ V} = \bar{U}_L = \bar{U}_C}$$

$$\bar{I}_L = \frac{\bar{U}_{LC}}{\bar{Z}_L} = \frac{100}{j10} = -j10 \text{ A}$$

$$\bar{I}_C = \frac{\bar{U}_{LC}}{\bar{Z}_C} = \frac{100}{-j5} = j20 \text{ A}$$

$$\bar{U}_R = R \cdot \bar{I}_R = j100 \text{ V}$$

b) $\bar{I}_C = j20 \text{ A} \Rightarrow I_C = 20 \text{ A} \quad I_{\text{eff}} = 20\sqrt{2} \text{ A}$
 $\bar{I}_e = 20 e^{j\pi/2} \quad \varphi_C = \pi/2$

$$i_C(t) = 20\sqrt{2} \sin(1000t + \pi/2) [A]$$

c) $\bar{S} = \bar{E} \bar{I}_e^* = \bar{Z}_e \bar{I}_e^2 = 10\sqrt{2} e^{-j\pi/4} \cdot 100 = 1000\sqrt{2} e^{-j\pi/4} \text{ VA}$

$$S = 1000\sqrt{2} \text{ VA} = \sqrt{2} \text{ kVA}$$

$$P = 1000 \text{ W} = 1 \text{ kW}$$

$$Q = -1000 \text{ VAR} = -1 \text{ kVAR}$$

$$= 1000\sqrt{2} \left(\frac{\sqrt{2}}{2} - j \frac{\sqrt{2}}{2} \right)$$

$$= (1000 - j1000) \text{ VA}$$