


# Elektrotehnika

01. februar 2023.


1. U kolu na Slici 1 uspostavljeno je stacionarno stanje. Poznato je  $R_1 = R_2 = R_3 = 10\Omega$ ,  $C_1 = C_2 = 10\text{ nF}$ ,  $E_1 = 40\text{ V}$  i  $E_2 = 10\text{ V}$ .

a) Odrediti količine naelektrisanja kondenzatora  $C_1$  i  $C_2$ . (10 poena)

b) Odrediti površinu ploča kondenzatora  $S_1$  i  $S_2$  ako polje u svakom od kondenzatora iznosi  $K=10^4\text{ V/m}$ , a dielektrična konstanta je  $\epsilon=10\text{ nF/m}$ . (10 poena)

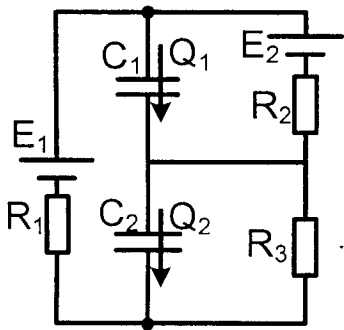


Slika 1

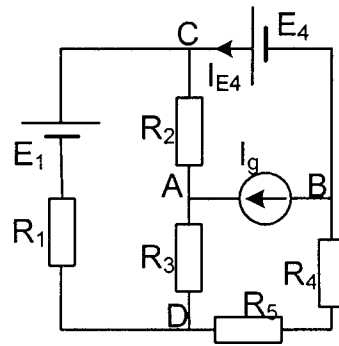


Slika 2

2. U kolu na Slici 2 poznate su vrednosti  $R_1 = R_2 = R_3 = 3\Omega$ ,  $R_4 = 1\Omega$ ,  $R_5 = 2\Omega$ ,  $I_g = 1\text{ A}$ ,  $E_1 = 6\text{ V}$ ,  $E_4 = 18\text{ V}$ . Primenom Tevenenove teoreme odrediti intenzitet struje kroz naponski generator  $E_4$ . (20 poena)

3. Na Slici 3 je prikazan izlomljeni pravolinijski provodnik, koji se sastoji od segmenta dužine  $a$  i dva veoma dugačka segmenta. Provodnik se nalazi u vazduhu, a kroz njega protiče struja intenziteta  $I$ . Odrediti i skicirati vektor magnetne indukcije u tački M. (20 poena)

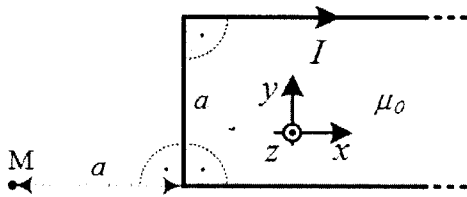

Slika 3

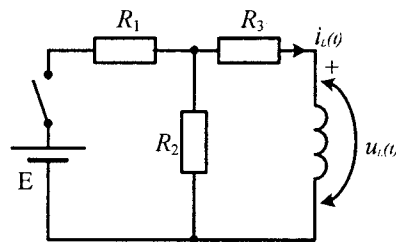

Slika 4

4. U kolu na Slici 4 poznate su vrednosti elemenata:  $E = 12\text{ V}$ ,  $R_1 = 1\Omega$ ,  $R_2 = R_3 = 2\Omega$  i  $L = 4\mu\text{H}$ . Prekidač je zatvoren i u kolu je uspostavljeno stacionarno stanje. U trenutku  $t = 0$ , prekidač se otvara.

a) Odrediti izraze za struju i napon kalemata nakon otvaranja prekidača i nacrtati odgovarajuće vremenske dijagrame. (15 poena)

b) Odrediti trenutak  $t_1$  u kome struja kalemata opadne na 50% od svoje maksimalne vrednosti (5 poena)


5. Na Slici 5 prikazan je simetrični trofazni, čisto kapacitivni potrošač, priključen na trofazni sistem napona  $3 \times 300\text{ V}$ , učestanosti  $f = \frac{50}{\pi}\text{ Hz}$ .

Kapacitivnost kondenzatora iznosi  $C = 0.1\text{ mF}$ . Odrediti:


a) efektivnu vrednost linijske struje. (10 poena)

b) prividnu i reaktivnu snagu potrošača. (6 poena)

c) faktor snage potrošača. (4 poena)

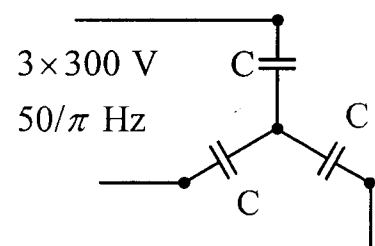

Slika 5

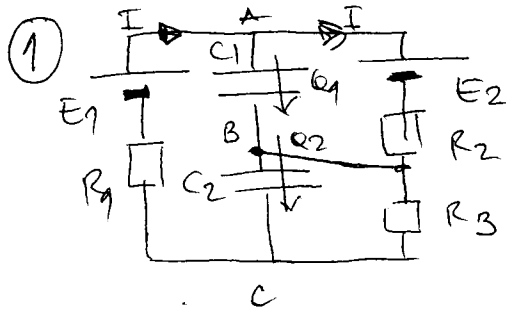

a)  $I = \frac{E_1 - E_2}{R_1 + R_2 + R_3} = \frac{40 - 10}{30} = 1 \text{ A}$

$U_1 = U_{AB} = E_2 + R_2 I = 10 + 10 = 20 \text{ V}$

$Q_1 = U_1 \cdot C_1 = 2000 \text{ C}$

$U_2 = U_{BC} = R_3 \cdot I = 10 \text{ V}$


$Q_2 = U_2 \cdot C_2 = 1000 \text{ C}$

b)  $K_1 = \frac{U_1}{d_1} \Rightarrow d_1 = \frac{U_1}{K_1} = \frac{20}{10^4} = 2 \cdot 10^{-3} \text{ m}$

$K_2 = \frac{U_2}{d_2} \Rightarrow d_2 = \frac{U_2}{K_2} = \frac{10}{10^4} = 10^{-3} \text{ m}$

$C_1 = \epsilon \frac{S_1}{d_1} \Rightarrow S_1 = \frac{C_1 \cdot d_1}{\epsilon} = \frac{10^{-6} \cdot 2 \cdot 10^{-3}}{10^{-9}} = 2 \cdot 10^{-3} \text{ m}^2 = S_1$

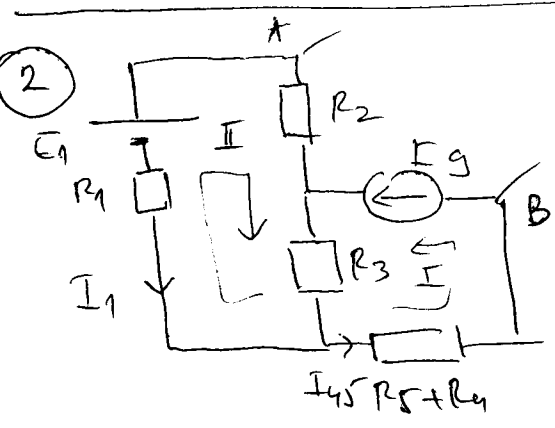$C_2 = \epsilon \frac{S_2}{d_2} \Rightarrow S_2 = \frac{C_2 \cdot d_2}{\epsilon} = \frac{10^{-6} \cdot 10^{-3}}{10^{-9}} = 1 \cdot 10^{-3} \text{ m}^2 = S_2$



$E_T = U_{AB}^{OV} = E_1 + R_1 I_1 + (R_4 + R_5) I_4$

$I_I = I_g$

$R_3 I_I + (R_1 + R_2 + R_3) I_{II} = E_1$

$I_{II} = \frac{E_1 - R_3 I_g}{R_1 + R_2 + R_3} \quad I_I = I_g$


$I_1 = -I_{II} = \frac{R_3 I_g - E_1}{R_1 + R_2 + R_3}$

$I_{45} = I_I = I_g$

$E_T = 8 \text{ V}$

$R_1 = R_2 = R_3 = R$   
 $R_4 + R_5 = R$

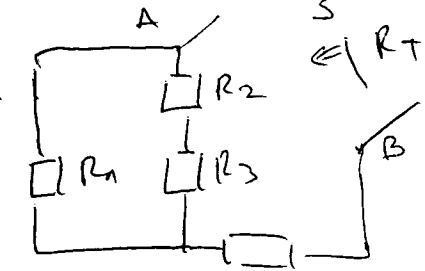
$E_T = E_1 + R_1 \frac{R_3 I_g - E_1}{R_1 + R_2 + R_3} + (R_4 + R_5) I_g = E_1 + R \cdot \frac{R I_g - E_1}{3R} + R I_g$   
 $= E_1 + \frac{R I_g}{3} - \frac{E_1}{3} + R I_g = \frac{2}{3} E_1 + \frac{4}{3} R I_g = \frac{2}{3} \cdot 6 + \frac{4}{3} \cdot 3 \cdot 1 = 8 \text{ V}$



$R_T = R_4 + R_5 + R_1 \parallel (R_2 + R_3)$

$= R + R \parallel 2R = R + \frac{R \cdot 2R}{3R} = \frac{5}{3} R = 5 \Omega$


$R_T = 5 \Omega$

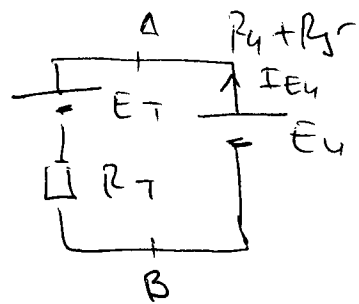

$I_{E4} = \frac{E_4 - E_T}{R_T} = \frac{18 - 8}{5} = \frac{10}{5} = 2 \text{ A}$

$I_{E4} = 2 \text{ A}$

3

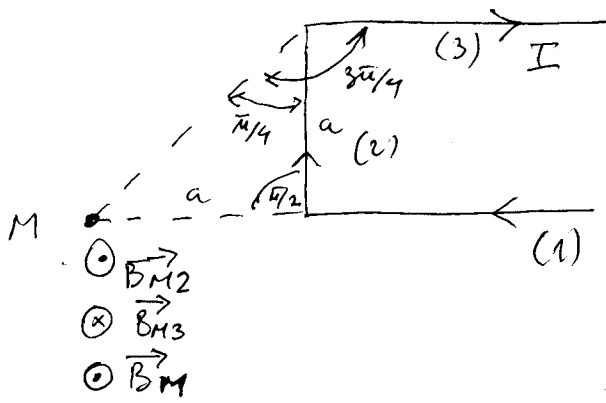

$$\vec{B}_M = \vec{B}_{M1} + \vec{B}_{M2} + \vec{B}_{M3}$$

$$\vec{B}_{M1} = \vec{0}$$

$$\vec{B}_{M2} = \frac{\mu_0 I}{4\pi a} (\cos \frac{\pi}{2} + \cos \frac{\pi}{4}) \cdot \vec{k}$$

$$\vec{B}_{M2} = \frac{\mu_0 I \sqrt{2}}{8\pi a} \vec{k} - \frac{\sqrt{2}}{2}$$


$$\vec{B}_{M3} = \frac{\mu_0 I}{4\pi a} (\cos \frac{3\pi}{4} + \cos 0) (-\vec{k})$$

$$\vec{B}_{M3} = \frac{\mu_0 I (2 - \sqrt{2})}{8\pi a} (-\vec{k})$$

$$\vec{B}_M = \vec{0} + \frac{\mu_0 I \sqrt{2}}{8\pi a} \vec{k} - \frac{\mu_0 I (2 - \sqrt{2})}{8\pi a} \vec{k}$$

$$\vec{B}_M = \frac{\mu_0 I}{4\pi a} (\sqrt{2} - 1) \vec{k}$$

4

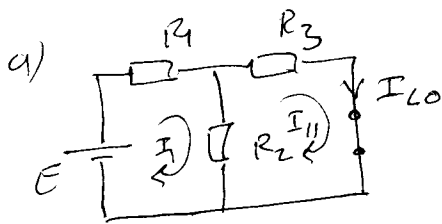

$$(R_1 + R_2) I_1 - R_2 I_{11} = E$$


$$-R_2 I_1 + (R_2 + R_3) I_{11} = 0$$

$$3 I_1 - 2 I_{11} = 12$$

$$-2 I_1 + 4 I_{11} = 0 \Rightarrow I_1 = 2 I_{11}$$

$$\Rightarrow \begin{cases} 6 I_{11} - 2 I_{11} = 12 \\ I_{11} = 3 \text{ A} \end{cases}$$
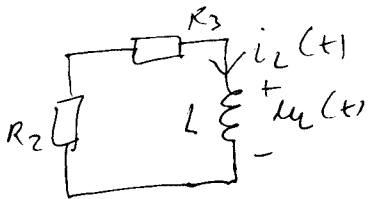
$$\boxed{I_{20} = I_{11} = 3 \text{ A}}$$



$$(R_2 + R_3) i_L + u_L = 0$$

$$(R_2 + R_3) i_L + L \frac{di_L}{dt} = 0 \quad | : L$$

$$\boxed{\frac{di_L}{dt} + \left( \frac{R_2 + R_3}{L} \right) i_L = 0}$$

$$\alpha = \frac{R_2 + R_3}{L} = 10^6 \frac{1}{s}$$


$$\boxed{\tau = \frac{1}{\alpha} = \frac{L}{R_2 + R_3} = 1 \mu s}$$

$$i_L(t) = A e^{-\frac{t}{\tau}} + B$$

$$B = 0$$

$$I_{20} = A + B \Rightarrow A = I_{20}$$

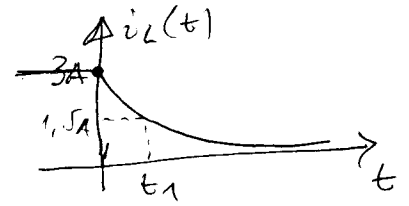
$$\Rightarrow \begin{cases} i_L(t) = I_{20} e^{-\frac{t}{\tau}} \\ i_L(t_1) = 3 e^{-\frac{t_1}{1 \mu s}} \text{ A} \end{cases}$$



$$u_L(t) = L \frac{di_L}{dt} = L \cdot I_{20} \cdot \left(-\frac{1}{\tau}\right) e^{-t/\tau}$$

$$u_L(t) = -I_{20} \cdot \frac{R_2 + R_3}{L} e^{-t/\tau} = -(R_2 + R_3) I_{20} e^{-t/\tau}$$

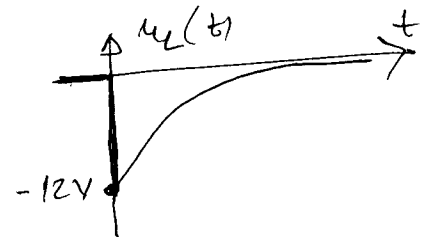
$$\boxed{u_L(t) = -12 e^{-\frac{t}{1 \mu s}} \text{ V}}$$



b)

$$\left. \begin{aligned} i_L(t_1) &= 0,5 \cdot I_{20} \\ i_L(t_1) &= I_{20} e^{-t_1/\tau} \end{aligned} \right\} \Rightarrow e^{-t_1/\tau} = 0,5$$
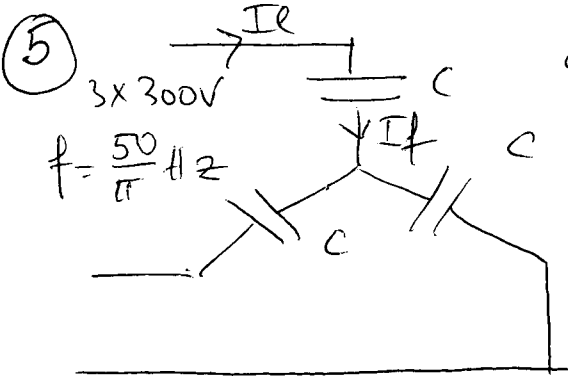
$$t_1 = -\tau \ln(0,5) = \tau \ln(2) = 0,69 \mu s$$



a)  $C = 0,1 \mu F$

$$Z_f = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \cdot \frac{50}{\pi} \cdot 0,1 \cdot 10^{-6}} = \frac{10^4}{2} = 100 \Omega$$

$Z_f = 100 \Omega$

$$U_l = 300V$$

$$U_f = \frac{U_l}{\sqrt{3}} = \frac{300}{\sqrt{3}} = 100\sqrt{3} V$$

$$I_l = I_f = \frac{U_f}{Z_f} = \sqrt{3} A$$

b)  $S = 3U_f I_f = 3 \cdot 100\sqrt{3} \cdot \sqrt{3} = 900 VA = S$

$P = 0 \Rightarrow Q = -900 VAR$

c)  $\cos \varphi = \frac{P}{S} = 0$