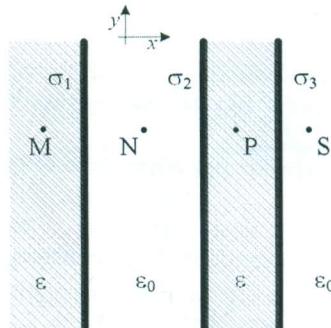


Elektrotehnika


15. jun 2023.

1. Na Slici 1 prikazane su tri paralelne, veoma velike, ravnomerno nanelektrisane površi, površinskih gustina nanelektsanja $\sigma_1 = \sigma > 0$, $\sigma_2 = -\sigma$ i $\sigma_3 = -\sigma/2$. Odrediti i skicirati vektore električnog polja u tačkama M, N, P i S. Poznato je: $\epsilon = 4 \cdot \epsilon_0$. (20 poena)

- MODIFIKOVAN ZADATAK III-3 i 2 ZBIRKE
i ZADATAK SA VEZBI



Slika 1

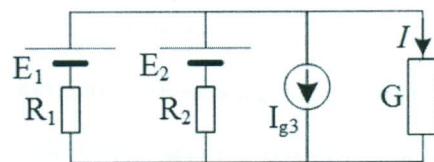


Slika 2


2. U kolu na Slici 2 poznato je: $R_1 = 10 \Omega$, $R_2 = 5 \Omega$, $E_1 = 50 \text{ V}$, $E_2 = 20 \text{ V}$, $I_{g3} = 3 \text{ A}$, $G = 0.2 \text{ S}$. Odrediti struju I primenom Tevenenove teoreme. (20 poena)

3. Na Slici 3 je prikazano magnetno kolo, koje je sačinjeno od jezgra relativne permeabilnosti μ_r . Jezgro se sastoji iz dva dela koji imaju površine poprečnih preseka S_1 i S_2 i čije su dužine srednjih linija l_1 i l_2 . Na jezgru su namotana dva namotaja sa N_1 i N_2 navojaka, kroz koje protiču struje intenziteta I_1 i I_2 . Odrediti magnetni fluks u jezgru, gustinu energije magnetnog polja u delu jezgra dužine l_1 i međusobnu induktivnost namotaja. (20 poena)

ZADATAK III-13 12 ZBIRKE
+ MEĐUSOBNA INDUKTIVNOST

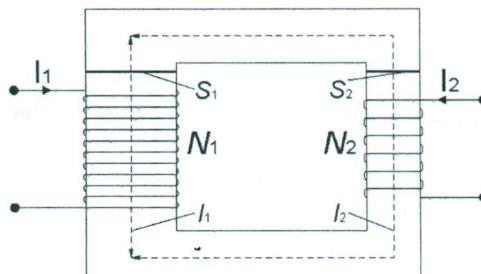

Slika 3

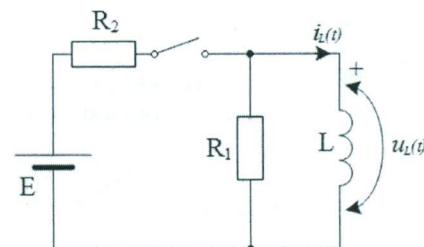

Slika 4

4. U kolu na Slici 4, poznate su vrednosti elemenata: E , $R_1 = R$, $R_2 = 2R$, L . Prekidač je zatvoren i u kolu je uspostavljeno stacionarno stanje. U trenutku $t = 0$, prekidač se otvara.


- a) Odrediti izraze za struju i napon kalema nakon otvaranja prekidača i nacrtati odgovarajuće vremenske dijagrame. (15 poena)
- b) Odrediti trenutak t_1 u kome struja kalema dostiže 25% svoje maksimalne vrednosti. (5 poena)

5. U kolu naizmenične struje (Slika 5), potrošač kompleksne impedanse $\bar{Z} = (1+j)\Omega$ priključen je na naponski izvor poznatih parametara $U_m = 200 \text{ V}$, $\omega = 100 \text{ rad/s}$.

- a) Odrediti kapacitivnost kondenzatora koji je potrebno priključiti paralelno potrošaču da bi se faktor snage popravio na vrednost $\cos \varphi = 1$.



(10 poena) MODIFIKOVAN ZADATAK V-14 12 ZBIRKE

- b) Nacrtati fazorski dijagram za sve električne veličine označene na slici, u situaciji nakon priključenja kondenzatora. (10 poena)

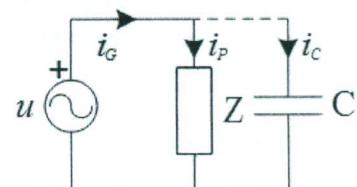

Slika 5

①

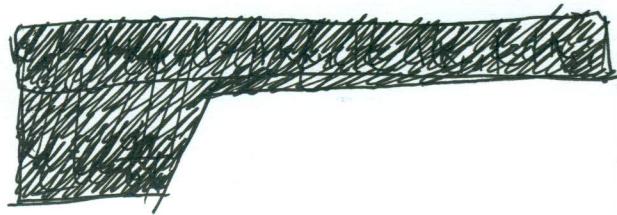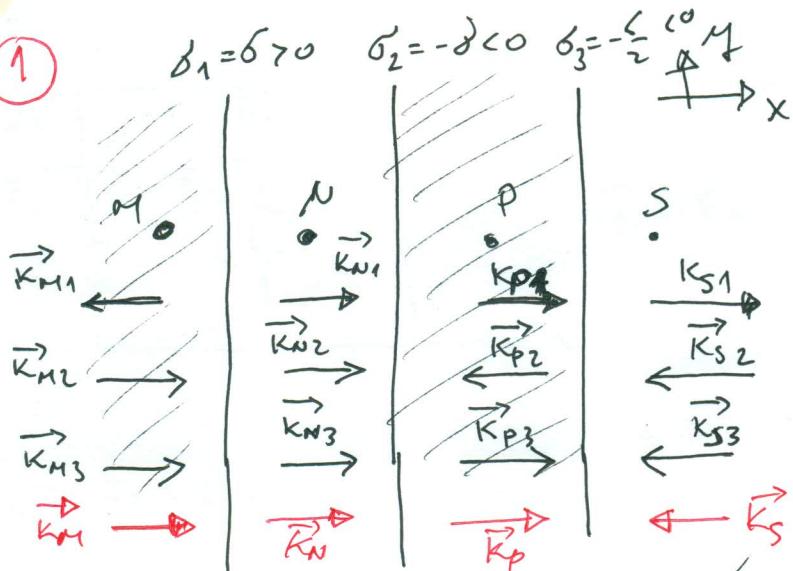

$$\vec{K}_M = \vec{K}_{M1} + \vec{K}_{M2} + \vec{K}_{M3} = \frac{\delta_{70}}{2\varepsilon} (-\vec{i}) + \frac{\delta_{10}}{2\varepsilon} \vec{i} + \frac{\delta/2}{2\varepsilon} \vec{i} = \frac{\delta}{4\varepsilon} \vec{i}$$



$$\boxed{\vec{k}_M = \frac{\delta}{16\varepsilon_0} \vec{i}}$$

$$\boxed{\vec{K}_N = \vec{K}_{N1} + \vec{K}_{N2} + \vec{K}_{N3} = \frac{\delta}{2\varepsilon} \vec{i} + \frac{\delta}{2\varepsilon_0} \vec{i} + \frac{\delta}{4\varepsilon_0} \vec{i} = \frac{5\delta}{4\varepsilon_0} \vec{i} = \vec{k}_N}$$


$$\boxed{\vec{k}_P = \vec{k}_{P1} + \vec{k}_{P2} + \vec{k}_{P3} = \cancel{\frac{\delta}{2\varepsilon} \vec{i}} - \cancel{\frac{\delta}{2\varepsilon} \vec{i}} + \frac{\delta}{4\varepsilon} \vec{i} = \frac{\delta}{16\varepsilon_0} \vec{i} = \vec{k}_P}$$

$$\vec{k}_S = \vec{k}_{S1} + \vec{k}_{S2} + \vec{k}_{S3} = \cancel{\frac{\delta}{2\varepsilon} \vec{i}} - \cancel{\frac{\delta}{2\varepsilon_0} \vec{i}} - \cancel{\frac{\delta}{4\varepsilon_0} \vec{i}} = -\frac{\delta}{4\varepsilon_0} \vec{i} = \vec{k}_S$$


②

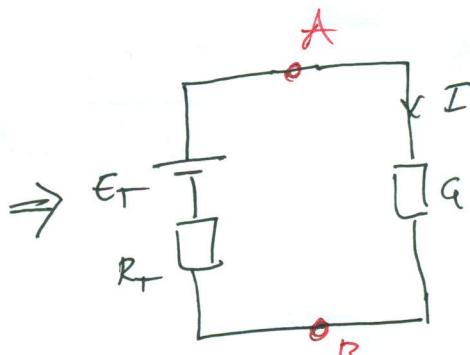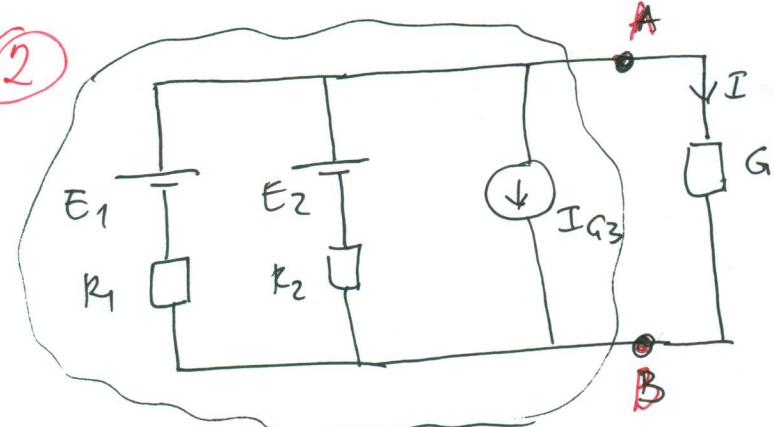

$$I = \frac{E_T}{R_T + \frac{1}{G}}$$

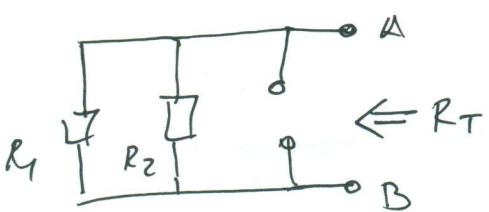
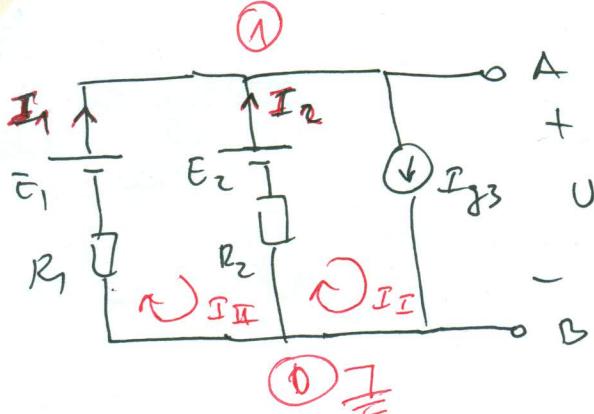
$$R_T = R_1 + R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 \cdot 5}{10 + 5} = \frac{10}{3} \Omega$$



(II) NAEIN

$$I_1 + I_2 = I_{j3} \Rightarrow I_2 = \frac{I_{j3}}{j} - I_1$$

$$E_1 - E_2 + R_2 I_2 - R_1 I_1 = 0$$

$$E_1 - E_2 + R_2 (I_{j3} - I_1) - R_1 I_1 = 0$$

$$E_1 - E_2 + R_2 I_{j3} - (R_1 + R_2) I_1 = 0$$

$$I_1 = \frac{E_1 - E_2 + R_2 I_{j3}}{R_1 + R_2} = \frac{45}{15} = 3A$$

$$E_T = U_{AB}^{OV} = E_1 - R_1 I_1 = 20V$$

(II) NAEIN

$$I_2 = I_{j3}$$

$$-R_2 I_2 + (R_1 + R_2) I_{j3} = E_1 - E_2$$

$$I_1 = I_{j3} = \frac{E_1 - E_2 + R_2 I_{j3}}{R_1 + R_2} = 3A$$

$$E_T = U_{AB}^{OV} = E_1 - R_1 I_1 = 20V$$

$$I = \frac{E_T}{R_1 + \frac{1}{G}} = \frac{20}{\frac{10}{3} + 5} = \frac{60}{10 + 15}$$


$$I = \frac{60}{25} = \frac{12}{5} = 2,4A$$

(III) NAEIN

$$\left(\frac{1}{R_1} + \frac{1}{R_2} \right) U_{10} = \frac{E_1}{R_1} + \frac{E_2}{R_2} - I_{j3}$$

$$E_T = U_{AB}^{OV} = U_{10} = \frac{\frac{E_1}{R_1} + \frac{E_2}{R_2} - I_{j3}}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{5+4-3}{0,1+0,2}$$

$$E_T = \frac{60}{3} = 20V$$

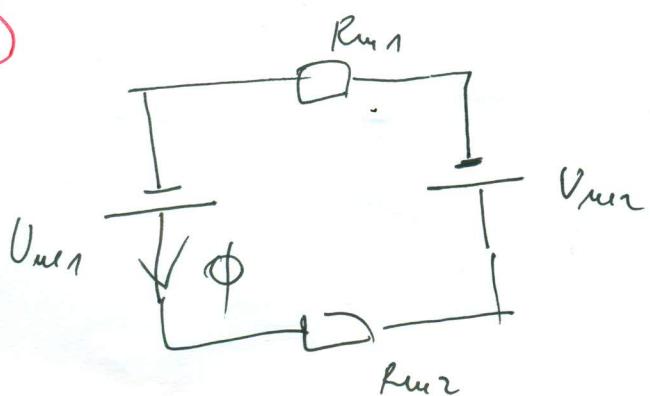

$$U_{mn1} = N_1 I_1$$

$$U_{mn2} = N_2 I_2$$

$$R_{mn1} = \frac{l_1}{\mu_0 \mu_r S_1} \quad R_{mn2} = \frac{l_2}{\mu_0 \mu_r S_2}$$

$$\Phi = \frac{U_{mn1} - U_{mn2}}{R_{mn1} + R_{mn2}} = \frac{N_1 I_1 - N_2 I_2}{\frac{l_1}{\mu_0 \mu_r S_1} + \frac{l_2}{\mu_0 \mu_r S_2}}$$

$$W_m = \frac{1}{2} B_1 H_1 = \frac{1}{2} B_1 \frac{B_1}{\mu_0 \mu_r} = \frac{B_1^2}{2 \mu_0 \mu_r}$$

$$W_{M1} = \frac{(\Phi/S_1)^2}{2 \mu_0 \mu_r} = \frac{\Phi^2}{2 \mu_0 \mu_r S_1^2}$$


$$= \frac{(N_1 I_1 - N_2 I_2)^2}{2 \mu_0 \mu_r S_1^2 \left(\frac{l_1}{S_1} + \frac{l_2}{S_2} \right)^2}$$

$$w_{M1} = \frac{\mu_0 \mu_r (N_1 I_1 - N_2 I_2)^2}{2 \left(l_1 + \frac{l_2 S_1}{S_2} \right)^2}$$

$$h_{12} = h_{21} = -\frac{N_1 N_2}{R_{mn1} + R_{mn2}} = \frac{-\mu_0 \mu_r k_1 N_2}{\frac{l_1}{S_1} + \frac{l_2}{S_2}}$$


(4)

a)

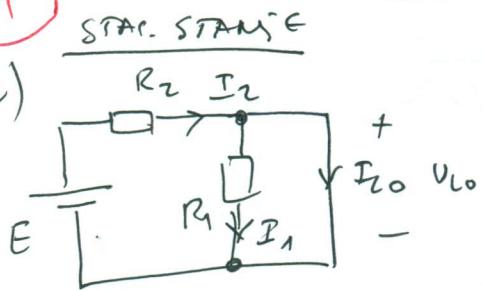

$$v_{L0} = 0 \Rightarrow I_1 = \frac{v_{L0}}{R_1} = 0 \Rightarrow I_2 = I_{L0}$$

$$I_{L0} = \frac{E}{R_2} = \frac{E}{2R}$$

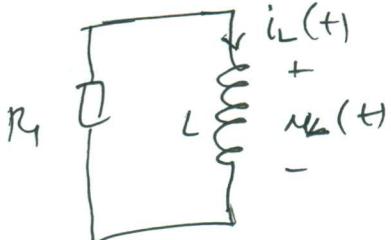PRZ. PROZES

$$R_1 i_L(t) + u_L(t) = 0$$

$$u_L(t) = L \frac{di_L(t)}{dt}$$

$$R_1 i_L + L \frac{di_L}{dt} = 0 \Rightarrow \frac{d i_L}{dt} + \left(\frac{R_1}{L} \right) i_L = 0$$

$$i_L(t) = A e^{-t/\tau} + B$$

$$B = kT = 0$$

$$A = i_L(0) - B = I_{L0} = \frac{E}{2R}$$



$$i_L(t) = \frac{E}{2R} e^{-\frac{R}{L} t}$$

$$u_L(t) = L \frac{di_L}{dt} = L \frac{E}{2R} \left(-\frac{R}{L} \right) e^{-\frac{R}{L} t}$$

$$u_L(t) = -\frac{E}{2} e^{-\frac{R}{L} t} + C$$

$$\alpha = \frac{R_1}{L} = \frac{R}{L} \quad k = 0$$
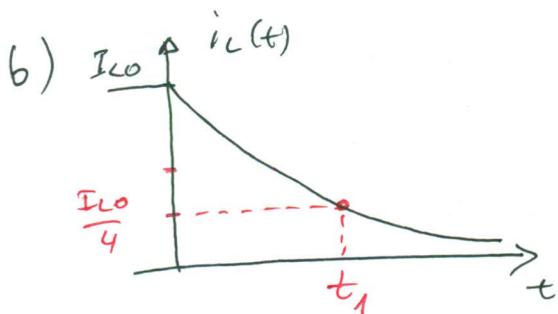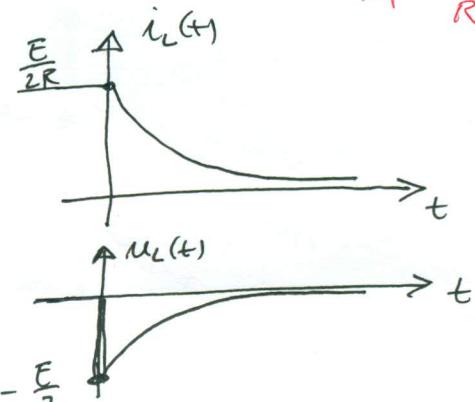
$$\tau = \frac{1}{\alpha} = \frac{L}{R_1} = \frac{L}{R}$$



$$i_L(t_1) = I_{L0} e^{-\frac{R}{L} t_1} = 25\% \cdot I_{L0}$$

$$e^{-\frac{R}{L} t_1} = \frac{1}{4} \quad | \ln(\cdot)$$

$$-\frac{R}{L} t_1 = \ln \frac{1}{4}$$

$$t_1 = \frac{L}{R} \ln 4$$

5

$$\bar{Z} = 1 + j \cdot 2$$

$$U_M = 200 \text{ V}$$

$$\omega = 100 \text{ rad/s}$$

$$b) \bar{U} = U e^{j\theta}, U = \frac{U_M}{\sqrt{2}}, \theta = 0$$

$$\boxed{\bar{U} = 100\sqrt{2} \text{ V}}$$

$$\bar{I}_G = \frac{\bar{U}}{\bar{Z}_{ew}} = \bar{U} Y_{ew} = \frac{100\sqrt{2}}{2}$$

$$\boxed{\bar{I}_G = 50\sqrt{2} \text{ A}}$$

$$a) \bar{Y} = \frac{1}{\bar{Z}} = \frac{1}{1+j} \cdot \frac{1-j}{1-j} = \frac{1}{2} - j \frac{1}{2} S$$

$$\bar{Y}_C = j\omega C$$

$$\bar{Y}_{ew} = \bar{Y} + \bar{Y}_C = \frac{1}{2} + j(\omega C - \frac{1}{2})$$

$$\bar{Y}_{ew} = Y_{ew} e^{-j\varphi} = Y_{ew} (\underbrace{\cos \varphi}_1 - j \underbrace{\sin \varphi}_0)$$

$$\Rightarrow \boxed{C = \frac{1}{2\omega} = \frac{1}{200} = 5 \mu F}$$

$$\bar{I}_P = \frac{\bar{U}}{\bar{Z}_p} = \bar{U} \bar{Y} = 100\sqrt{2} \left(\frac{1}{2} - j \frac{1}{2} \right) = \boxed{50\sqrt{2} - j50\sqrt{2} = \bar{I}_P}$$


$$\bar{I}_C = \frac{\bar{U}}{\bar{Z}_C} = \bar{U} \bar{Y}_C = \bar{U} j\omega C = j \frac{100\sqrt{2}}{2} = \boxed{j50\sqrt{2} = \bar{I}_C}$$

Provera:

$$\bar{I}_G = \bar{I}_P + \bar{I}_C$$

$$50\sqrt{2} = 50\sqrt{2} - j50\sqrt{2} + j50\sqrt{2}$$

on

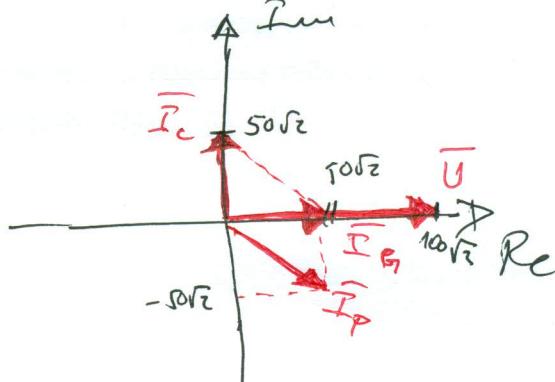

a) II način (snage)

$$\bar{S} = \frac{|\bar{U}|^2}{\bar{Z}^*} = |\bar{U}|^2 = (100\sqrt{2})^2 \left(\frac{1}{2} + j \frac{1}{2} \right) = (10k + j10k) VA \Rightarrow P = 10kW$$

$$Q = 10kVAR$$

$$\bar{S}_{ew} = P_{ew} + j Q_{ew}$$

$$P_{ew} = P = 10kW$$

$$\cos \varphi = 1 \Rightarrow Q_{ew} = 0 \Rightarrow Q_{ew} = Q + Q_C = 0$$

$$Q_C = -Q$$

$$Q_C = -U^2 \omega C = -Q$$

$$C = \frac{Q}{\omega U^2} = \frac{\frac{1}{2} U^2}{\omega U^2} = \frac{1}{2\omega} = \frac{1}{200} = 5 \mu F$$