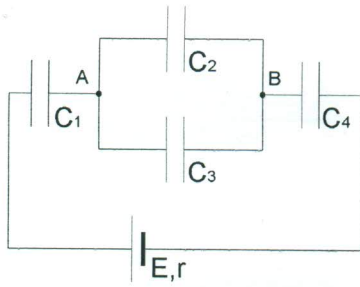


Elektrotehnika


31. avgust 2023.

1. U kolu na Slici 1 odrediti napon U_{AB} i elektrostatičku energiju kondenzatora C_1 i C_2 . Parametri elemenata su: $E = 30V$, $C_1 = 20nF$, $C_2 = 10nF$, $C_3 = 10nF$, $C_4 = 20nF$. Pre povezivanja u kolo, kondenzatori su bili neopterećeni. (20 poena)

REŠENJE ZAD I.5. IZ ZBIRKE




Slika 1

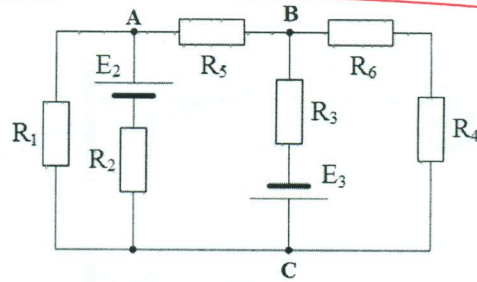

Slika 2

2. Poznate su sve otpornosti i ems u kolu prikazanom na Slici 2: $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 5\Omega$, $E_2 = 20V$, $E_3 = 40V$. Rešiti kolo primenom metode napona između čvorova, a nakon toga odrediti struju kroz otpornik R_5 i snagu generatora E_3 . (20 poena)

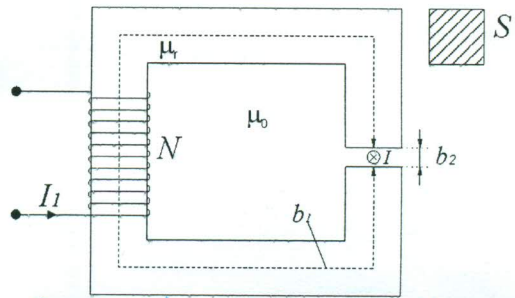3. Na pravougaonom jezgru od feromagnetnog materijala, relativne magnetne permeabilnosti $\mu_r = 1000$, sa vazдушnim procepom širine $b_2 = 2mm$, ravnomerno je namotano $N = 20000$ navojaka, tako da nema magnetnog rasipanja (Slika 3). Dužina srednje linije magnetnog jezgra je $b_1 = 20cm$, a površina kvadratnog poprečnog preseka jezgra iznosi $S = 9cm^2$. Mehanička sila koja deluje na tanak pravolinijski provodnik, postavljen paralelno gornjoj i donjoj ivici proreza, kroz koji protiče struja intenziteta $I = 1A$, iznosi $F = 3 \cdot 10^{-2}N$. Izračunati struju I_1 u navojcima. (20 poena)




REŠENJE ZADATAK III.12
Slika 3 IZ ZBIRKE


4. U kolu na Slici 4, poznate su vrednosti elemenata: E , $R_1 = R$, $R_2 = 2R$, L . Prekidač Π je otvoren i u kolu je uspostavljeno stacionarno stanje. U trenutku $t = 0$, prekidač se zatvara.

a) Odrediti izraze za struju i napon kalema nakon zatvaranja prekidača i nacrtati odgovarajuće vremenske dijagrame. (15 poena)

b) Odrediti trenutak t_1 u kome energija kalema dostiže 25% svoje maksimalne vrednosti. (5 poena)

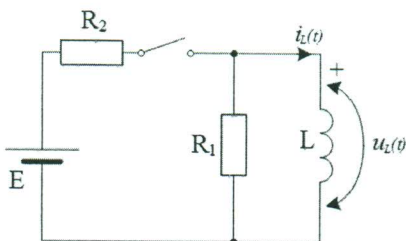

Slika 4

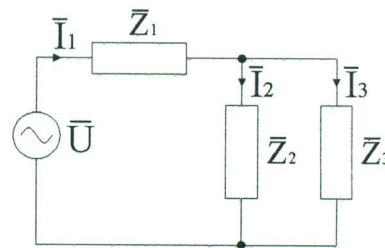

Slika 5

5. Na Slici 5 je prikazano kolo naizmenične struje koje čine naponski generator efektivne vrednosti napona $U = 50V$ i tri potrošača impedansi $Z_1 = (1 - 2j)\Omega$, $Z_2 = (1 - j)\Omega$ i $Z_3 = (1 + 3j)\Omega$. Odrediti:


a) kompleksne izraze za struje u svim granama kola; (8 poena)

b) efektivnu vrednost napona na potrošaču Z_1 ; (6 poena)

c) aktivnu snagu potrošača Z_2 i kompleksnu prividnu snagu potrošača Z_3 . (8 poena)

REŠENJE ZADATAK V.6 IZ ZBIRKE

②

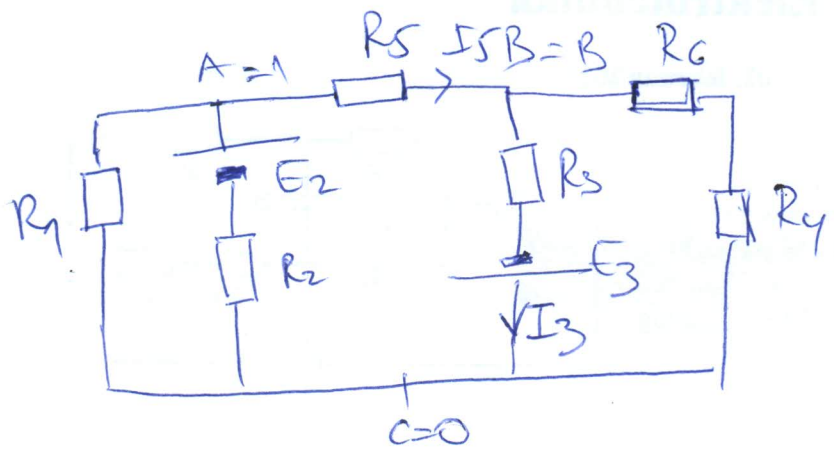

$E_2 = 20\text{V}$
 $E_3 = 40\text{V}$
 $R_1 = R_2 = R_5 = R_3 = R_4 = R_6 = 5\Omega$

1. $U_{10} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5} \right) - U_{20} \frac{1}{R_5} = \frac{E_2}{R_2}$
 2. $-U_{10} \frac{1}{R_5} + \left(\frac{1}{R_5} + \frac{1}{R_3} + \frac{1}{R_4 + R_6} \right) U_{20} = \frac{-E_3}{R_3}$

$$\frac{3U_{10}}{R} - \frac{U_{20}}{R} = \frac{E_2}{R}$$

$$- \frac{U_{10}}{R} + U_{20} \left(\frac{1}{R} + \frac{1}{R} + \frac{1}{2R} \right) = \frac{-E_3}{R}$$

$$3U_{10} - U_{20} = E_2 \Rightarrow U_{20} = 3U_{10} - E_2$$

$$-U_{10} + \frac{5}{2}U_{20} = -E_3$$

$$U_{20} = 3U_{10} - E_2$$

$$-U_{10} + \frac{15}{2}U_{10} - \frac{5}{2}E_2 = -E_3 \Rightarrow \frac{13}{2}U_{10} = \frac{5}{2}E_2 - E_3$$

$$U_{10} = \frac{2}{13} \left(\frac{5}{2}E_2 - E_3 \right) = \frac{2}{13} \left(\frac{5}{2} \cdot 20 - 40 \right) = \frac{2}{13} (50 - 40) = \frac{20}{13} \text{V}$$

$$U_{20} = 3U_{10} - E_2 = \frac{60}{13} - 20 = \frac{60}{13} - \frac{260}{13} = \frac{-200}{13} \text{V}$$

$$U_{AB} = U_{10} - U_{20} = \frac{20}{13} + \frac{200}{13} = \frac{220}{13} \text{V}$$


$$I_5 = \frac{U_{AB}}{R_5} = \frac{220}{13 \cdot 5} = \frac{440}{130} = \frac{44}{13} \text{A}$$

$$U_{20} = R_3 I_3 - E_3 \Rightarrow I_3 = \frac{U_{20} + E_3}{R_3} = \frac{\frac{-200}{13} + 40}{5} = \frac{-\frac{40}{13} + 8}{1} = \frac{44}{13} \text{A}$$

$$P_{E_3} = E_3 I_3 = \frac{44}{13} \cdot 40 = \frac{2560}{13} \text{W}$$

4



a)

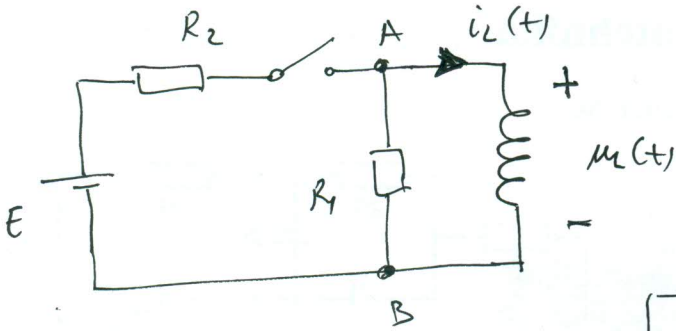

STAC. STAMME:

$$i_L(0) = I_{L0} = 0A$$

PREL. PROCES:

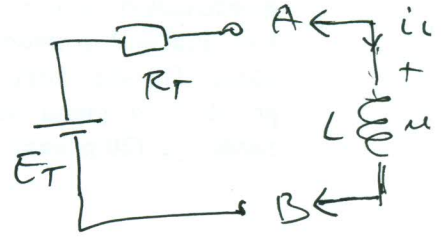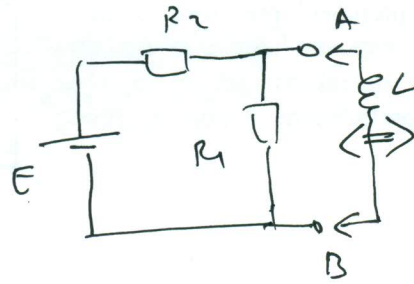

$$E_T = \frac{R_1}{R_1 + R_2} E = \frac{RE}{3R}$$

$$E_T = E/3$$

$$R_T = R_1 || R_2 = \frac{R \cdot 2R}{3R}$$

$$R_T = \frac{2}{3} R$$

$$-E_T + R_T i_L + u_L = 0$$

$$R_T i_L + L \frac{di_L}{dt} = E_T$$

$$\frac{di_L}{dt} + \frac{R_T}{L} i_L = \frac{E_T}{L}$$

$$\frac{di_L}{dt} + \left(\frac{2R}{3L}\right) i_L = \left(\frac{E}{3L}\right) \quad \tau = \frac{3L}{2R}$$

$$i_L(t) = A e^{-t/\tau} + B, \quad B = \tau \cdot \frac{E_T}{L} = \frac{E}{3L} \cdot \left(\frac{3L}{2R}\right) = \frac{E}{2R} = B$$

$$I_{L0} = A + B \Rightarrow A = -B = -\frac{E}{2R}$$

$$i_L(t) = -\frac{E}{2R} e^{-\frac{2R}{3L}t} + \frac{E}{2R}$$

$$u_L(t) = L \frac{di_L}{dt} = -\frac{E}{2R} \cdot \left(-\frac{2R}{3L}\right) e^{-\frac{2R}{3L}t} = \frac{E}{3} e^{-\frac{2R}{3L}t} = u_L(t)$$

b) $W_L(t) = \frac{1}{2} L i_L^2(t) = \frac{LE^2}{8R^2} \left(1 - e^{-\frac{2R}{3L}t}\right)^2$

$$W_{Lmax} = \frac{LE^2}{8R^2}$$

$$\frac{LE^2}{8R^2} \left(1 - e^{-\frac{2R}{3L}t_1}\right)^2 = \frac{1}{4} \frac{LE^2}{8R^2} \quad \sqrt{(\cdot)}$$

$$1 - e^{-\frac{2R}{3L}t_1} = \frac{1}{2}$$

$$e^{-\frac{2R}{3L}t_1} = \frac{1}{2} \quad \ln(\cdot)$$

$$-\frac{2R}{3L}t_1 = -\ln(2)$$

$$t_1 = \frac{3L}{2R} \ln(2)$$

