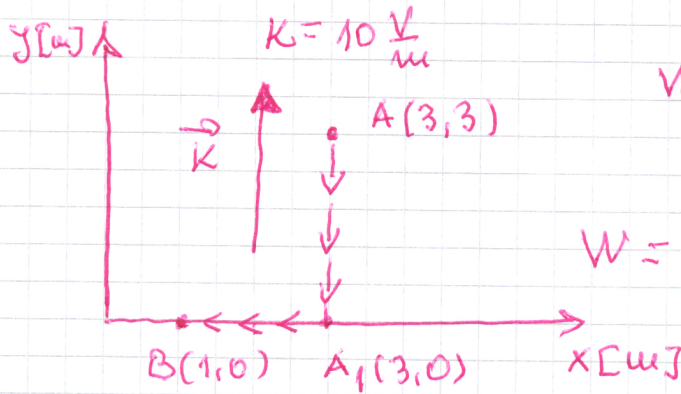


GRUPA 1

1



$$W = \Delta Q \left(k \cdot |A_1 B| \cos \pi + k(A_1 B) \cdot \cos \frac{\pi}{2} \right)$$



$$W = \Delta Q \cdot k(3) \cdot (-1) = 10 \cdot 10^{-6} \cdot 10 \cdot 3(-1) = -3 \cdot 10^{-4} \text{ J}$$

$$W = -3 \cdot 10^{-4} \text{ J}$$

Кег уздура угундге керүүлөгө ю түбүсү

$$\varphi(k, \vec{e}) = \begin{cases} 0 \\ \pi \\ \pi/2 \end{cases}$$

2

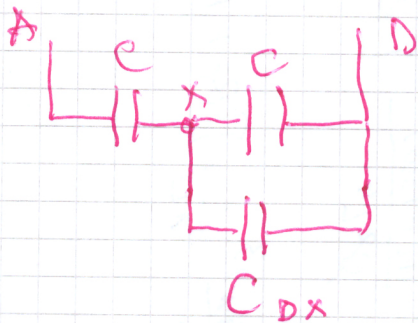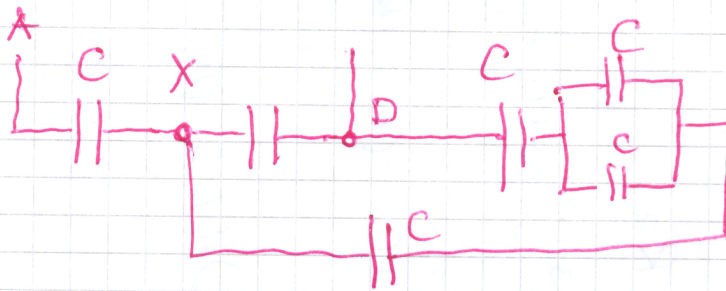

$$\frac{1}{C_{DX}} = \frac{1}{C} + \frac{1}{2C} + \frac{1}{C} = \frac{5}{2C}$$

$$C_{DX} = \frac{2C}{5}$$


$$C + C_{DX} = C + \frac{2C}{5} = \frac{7C}{5}$$

$$\frac{1}{C_{AD}} = \frac{1}{C} + \frac{1}{C + C_{DX}}$$

$$\frac{1}{C_{AD}} = \frac{1}{C} + \frac{5}{7C} = \frac{12}{7C}$$

$$C_{AD} = \frac{7C}{12}$$

3

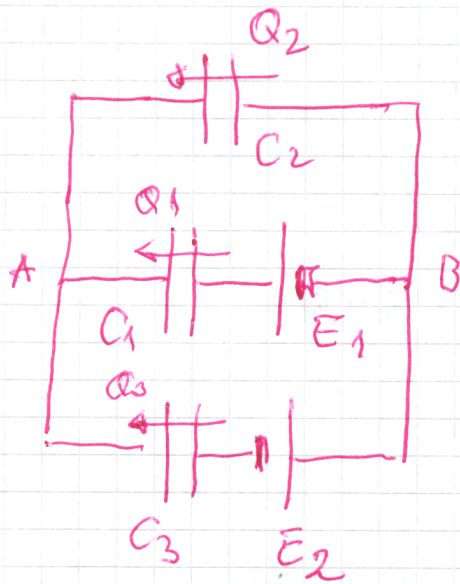



$$U_{BA} = \frac{Q_2}{C_2} = \frac{Q_1}{C_1} - E_1 = \frac{Q_3}{C_3} + E_2$$

$$Q_2 = C_2 \left[\frac{Q_1}{C_1} - E_1 \right]$$

$$Q_3 = C_3 \left[\frac{Q_1}{C_1} - E_1 - E_2 \right]$$

4


КОРО УКАЗ 3 ЧИОПА

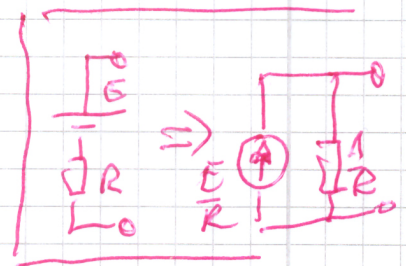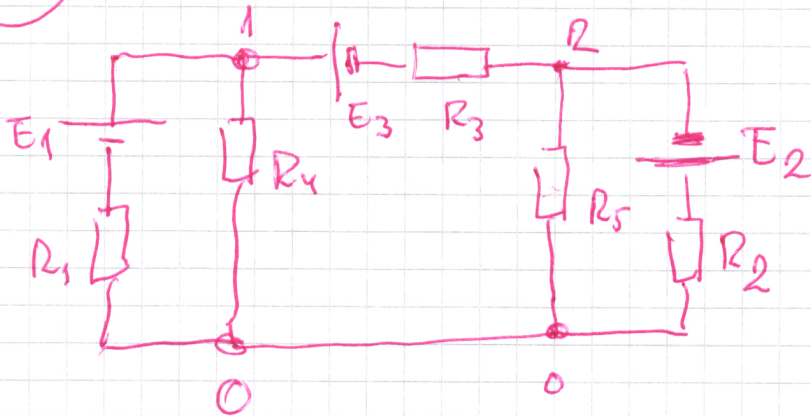

$$\left(\frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_3} \right) U_{10} - \frac{1}{R_3} U_{20} = \frac{E_1}{R_1} + \frac{E_3}{R_3}$$

$$- \frac{1}{R_3} U_{10} + \left(\frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_5} \right) U_{20} = - \frac{E_3}{R_3} - \frac{E_2}{R_2}$$

5

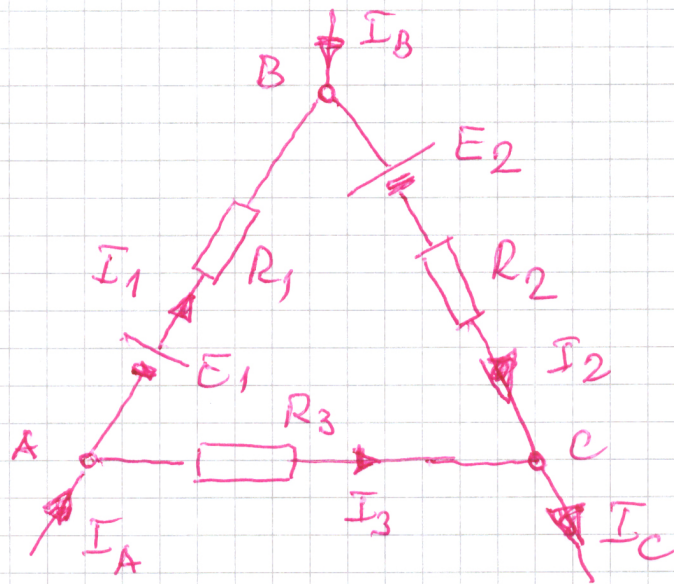

$$I_A = 5A$$

$$I_1 = 2A$$

$$R_3 = 2A$$

$$R_1 = 3\Omega$$

$$I_A - I_1 - I_3 = 0 \quad I_3 = I_A - I_1 = 3A$$

$$U_{AC} = R_3 I_3 = 2 \cdot 3 = 6V$$

$$U_{AC} = -E_1 + R_1 I_1 + E_2 + R_2 I_2$$

$$\frac{U_{AC} + E_1 - E_2 - R_1 I_1}{R_2} = I_2$$

$$I_2 = \frac{6 + 4 - 6 - 3 \cdot 2}{1} = -2A$$

$$I_C = I_3 + I_2 = 3 - 2 = 1A$$

$$I_B + I_1 - I_2 = 0 \quad I_B = I_2 - I_1 = -2 - 2 = -4A$$

ПРОБЕРА


$$I_A + I_B - I_C = 0$$

$$5 - 4 - 1 = 0$$

Prvi kolokvijum GRUPA 2


Ime Prezime br.indeksa

1. U ravni pravougaonog koordinatnog sistema postoji homogeno elektrostatičko polje intenziteta $K = 10 \frac{V}{m}$, prikazano ravnomerno raspoređenim orijentisanim linijama paralelnim osi y , slika (1). Izračunati rad sila elektrostatičkog polja koji je potreban da se naelektrisanje $\Delta Q = 10 \mu C$ prenese iz tačke A u tačku B

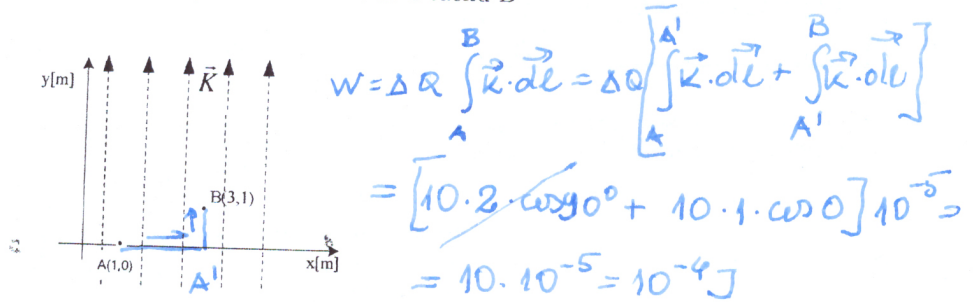


Slika 1

2. Grupa od šest kondenzatora poznatog kapaciteta C vezana je kao na slici (2). Odrediti ekvivalentni kapacitet između tačaka B i D

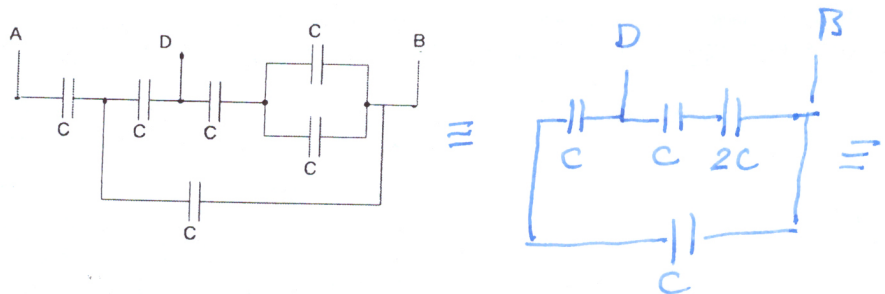

Slika 2

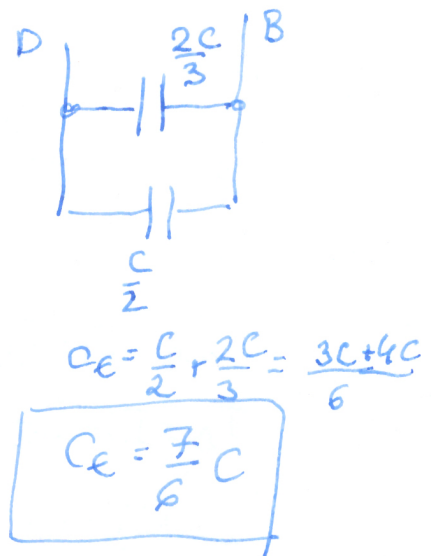


3. U kolu na slici (3) poznate su vrednosti E_1, E_2, C_1, C_2, C_3 . Ako je kondenzator C_3 opterećen sa količinom naelektrisanja Q_3 u naznačenom smeru. Izračunati Q_1 i Q_2 .

$$E_2 + \frac{Q_3}{C_3} = \frac{Q_1}{C_1} - E_1$$

$$\frac{Q_1}{C_1} = E_1 + E_2 + \frac{Q_3}{C_3}$$

$$Q_1 = C_1(E_1 + E_2) + \frac{C_1}{C_3} Q_3$$

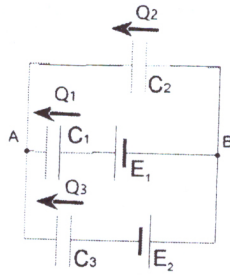


Slika 3

$$\frac{Q_2}{C_2} = E_2 + \frac{Q_3}{C_3}$$

$$Q_2 = C_2 E_2 + \frac{C_2}{C_3} Q_3$$

$$\frac{Q_2}{C_2} = \frac{Q_1}{C_1} - E_1$$

4. Za električno kolo slici (4) postaviti odgovarajući sistem jedančina po metodi napona između čvorova. Sve vrednosti otpornosti otpornika i elektromotornih sila su poznate

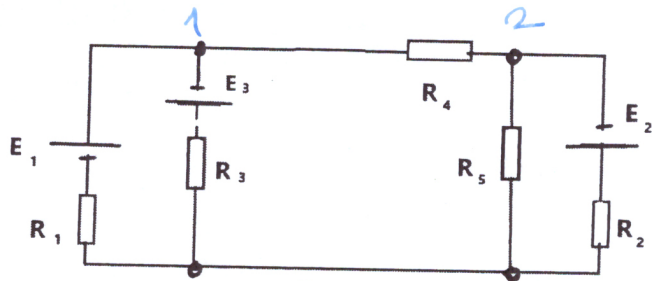

Slika 4

$$\sum I_y = -\frac{E_2}{R_2}$$

$$\sum I_y = \frac{E_1}{R_1} - \frac{E_3}{R_3}$$

$$G_{11}U_{10} - G_{12}U_{20} = \sum I_k$$


$$-G_{21}U_{10} + G_{22}U_{20} = \sum I_k$$

$$G_{11} = \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4}\right)$$

$$G_{12} = \frac{1}{R_4}$$

$$G_{22} = \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_2}$$

5. U delu složenog električnog kola prikazanog na slici (5) poznate su vrednosti elektromotornih sila $E_1 = 4V$ i $E_2 = 6V$, otpornosti otpornika $R_1 = 3\Omega, R_2 = 1\Omega$ i $R_3 = 2\Omega$ kao i struje $I_C = 1A$ i $I_2 = 2A$. Odrediti struje I_A i I_B .

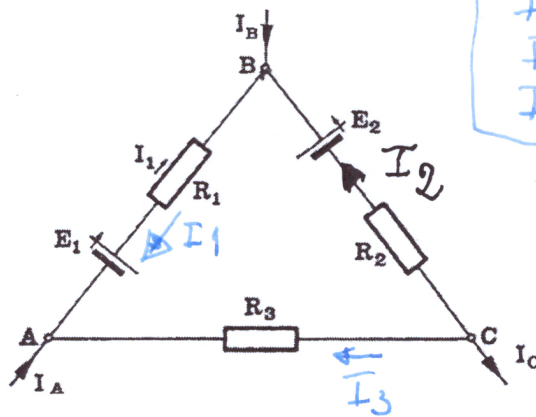

Slika 5

$$I_B = -4A$$

$$I_C = 1A$$

$$I_A = 5A$$

$$I_3 = -I_C - I_2 = -3A$$

$$U_{CA} = I_3 R_3 = -3 \cdot 2 = -6V$$

$$I_3 + I_C + I_2 = 0$$

$$I_3 = -I_C - I_2 = -3A$$

$$I_B - I_1 + I_2 = 0$$

$$I_B = I_1 - I_2 = -2 - 2 = -4A$$

$$I_A + I_3 + I_1 = 0$$

$$I_A = -I_3 - I_1 = 3 + 2 = 5A$$

$$-2 + I_A - 3 = 0$$

$$U_{CA} = R_2 I_2 - E_2 + R_1 I_1 + E_1$$

$$U_{CA} - R_2 I_2 + E_2 - E_1 = R_1 I_1$$

$$-6 - 1 \cdot 2 + 6 - 4 = R_1 I_1$$

$$-6 = R_1 I_1 \quad I_1 = -2A$$

$$I_1 = -2A$$

$$I_A = 5$$