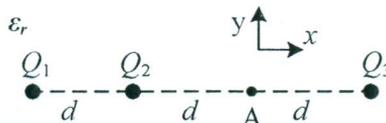


# Elektrotehnika

12. septembar 2024.


1. Na Slici 1 su prikazana tri tačkasta naelektrisanja  $Q_1=Q$ ,  $Q_2=-2Q$  i  $Q_3=-3Q$  ( $Q > 0$ ) koja se nalaze u dielektriku relativne dielektrične konstante  $\epsilon_r$ .

- Odrediti i nacrtati vektor električnog polja u tački A. (15 p.)
- Ako bi se u tačku A postavilo tačkasto naelektrisanje  $Q_A=-Q$ , odrediti i nacrtati vektor sile koja bi delovala na to naelektrisanje. (5 p.)




Slika 1

2. U kolu na Slici 2, odrediti snagu generatora  $E_1$ . Poznato je  $E_1=14V$ ,  $E_2=10V$ ,  $R_1=15\Omega$ ,  $R_2=10\Omega$ ,  $R_3=10\Omega$ ,  $R_4=15\Omega$ . (20 poena)

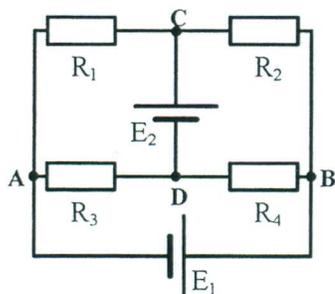

Slika 2

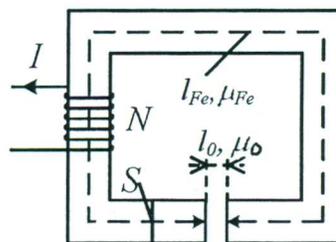


Slika 3

3. Na jezgro magnetne permeabilnosti  $\mu_{Fe} = \pi \cdot 10^{-4} \text{ H/m}$ , dužine srednje linije  $l_{Fe} = 50 \text{ cm}$ , debljine vazdušnog procepa  $l_0 = 5 \text{ mm}$  i površine poprečnog preseka  $S = 1 \text{ cm}^2$ , namotan je provodnik sa  $N = 100$  navojaka, kao što je prikazano na Slici 3.


- Odrediti induktivnost namotaja. (10 poena)
- Ako kroz namotaj protiče struja intenziteta  $I = 0.1 \text{ A}$ , odrediti intezitet vektora jačine magnetnog polja u vazdušnom procepu. (10 poena)

4. U kolu na Slici 4, poznate su vrednosti elemenata:  $E_1 = 20V$ ,  $E_2 = 10V$ ,  $R = 10\Omega$  i  $C = 2\mu F$ . Preklopnik  $\Pi$  je u položaju 1 i u kolu je uspostavljeno stacionarno stanje. U trenutku  $t = 0$ , preklopnik se prebacuje u položaj 2.

- Odrediti izraze za napon i struju kondenzatora nakon prebacivanja preklopnika u položaj 2 i nacrtati odgovarajuće vremenske dijagrame. (15 poena)
- Odrediti trenutak,  $t_1$ , u kome će vrednost napona kondenzatora biti jednaka 15V. (5 poena)

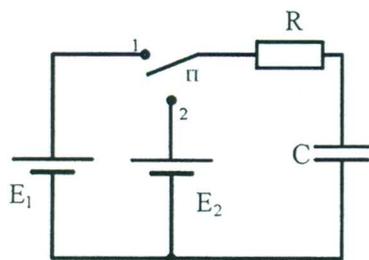

Slika 4

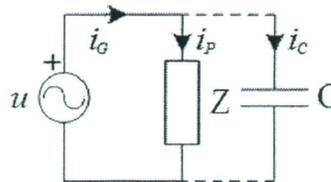

Slika 5

5. U kolu naizmenične struje sa Slike 5, potrošač kompleksne impedanse  $\bar{Z} = (10 + j10)\Omega$  priključen je na naponski izvor  $u(t)$ , pri čemu je poznata struja potrošača  $i_p(t) = 5\sqrt{2} \cdot \sin(2000 \cdot t) \text{ A}$ .

- Odrediti kompleksne predstavnike napona i struje potrošača  $\bar{Z}$ , nacrtati njihov fazorski dijagram i odrediti vremenski oblik napona  $u(t)$ . (7 poena)
- Odrediti aktivnu, reaktivnu i prividnu snagu potrošača  $\bar{Z}$ . (3 poena)
- Odrediti kapacitivnost kondenzatora  $C$  koji je potrebno priključiti paralelno potrošaču  $\bar{Z}$  (kao na Slici 5) da bi faktor snage ekvivalentnog potrošača iznosio  $\cos \varphi = 1$ . (10 poena)

1

a)  $\vec{k}_{A1} = \frac{Q_1}{4\pi\epsilon_0\epsilon_r(2d)^2} \vec{l} = \frac{Q}{4\pi\epsilon_0\epsilon_r 4d^2} \vec{l}$

$$\vec{k}_{A1} = \frac{Q}{16\pi\epsilon_0\epsilon_r d^2} \vec{l}$$


$$\vec{k}_{A2} = \frac{Q_2}{4\pi\epsilon_0\epsilon_r d^2} \vec{l} = \left[ \frac{-2Q}{4\pi\epsilon_0\epsilon_r d^2} \vec{l} = \vec{k}_{Ac} \right]$$

$$\vec{k}_{A3} = \frac{Q_3}{4\pi\epsilon_0\epsilon_r d^2} (-\vec{l}) = \frac{-3Q}{4\pi\epsilon_0\epsilon_r d^2} (-\vec{l}) = \left[ \frac{3Q}{4\pi\epsilon_0\epsilon_r d^2} \vec{l} = \vec{k}_{A3} \right]$$

$$\vec{k}_A = \vec{k}_{A1} + \vec{k}_{A2} + \vec{k}_{A3} = \frac{Q}{4\pi\epsilon_0\epsilon_r d^2} \vec{l} \left( \frac{1}{4} - 2 + 3 \right)$$


$$\vec{k}_A = \frac{5Q}{16\pi\epsilon_0\epsilon_r d^2} \vec{l}$$

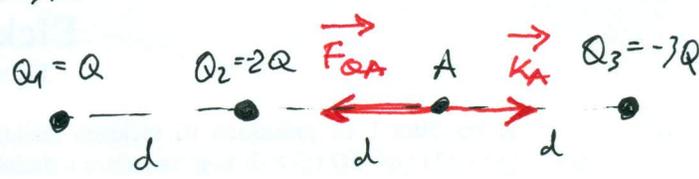b)  $\vec{F}_{QA} = Q_A \cdot \vec{k}_A = -\frac{5Q^2}{16\pi\epsilon_0\epsilon_r d^2} \vec{l}$



2

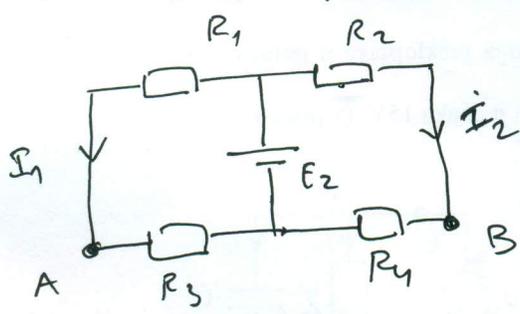Zadatak se može raditi na više načina. U nastavku je dato rešenje na bazi Theveninove teorije.




$$I_1 = \frac{E_2}{R_1 + R_3} = \frac{10}{15 + 10} = \frac{10}{25} = 0,4A$$

$$I_2 = \frac{E_2}{R_2 + R_4} = \frac{10}{10 + 15} = 0,4A$$


$$E_T = U_{AB}^{ov} = R_3 I_1 - R_4 I_2$$
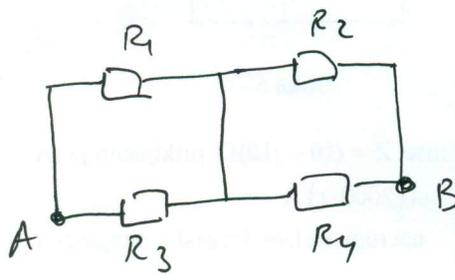
$$E_T = 10 \cdot 0,4 - 15 \cdot 0,4 = -2V$$



$$R_T = R_{AB}^{ov} = R_1 \parallel R_3 + R_2 \parallel R_4 = 2 \cdot \frac{10 \cdot 15}{10 + 15}$$

$$R_T = 12 \Omega$$

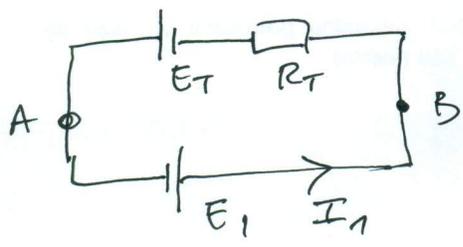

$$I_1 = \frac{E_1 + E_T}{R_T} = \frac{14 - 2}{12} = 1A = I_1$$

$$P_{E1} = E_1 I_1 = 14W$$

3


a)

$$L = \frac{N^2}{R_{m0} + R_{lFe}} = \frac{N^2}{\frac{l_0}{\mu_0 S} + \frac{l_{Fe}}{\mu_{Fe} S}} = \frac{10^4}{\frac{5 \cdot 10^{-3}}{4\bar{u} \cdot 10^{-7} \cdot 10^{-4}} + \frac{50 \cdot 10^{-2} \cdot 10^{-4}}{\bar{u} \cdot 10^{-4} \cdot 10^{-4} \cdot 10^{-3}}}$$

$$L = \frac{10^4}{\frac{5}{4\bar{u} \cdot 10^{-8}} + \frac{5}{\bar{u} \cdot 10^{-7}}} = \frac{10^4}{\frac{5 \cdot 10^7}{\bar{u}} \left( \frac{10}{4} + 1 \right)} = \frac{\bar{u}}{17,5} \cdot 10^{-3} \text{ H}$$

$$L = \frac{\bar{u}}{17,5} \text{ mH} = \frac{4\bar{u}}{70} \text{ mH}$$

b)

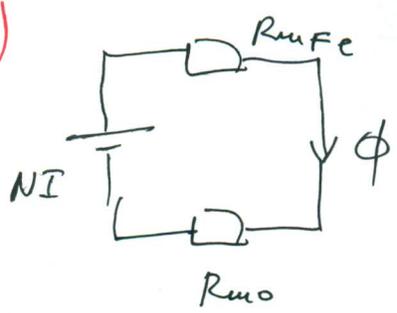

$$\phi = \frac{NI}{R_{lFe} + R_{m0}} \quad / \quad \phi = BS \Rightarrow B = \frac{\phi}{S}$$

$$B = \frac{NI}{S(R_{lFe} + R_{m0})} \quad / \quad B = \mu H$$

$$H_0 = \frac{B}{\mu_0} = \frac{NI}{\mu_0 S (R_{lFe} + R_{m0})}$$


$$H_0 = \frac{NI}{\frac{\mu_0 l_{Fe}}{\mu_{Fe}} + l_0}$$

$$H_0 = \frac{100 \cdot 0,1}{\frac{4\bar{u} \cdot 10^{-7} \cdot 50 \cdot 10^{-2}}{\bar{u} \cdot 10^{-4}} + 5 \cdot 10^{-3}} = \frac{10}{2 \cdot 10^{-3} + 5 \cdot 10^{-3}} = \frac{10000}{7} \frac{\text{H}}{\text{m}}$$

4

$u_c(0^+) = u_c(0^-) = U_{c0} = E_1 = 20\text{V}$  ← ПОЧЕТНИ УСЛОВ

a)

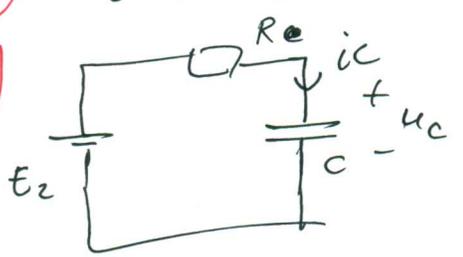

$$-E_2 + R_c i_c + u_c = 0$$

$$RC \frac{du_c}{dt} + u_c = E_2$$

$$\frac{du_c}{dt} + \frac{u_c}{RC} = \frac{E_2}{RC} = K \quad / \quad \tau = RC = 20\text{ms}$$

$$u_c(t) = A e^{-t/\tau} + B$$

$$B = K\tau = \frac{E_2 RC}{RC} = E_2 = 10\text{V}$$

$$u_c(0) = A + B \Rightarrow A = -B + u_c(0)$$

$$A = -E_2 + E_1 = -20 + 10 = -10\text{V}$$

$$u_c(t) = (E_1 - E_2) e^{-t/\tau} + E_2$$

$$u_c(t) = (10 e^{-\frac{t}{20\text{ms}}} + 10) \text{ V}$$

$$i_c(t) = C \frac{d u_c}{dt} = C \cdot \frac{E_1 - E_2}{-\tau} e^{-t/\tau} = \frac{E_2 - E_1}{R} e^{-t/\tau}$$

$$i_c(t) = (- e^{-\frac{t}{20\mu s}}) A$$

b)

$$u_c(t_1) = 15 V$$


$$10 e^{-\frac{t_1}{\tau}} + 10 = 15$$

$$10 e^{-t_1/\tau} = 5$$

$$e^{-t_1/\tau} = \frac{1}{2} \quad | \ln(\cdot)$$

$$-t_1/\tau = \ln\left(\frac{1}{2}\right) = -\ln(2)$$

$$t_1 = \tau \ln(2) = 20 \ln(2) \mu s$$

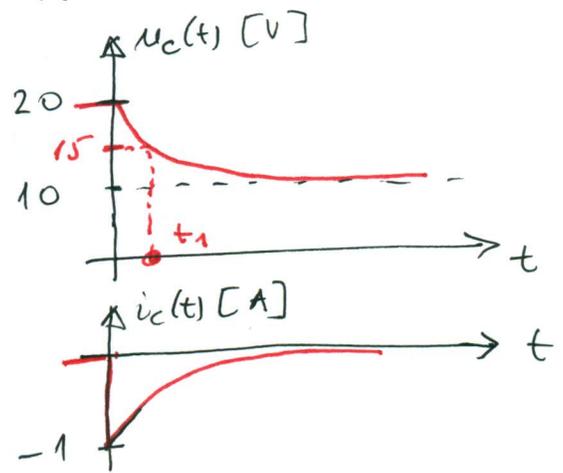


5

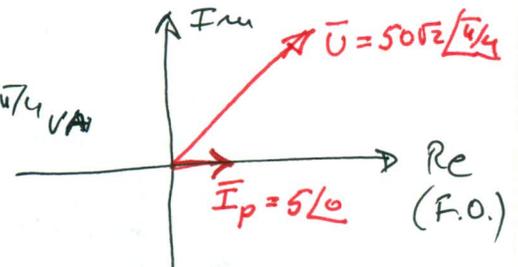a)  $\bar{I}_p = 5 e^{j0} = 5 A$

$$\bar{U} = \bar{Z} \bar{I}_p = (10 + j10) \cdot 5 = (50 + j50) V = (50\sqrt{2} e^{j\pi/4}) V = \bar{U}$$

$$u(t) = 50\sqrt{2} \cdot \sqrt{2} \sin(2000t + \pi/4) V = 100 \sin(2000t + \pi/4) V$$



b)  $\bar{S}_p = \bar{Z} \bar{I}_p^2 = \bar{U} \bar{I}_p^* = 250 + j250 = 250\sqrt{2} e^{j\pi/4} VA$

$$P_p = 250 W$$

$$Q_p = 250 VAR$$

$$S_p = 250\sqrt{2} VA$$

c)  $\cos \varphi = 1 \Rightarrow S = P \Rightarrow Q = 0$   $\left. \begin{array}{l} \\ \\ \end{array} \right\} Q_c = -Q_p = -250 VAR \quad (1)$   
 $Q = Q_p + Q_c$

$$Q_c = -\omega C \cdot U^2 \quad (2)$$

$$(1), (2) \Rightarrow -Q_p = -\omega C U^2 \Rightarrow C = \frac{Q_p}{\omega U^2} = \frac{250}{2000 \cdot (50\sqrt{2})^2}$$

$$C = \frac{250}{2000 \cdot \frac{2500 \cdot 2}{10}} = \frac{1}{40 \cdot 10^3}$$

$$C = 25 \mu F$$