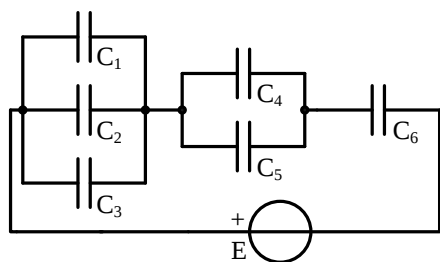



Elektrotehnika - pismeni ispit

13. mart 2026.

1. U kolu na Slici 1 poznate su kapacitivnosti $C_1 = C = 20 \mu\text{F}$, $C_2 = 2C$, $C_3 = C_4 = C_5 = C_6 = 3C$, i elektromotorna sila idealnog naponskog generatora $E = 2 \text{ V}$. Pre povezivanja, svi kondenzatori su bili neopterećeni. Odrediti naelektrisanje na C_3 , napon na C_5 i ukupnu energiju svih kondenzatora. (8 poena)



Slika 1

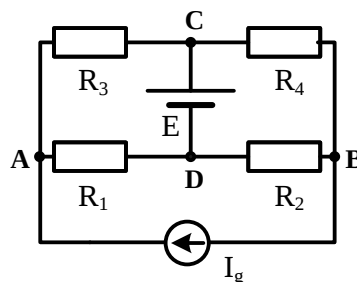


Slika 2


2. U kolu na Slici 2 poznati su parametri: $R_1 = R_3 = 2 \Omega$, $R_2 = R_4 = 4 \Omega$, $E = 40 \text{ V}$, $I_g = 10 \text{ A}$. Primenom metode potencijala čvorova ili metode konturnih struja odrediti intenzitete struja kroz generator E i otpornik R_2 (samostalno zadati referentni smer), a zatim odrediti snagu ovih elemenata. (12 poena)

3. U kolu na Slici 3 prikazano je magnetno kolo sa dva namotaja. Kroz namotaj sa $N_1 = 25$ navojaka protiče konstantna struja $I_1 = 12 \text{ A}$, a krajevi namotaja sa $N_2 = 50$ navojaka su otvoreni. Jezgro je površine poprečnog preseka $S = 5 \text{ cm}^2$, dužine srednje linije $l = 20 \text{ cm}$ i magnetne permeabilnosti $\mu = 2 \cdot 10^{-4} \text{ H/m}$.


- Odrediti fluks vektora magnetne indukcije i jačinu magnetnog polja u jezgru. (3 poena)
- Odrediti energiju magnetnog polja u jezgru. (3 poena)
- Odrediti međusobnu induktivnost namotaja. (2 poena)
- Odrediti indukovanu elektromotornu silu na krajevima otvorenog namotaja. (2 poena)

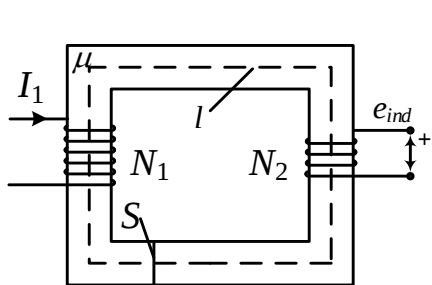

Slika 3

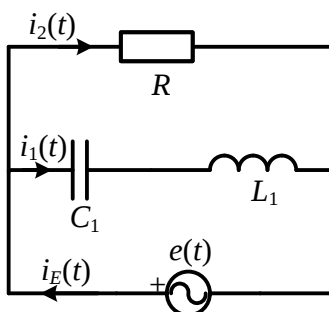

Slika 4

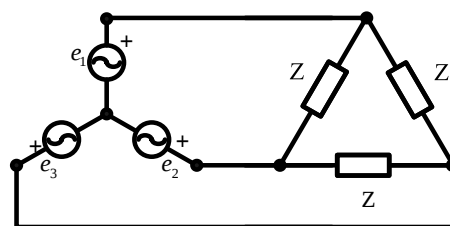



Slika 5

4. U kolu na Slici 4 poznato je: $e(t) = 200\sqrt{2} \cos(500t - \pi) \text{ V}$, $C_1 = 80 \mu\text{F}$, $L_1 = 40 \text{ mH}$, $R = 5 \Omega$. Odrediti:

- kompleksne struje u granama i nacrtati fazorski dijagram svih struja, (5 poena)
- vremenski oblik napona na induktivnom kalem, (2 poena)
- aktivnu, reaktivnu i prividnu snagu i faktor snage celokupnog potrošača, (4 poena)
- kompleksnu admitansu potrošača. (1 poen)


5. Na Slici 5 prikazan je trofazni sistem generator-potrošač. Efektivna vrednost elektromotornih sila generatora iznosi $E = 150 \text{ V}$, aktivna snaga potrošača $P = 2.7 \text{ kW}$, a reaktivna snaga $Q = -3.6 \text{ kVar}$. Odrediti: efektivnu vrednost linijske struje i kompleksnu impedansu potrošača. (8 poena)

①

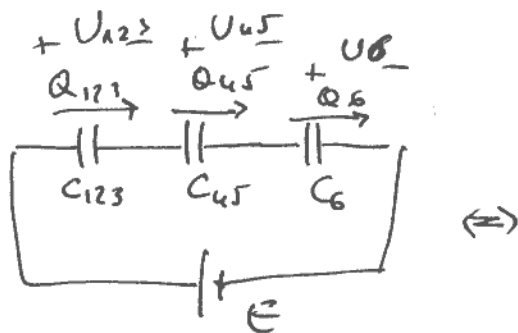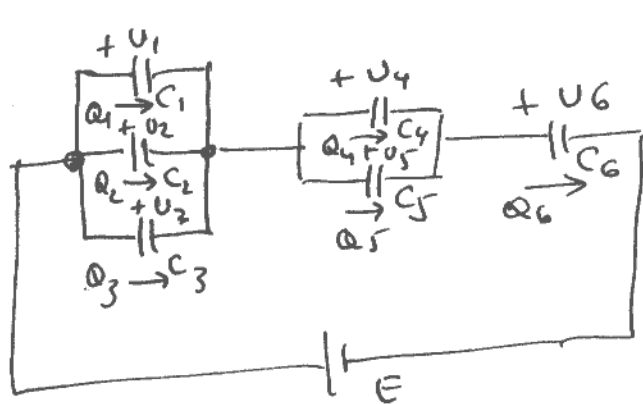

$$C_{123} = C_1 + C_2 + C_3 = 6C = 120\mu C$$

$$C_{45} = C_4 + C_5 = 6C = 120\mu C$$

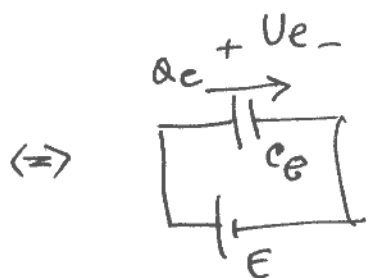

$$C_e = \frac{1}{\frac{1}{C_{123}} + \frac{1}{C_{45}} + \frac{1}{C_6}} = \frac{1}{\frac{1}{6C} + \frac{1}{6C} + \frac{1}{3C}} = \frac{1}{\frac{4}{6C}} = \frac{3}{2}C$$

$$C_e = 30\mu C$$

$$U_e = E = 2V$$

$$Q_e = C_e \cdot U_e = \frac{3}{2}CE = \frac{3}{2} \cdot 20\mu \cdot 2 = 60\mu C = Q_{123} = Q_{45} = Q_6$$

$$U_{45} = \frac{Q_{45}}{C_{45}} = \frac{\frac{3}{2}CE}{6C} = \frac{1}{4}E = 0.5V = U_4 = U_5$$


$$Q_4 = C_4 U_{45} = 3C \cdot \frac{E}{4} = \frac{3}{4}CE = 30\mu C$$

$$U_{123} = \frac{Q_{123}}{C_{123}} = \frac{\frac{3}{2}CE}{6C} = \frac{1}{4}E = 0.5V = U_1 = U_2 = U_3$$

$$Q_3 = C_3 U_3 = 3C \cdot \frac{1}{4}E = \frac{3}{4}CE = 30\mu C$$

$$W_{ce} = \frac{1}{2} C_e U_e^2 = \frac{1}{2} \cdot \frac{3}{2}C \cdot E^2 = \frac{3}{4}CE^2 = 60\mu J$$

②

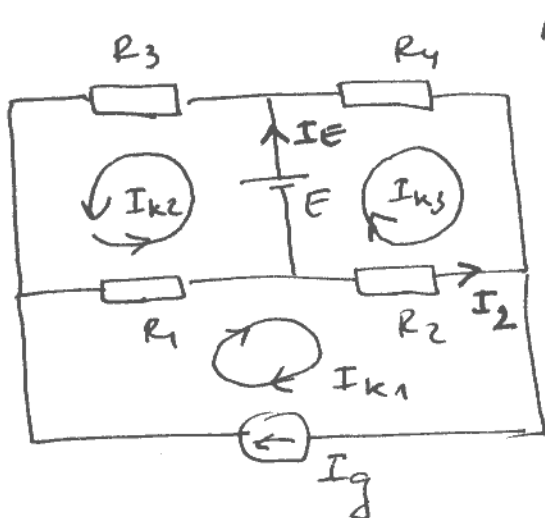

MKS

$$(1) I_{K1} = I_g = 10A$$

$$(2) R_{21} I_{K1} + R_{22} I_{K2} + R_{23} I_{K3} = \sum_{K_L} E_i$$

$$(3) R_{31} I_{K1} + R_{32} I_{K2} + R_{33} I_{K3} = \sum_{K_S} E_i$$

$$(2) R_1 I_{K1} + (R_1 + R_3) I_{K2} + 0 I_{K3} = E$$

$$(3) -R_2 I_{K1} + 0 I_{K2} + (R_2 + R_4) I_{K3} = E$$

$$(2) 2 \cdot 10 + 4 I_{K2} = 40 \Rightarrow I_{K2} = 5A$$


$$(3) -4 \cdot 10 + 8 I_{K3} = 40 \Rightarrow I_{K3} = 10A$$

$$I_E = I_{K2} + I_{K3} = 15A \Rightarrow P_E = E \cdot I_E = 40 \cdot 15 = 600W$$

$$I_2 = I_{K1} - I_{K3} = 0A \Rightarrow P_{R2} = R_2 I_2^2 = 0W$$

3

a)

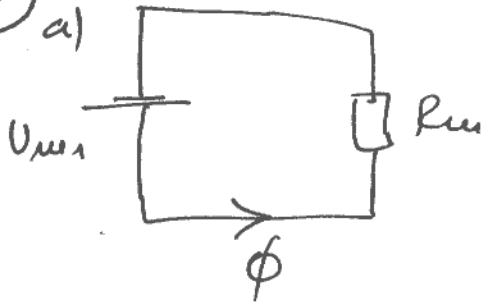

$$U_{M1} = N_1 I_1$$

$$R_{M1} = \frac{l}{\mu S}$$

$$\phi = \frac{U_{M1}}{R_{M1}}$$

$$\phi = \frac{N_1 I_1}{\frac{l}{\mu S}}$$

$$\phi = \frac{\mu S N_1 I_1}{l} = \frac{2 \cdot 10^{-4} \cdot 5 \cdot 10^{-4} \cdot 25 \cdot 12}{20 \cdot 10^{-2}}$$

$$\phi = 150 \cdot 10^{-6} \text{ Wb} = 150 \mu\text{Wb}$$

$$B = \frac{\phi}{S} = \frac{\mu N_1 I_1}{l} = 0,3 \text{ T}$$

$$H = \frac{B}{\mu} = \frac{N_1 I_1}{l} = 1500 \text{ A/m}$$

b) $\omega = \frac{1}{2} \text{ BH}$

$$W = \omega \cdot V = \frac{1}{2} \text{ BH} \cdot l \cdot S = \frac{1}{2} \cdot 0,5 \cdot 1500 \cdot 20 \cdot 10^{-2} \cdot 5 \cdot 10^{-4} = 22,5 \mu\text{J}$$

c)

$$|L_{12}| = |L_{21}| = \frac{\Psi_{12}}{I_1} = \frac{N_2 \phi}{I_1} = \frac{N_1 N_2}{R_{M1}} = 625 \mu\text{H}$$

d)

$$e_{\text{ind}} = - \frac{d\Psi}{dt} = 0 \text{ V, fluxes = const!}$$

4

a)

$$\bar{E} = 200 e^{j\omega t} = -200 \text{ V}$$

$$\bar{Z}_R = R = 5 \Omega$$

$$\bar{Z}_{C1} = -j \frac{1}{\omega C_1} = -j \frac{1}{500 \cdot 80 \cdot 10^{-6}} = -j25 \Omega = 25 e^{-j\pi/2} \Omega$$


$$\bar{Z}_{L1} = j\omega L_1 = j500 \cdot 40 \cdot 10^{-3} = j20 \Omega = 20 e^{j\pi/2} \Omega$$

$$\bar{Z}_1 = \bar{Z}_{L1} + \bar{Z}_{C1} = j20 - j25 = -j5 \Omega = 5 e^{-j\pi/2} \Omega$$

$$\bar{I}_1 = \frac{\bar{E}}{\bar{Z}_1} = \frac{200 e^{j\omega t}}{5 e^{-j\pi/2}} = 40 e^{-j\pi/2} \text{ A} = -j40 \text{ A}$$

$$\bar{I}_2 = \frac{\bar{E}}{\bar{Z}_R} = \frac{-200}{5} = -40 \text{ A} = 40 e^{j\pi} \text{ A}$$
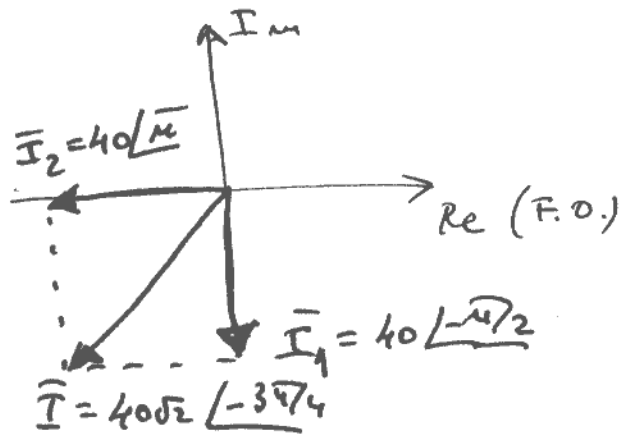
$$\bar{I}_E = \bar{I}_1 + \bar{I}_2 = (-40 - j40) \text{ A} = 40\sqrt{2} e^{-j^{3\pi/4}} \text{ A}$$



$$b) \bar{U}_{L1} = \bar{Z}_{L1} \cdot \bar{I}_1 = 20 e^{j\pi/2} \cdot 40 e^{-j\pi/2} = 800 e^{j0} \text{ V}$$

$$u_{L1}(t) = 800\sqrt{2} \cos(500t) \text{ V}$$

$$c) \bar{S}_{\text{pot}} = \bar{S}_{\text{gen}} = \bar{E} \cdot \bar{I}_E^* = 200 e^{-j\pi} \cdot 40\sqrt{2} e^{j^{3\pi/4}} = 8000\sqrt{2} e^{-j\pi/4} \text{ VA}$$

$$\bar{S}_{\text{pot}} = 8000\sqrt{2} \left(\underbrace{\cos(-\pi/4)}_{\frac{1}{\sqrt{2}}} + j \underbrace{\sin(-\pi/4)}_{-\frac{1}{\sqrt{2}}} \right) = (8000 - j8000) \text{ VA}$$

$$P_{\text{pot}} = 8000 \text{ W}, \quad Q_{\text{pot}} = -8000 \text{ VAR}, \quad S_{\text{pot}} = 8000\sqrt{2} \text{ VA}$$

$$\cos \varphi = 1/\sqrt{2}$$

$$d) \bar{Y} = \frac{\bar{I}_E}{\bar{E}} = \frac{-40 - j40}{-200} = (0,2 + j0,2) \text{ S}$$

$$\left[\bar{Y} = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} = \frac{1}{-j5} + \frac{1}{5} = (0,2 + j0,2) \text{ S} \right]$$

$\textcircled{5} \quad U_L = \sqrt{3} E = 150\sqrt{3} \text{ V} \quad (\text{generator})$ $U_F = U_L = 150\sqrt{3} \text{ V} \quad (\text{potrojac})$ $S = 3 U_F \cdot I_F \Rightarrow I_F = \frac{S}{3 U_F} = \frac{4500}{3 \cdot 150\sqrt{3}} = 10/\sqrt{3} \text{ A}$	$S = \sqrt{P^2 + Q^2}$ $S = \sqrt{2700^2 + 3600^2}$ $S = \sqrt{900^2 \cdot (3^2 + 4^2)}$ $S = 900 \cdot 5 = 4500 \text{ VA}$	
	$(\text{potrojac}) \quad I_L = \sqrt{3} I_F = 10 \text{ A}$	$Z = \frac{U_F}{I_F} = \frac{150\sqrt{3}}{10/\sqrt{3}} = 45 \Omega$
	$\cos \varphi = \frac{P}{S} = 3/5$	$\bar{Z} = Z \cos \varphi + j Z \sin \varphi = (27 - j36) \Omega$
	$\sin \varphi = \frac{Q}{S} = -4/5$	

$$\left\{ \begin{aligned} \bar{S} &= P + jQ = 3 \bar{Z} \cdot I_r^2 \\ \bar{Z} &= \frac{P + jQ}{3 I_r^2} = \frac{2700 - j3600}{3 \cdot \left(\frac{10}{\sqrt{3}}\right)^2} = (27 - j36) \Omega \end{aligned} \right\}$$