


Elektrotehnika - pismeni ispit

27. april 2026.


1. Tri veoma velike ravnomerno naelektrisanе metalne ploče, jednakih površina $S = 100 \text{ m}^2$, nalaze se u sredini čija je dielektrična konstanta $\varepsilon = 2 \cdot 10^{-9} \text{ F/m}$, na međusobnom rastojanju od $d = 2 \text{ cm}$, kao na Slici 1. Ploče su opterećene količinama naelektrisanja: $Q_1 = 2 \text{ } \mu\text{C}$, $Q_2 = 8 \text{ } \mu\text{C}$ i $Q_3 = -4 \text{ } \mu\text{C}$.

a) Usvojiti koordinatni sistem, a zatim odrediti i nacrtati vektor električnog polja u tačkama A i B. (6 p.)


b) Odrediti napon između prve i treće ploče U_{13} . (2 poena)

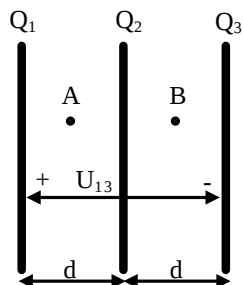

Slika 1

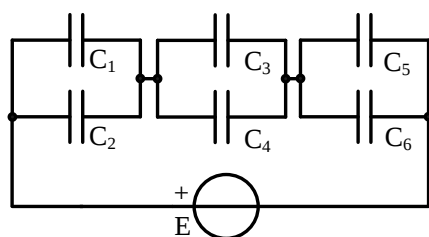

Slika 2

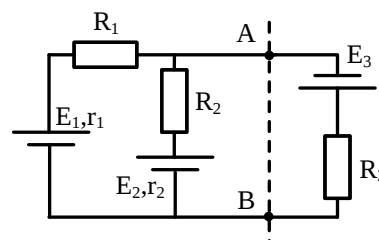

Slika 3

2. U kolu na Slici 2 poznate su kapacitivnosti $C_1 = 10 \text{ } \mu\text{F}$, $C_2 = 20 \text{ } \mu\text{F}$, $C_3 = C_4 = 30 \text{ } \mu\text{F}$, $C_5 = 50 \text{ } \mu\text{F}$, $C_6 = 10 \text{ } \mu\text{F}$ i elektromotorna sila naponskog generatora $E = 40 \text{ V}$. Pre povezivanja, svi kondenzatori su bili neopterećeni. Odrediti naelektrisanje na C_1 , napon na C_3 i energiju kondenzatora C_5 . (8 poena)

3. U kolu na Slici 3 poznati su parametri: $R_1 = 30 \text{ } \Omega$, $R_2 = 50 \text{ } \Omega$, $R_3 = 20 \text{ } \Omega$, $E_1 = 50 \text{ V}$, $r_1 = 10 \text{ } \Omega$, $E_2 = 10 \text{ V}$, $r_2 = 10 \text{ } \Omega$ i $E_3 = 10 \text{ V}$.

a) Nacrtati Tevenenov generator za deo kola levo od tačaka A i B i odrediti njegove parametre. (8 poena)

b) Primenom Tevenenove teoreme odrediti intenzitet struje kroz otpornik R_3 i napon U_{AB} . (2 poena)


4. Na Slici 4 prikazano je magnetno kolo sa dva namotaja. Kroz namotaj sa N_1 navojaka protiče struja I_1 , a kroz namotaj sa N_2 navojaka struja I_2 . Jezgro se sastoji od feromagnetnog materijala površine poprečnog preseka A , dužine srednje linije l i relativne magnetne permeabilnosti μ_r , i vazdušnog procepa debljine l_0 , kao što je ilustrovano na Slici 4. Odrediti:

a) intenzitet vektora magnetne indukcije i jačine magnetnog polja u vazdušnom procepu, (4 poena)


b) fluks vektora magnetne indukcije u feromagnetnom materijalu jezgra, (2 poena)

c) energiju magnetnog polja u feromagnetnom materijalu jezgra, (2 poena)

d) sopstvene induktivnosti i međusobnu induktivnost namotaja. (4 poena)

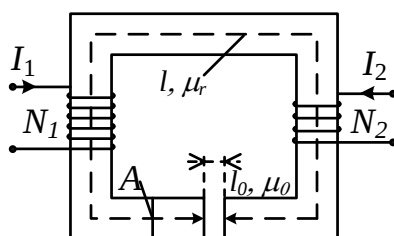

Slika 4

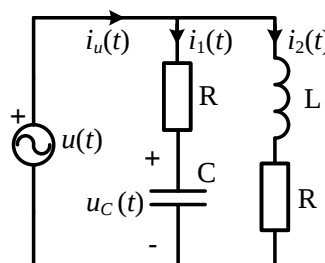

Slika 5


5. Na Slici 5 je prikazano kolo naizmenične struje poznatih parametara: $R = 25 \text{ } \Omega$, $L = 25 \text{ mH}$, $C = 40 \text{ } \mu\text{F}$ i $u(t) = 100\sqrt{2} \cos(1000t + \pi/2) \text{ V}$. Odrediti:

a) kompleksne izraze za sve označene struje u kolu i skicirati njihov fazorski dijagram, (6 poena)

b) vremenski oblik napona na kondenzatoru, (2 poena)

c) kompleksnu impedansu celokupnog potrošača, (1 poen)

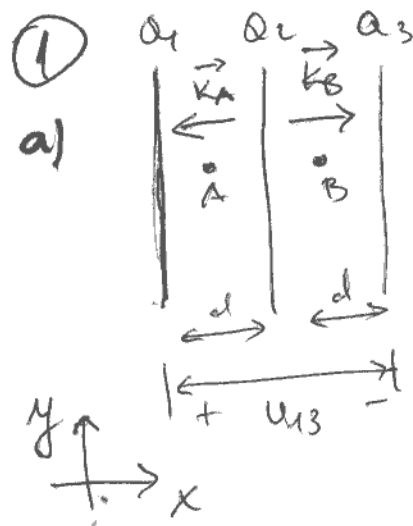d) aktivnu, reaktivnu i prividnu snagu celokupnog potrošača. (3 poena)



$$\vec{K}_A = \vec{K}_{A1} + \vec{K}_{A2} + \vec{K}_{A3} = \frac{\sigma_1}{2\epsilon} \vec{i} + \frac{\sigma_2}{2\epsilon} (-\vec{i}) + \frac{\sigma_3}{2\epsilon} (-\vec{i})$$

$$\vec{K}_A = \frac{Q_1 - Q_2 - Q_3}{2\epsilon S} \vec{i} = \frac{(2 - 8 + 4) \cdot 10^{-6}}{2 \cdot 2 \cdot 10^{-9} \cdot 100} \vec{i}$$


$$\vec{K}_A = -\frac{1}{2} \cdot 10^4 \vec{i} = -5 \vec{i} \text{ V/m}$$

$$\vec{K}_B = \vec{K}_{B1} + \vec{K}_{B2} + \vec{K}_{B3} = \frac{\sigma_1}{2\epsilon} \vec{i} + \frac{\sigma_2}{2\epsilon} \vec{i} + \frac{\sigma_3}{2\epsilon} (-\vec{i})$$

$$\vec{K}_B = \frac{Q_1 + Q_2 - Q_3}{2\epsilon S} \vec{i} = \frac{(2 + 8 + 4) \cdot 10^{-6}}{2 \cdot 2 \cdot 10^{-9} \cdot 100} \vec{i}$$

$$\vec{K}_B = 35 \vec{i} \text{ V/m}$$

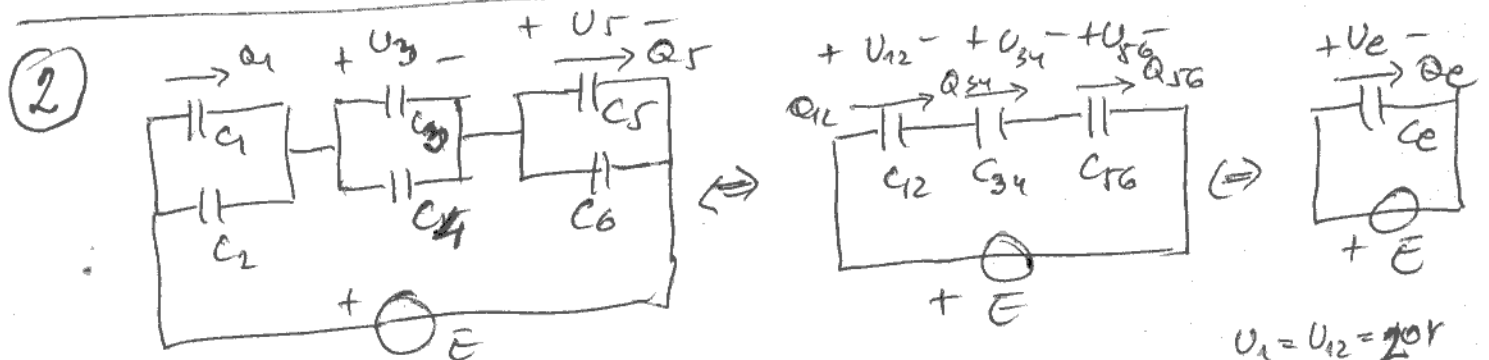b) $U_{13} = U_{12} + U_{23} = \vec{K}_A \cdot (d \cdot \vec{i}) + \vec{K}_B \cdot (d \cdot \vec{i}) = -5 \cdot 0,02 + 35 \cdot 0,02 = 0,6 \text{ V}$



$$C_{12} = C_1 + C_2 = 30 \mu\text{F}$$

$$C_{34} = C_3 + C_4 = 60 \mu\text{F}$$

$$C_{56} = C_5 + C_6 = 60 \mu\text{F}$$

$$C_e = \frac{1}{\frac{1}{C_{12}} + \frac{1}{C_{34}} + \frac{1}{C_{56}}}$$

$$C_e = \frac{1}{\frac{1}{30} + \frac{1}{60} + \frac{1}{60}} = 15 \mu\text{F}$$

$$Q_e = E = 40 \text{ V}$$

$$Q_e = C_e U_e = 600 \mu\text{C}$$

$$Q_{12} = Q_{34} = Q_{56} = Q_e = 600 \mu\text{C}$$

$$U_{12} = \frac{Q_{12}}{C_{12}} = \frac{600 \mu\text{C}}{30 \mu\text{F}} = 20 \text{ V}$$

$$U_{34} = \frac{Q_{34}}{C_{34}} = 10 \text{ V}$$

$$U_{56} = \frac{Q_{56}}{C_{56}} = 10 \text{ V}$$

$$U_1 = U_{12} = 20 \text{ V}$$

$$Q_1 = C_1 U_1 = 200 \mu\text{C}$$


$$U_3 = U_{34} = 10 \text{ V}$$

$$U_5 = U_{56} = 10 \text{ V}$$

$$W_5 = \frac{1}{2} C_5 U_5^2$$

$$W_5 = 2500 \mu\text{J}$$

$$W_5 = 2,5 \text{ mJ}$$

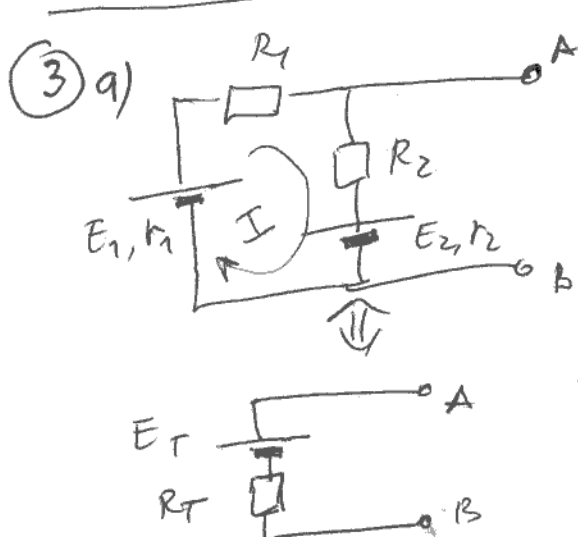

$$E_T = U_{AB} = 0 \text{ V}$$

$$-E_1 + R_1 I + r_1 I + R_2 I + E_2 + r_2 I = 0$$

$$I = \frac{E_1 - E_2}{R_1 + R_2 + r_1 + r_2} = \frac{50 - 10}{30 + 10 + 10 + 10} = 0,4 \text{ A}$$


$$E_T = U_{AB} = R_2 I + r_2 I + E_2 = 34 \text{ V}$$

$$R_T =$$

$$R_T = R_{AB} = \frac{(R_1 + r_1)(R_2 + r_2)}{R_1 + R_2 + r_1 + r_2}$$

$$R_T = \frac{40 \cdot 60}{100} = 24 \Omega$$

b)


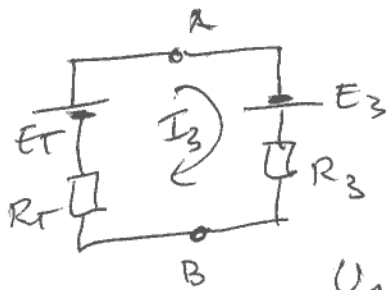


$$-E_1 + R_1 I_3 - E_3 + R_3 I_3 = 0$$

$$I_3 = \frac{E_1 + E_3}{R_1 + R_3} = \frac{34 + 10}{24 + 20} = 1 \text{ A}$$

$$U_{AB} = -E_3 + R_3 I_3 = -10 + 20 \cdot 1 = 10 \text{ V}$$

④

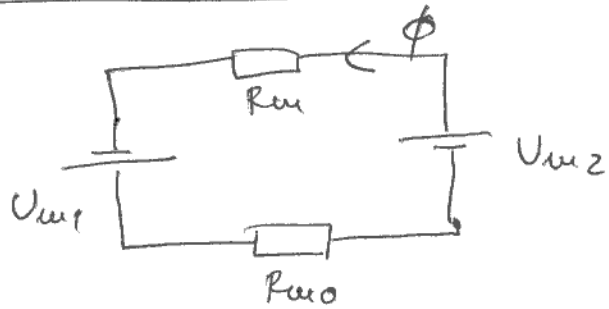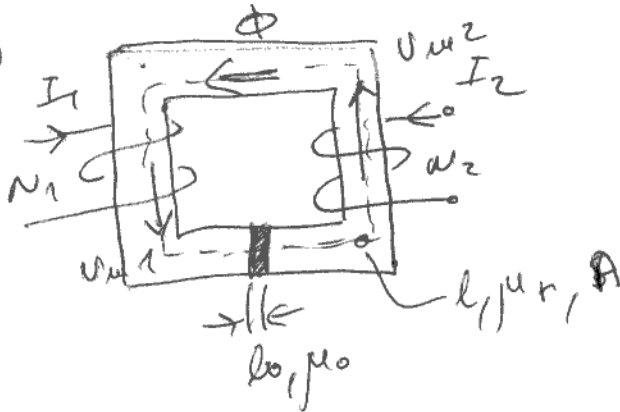

$$U_{m1} = N_1 I_1 \quad R_m = \frac{l}{\mu_0 \mu_r A}$$

$$U_{m2} = N_2 I_2 \quad R_{m0} = \frac{l_0}{\mu_0 A}$$

a, b)

$$\phi = \frac{U_{m1} + U_{m2}}{R_m + R_{m0}}$$

$$\phi = \frac{(N_1 I_1 + N_2 I_2) / \mu_0 A}{(l / \mu_r + l_0)}$$

$$B_0 = B = \frac{\phi}{A} = \frac{\mu_0 (N_1 I_1 + N_2 I_2)}{l_0 + l / \mu_r}$$

$$H_0 = \frac{B_0}{\mu_0} = \frac{N_1 I_1 + N_2 I_2}{l_0 + l / \mu_r}$$

$$c) \quad W = w \cdot V, \quad w = \frac{1}{2} B H, \quad V = l_0 A$$

$$W = \frac{1}{2} \frac{B^2}{\mu_0 \mu_r} l_0 A = \frac{\mu_0^2 (N_1 I_1 + N_2 I_2)^2}{2 \mu_0 \mu_r (l_0 + l / \mu_r)^2} \cdot l_0 A$$

$$W = \frac{\mu_0 l_0 A}{2 \mu_r} \left(\frac{N_1 I_1 + N_2 I_2}{l_0 + l / \mu_r} \right)^2$$


$$d) \quad L_1 = \frac{\psi_1}{I_1} \Big|_{I_2=0} = \frac{N_1 \phi (I_2=0)}{I_1} = \frac{N_1^2}{R_m + R_{m0}} = \frac{\mu_0 A N_1^2}{l_0 + l / \mu_r}$$

$$L_2 = \frac{\psi_2}{I_2} \Big|_{I_1=0} = \frac{N_2 \phi (I_1=0)}{I_2} = \frac{N_2^2}{R_m + R_{m0}} = \frac{\mu_0 A N_2^2}{l_0 + l / \mu_r}$$

$$L_{12} = \frac{\psi_2}{I_1} \Big|_{I_2=0} = \frac{\psi_1}{I_2} \Big|_{I_1=0} = \frac{N_1 N_2}{R_m + R_{m0}} = \frac{\mu_0 A N_1 N_2}{l_0 + l / \mu_r}$$

5

a)

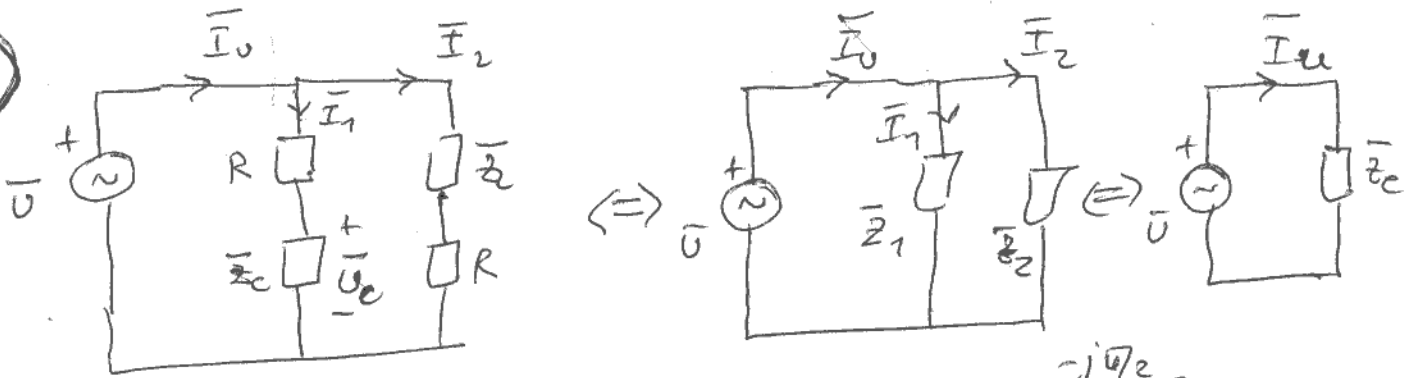

$$\bar{Z}_C = -j \frac{1}{\omega C} = -j \frac{1}{1000 \cdot 40 \cdot 10^{-6}} = -j 25 \Omega = 25 e^{-j\pi/2} \Omega$$

$$\bar{Z}_L = j\omega L = j 1000 \cdot 25 \cdot 10^{-3} = j 25 \Omega = 25 e^{j\pi/2} \Omega$$

$$\bar{Z}_1 = R + \bar{Z}_C = (25 - j 25) \Omega = 25\sqrt{2} e^{-j\pi/4} \Omega$$

$$\bar{Z}_2 = R + \bar{Z}_L = (25 + j 25) \Omega = 25\sqrt{2} e^{j\pi/4} \Omega$$

$$\bar{I}_1 = \frac{\bar{U}}{\bar{Z}_1} = \frac{100 e^{j\pi/2}}{25\sqrt{2} e^{-j\pi/4}} = 2\sqrt{2} e^{j3\pi/4} = 2\sqrt{2} \left(-\frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}}\right) = (-2 + j2) A$$

$$\bar{I}_2 = \frac{\bar{U}}{\bar{Z}_2} = \frac{100 e^{j\pi/2}}{25\sqrt{2} e^{j\pi/4}} = 2\sqrt{2} e^{j\pi/4} = (2 + j2) A$$

$$\bar{I}_0 = \bar{I}_1 + \bar{I}_2 = j4 A = 4 e^{j\pi/2} A$$

b) $\bar{U}_C = \bar{Z}_C \cdot \bar{I}_1 = 25 e^{-j\pi/2} \cdot 2\sqrt{2} e^{j3\pi/4}$

$$\bar{U}_C = 50\sqrt{2} e^{j\pi/4} V$$

$$u_C(t) = 100 \cos(1000t + \pi/4) V$$

c) $\bar{Z}_e = \frac{\bar{Z}_1 \cdot \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} = \frac{(25 - j25)(25 + j25)}{25 - j25 + 25 + j25} = \frac{25^2(1 - j)(1 + j)}{25(1 - j + 1 + j)} = \frac{25(1^2 - j^2)}{2}$

$$\bar{Z}_e = 25 \Omega$$

d) $\bar{S} = \bar{U} \cdot \bar{I}_0^* = \bar{Z}_e \bar{I}_0^2 = \frac{U^2}{\bar{Z}_e^*} = (400 + j0) VA$

$$P = 400 W$$

$$Q = 0 VAR$$

$$S = |\bar{S}| = \sqrt{P^2 + Q^2} = 400 VA$$

