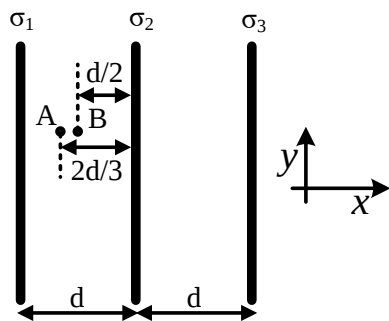



# Elektrotehnika - pismeni ispit

7. jul 2026.

1. Tri veoma tanke i veoma velike ravnomerno naelektrisane metalne ploče nalaze se u sredini čija je dielektrična konstanta  $\varepsilon = 0.5 \cdot 10^{-8} \text{ F/m}$ , na međusobnom rastojanju od  $d = 5 \text{ cm}$  kao što je prikazano na Slici 1. Poznate su površinske gustine naelektrisanja ploča  $\sigma_1 = 80 \text{ nC/m}^2$ ,  $\sigma_2 = -60 \text{ nC/m}^2$  i  $\sigma_3 = 20 \text{ nC/m}^2$ . Odrediti vektore električnog polja u tačkama A i B, a zatim odrediti napon  $U_{AB}$ . (10 poena)



Slika 1

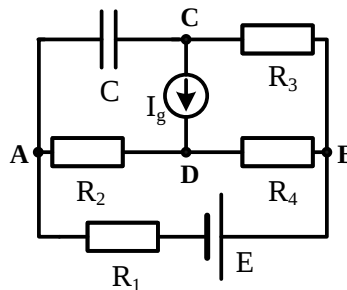

Slika 2


2. U kolu sa Slike 2 potrebno je odrediti energiju kondenzatora  $C$ , snagu strujnog generatora  $I_g$  i snagu idealnog naponskog generatora  $E$ .

Poznato je:  $E = 40 \text{ V}$ ,  $I_g = 4 \text{ A}$ ,  $R_1 = R_2 = R = 10 \Omega$ ,  $R_3 = R_4 = 2R = 20 \Omega$ ,  $C = 2 \text{ nF}$ . (12 poena)


3. U kolu na Slici 3 prikazano je magnetno kolo sa dva namotaja. Kroz namotaj sa  $N_1 = 100$  navojaka protiče struja  $I_1 = 3 \text{ A}$ , a kroz namotaj sa  $N_2 = 500$  navojaka protiče struja  $I_2 = 1 \text{ A}$ . Jezgro je površine poprečnog preseka  $S = 10 \text{ cm}^2$ , dužine srednje linije  $l = 40 \text{ cm}$  i magnetne permeabilnosti  $\mu = 2 \cdot 10^{-5} \text{ H/m}$ .

a) Odrediti fluks vektora magnetne indukcije i jačinu magnetnog polja u jezgru. (6 poena)


b) Odrediti koju vrednost bi trebalo da ima struja u drugom namotaju,  $I'_2 = ?$ , tako da energija magnetnog polja u jezgru bude jednaka nuli. (2 poena)

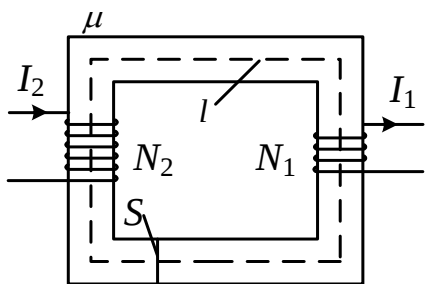

Slika 3

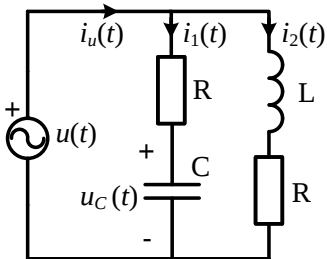

Slika 4

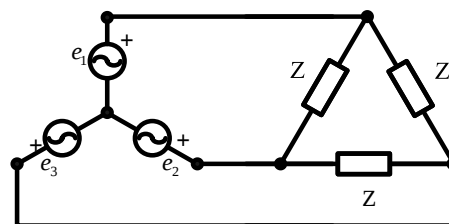

Slika 5

4. Na Slici 4 je prikazano kolo naizmenične struje poznatih parametara:  $R = 50 \Omega$ ,  $L = 100 \text{ mH}$ ,  $C = 40 \mu\text{F}$  i  $u(t) = 200\sqrt{2} \cos(500t) \text{ V}$ . Odrediti:

a) kompleksne izraze za sve označene struje u kolu i skicirati njihov fazorski dijagram, (6 poena)

b) vremenski oblik napona na kondenzatoru, (2 poena)

c) kompleksnu impedansu celokupnog potrošača, (1 poen)

d) aktivnu, reaktivnu i prividnu snagu celokupnog potrošača. (3 poena)

5. Na Slici 5 prikazan je trofazni sistem generator-potrošač. Efektivna vrednost elektromotornih sila generatora iznosi  $E = 400 \text{ V}$ , reaktivna snaga trofaznog potrošača  $Q = -12 \text{ kVar}$ , a faktor snage je  $\sqrt{3}/2$ . Odrediti linijsku struju i kompleksnu impedansu potrošača. (8 poena)

①  $\vec{K} = \vec{K}_A = \vec{K}_B$


$$\vec{K} = \frac{\sigma_1}{2\epsilon} \vec{i} + \frac{\sigma_2}{2\epsilon} (-\vec{i}) + \frac{\sigma_3}{2\epsilon} (-\vec{i}) = \frac{\sigma_1 - \sigma_2 - \sigma_3}{2\epsilon} \vec{i}$$

$$\vec{K} = \frac{80 \mu - (-60 \mu) - 20 \mu}{2 \cdot 0,5 \cdot 10^{-8}} \vec{i} = \frac{120 \cdot 10^{-9}}{10^{-8}} \vec{i} = 12 \vec{i} \frac{V}{m}$$

$$U_{AB} = \int_A^B \vec{K} \cdot d\vec{l} = \vec{K} \cdot \Delta \vec{l} = \vec{K} \cdot \left( \frac{d}{6} \vec{i} \right) = 12 \vec{i} \cdot \frac{5 \cdot 10^{-2}}{6} \vec{i} = 0,1 V$$

$$\Delta l = \frac{2d}{3} - \frac{d}{2} = \frac{4d - 3d}{6} = \frac{d}{6}$$

②

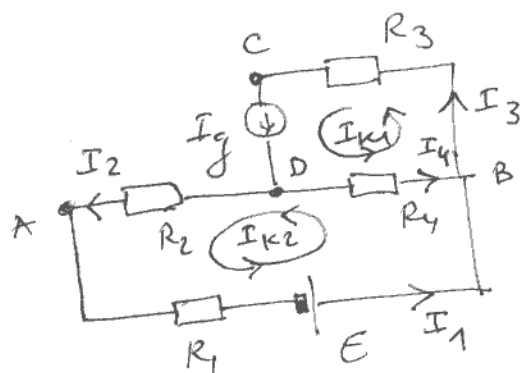

MKS:  $I_{K1} = I_g = 4 A$

$$R_{21} I_{K1} + R_{22} I_{K2} = \sum_{K2} \epsilon$$

$$-R_4 I_g + (R_1 + R_2 + R_4) I_{K2} = E$$

$$I_{K2} = \frac{E + R_4 I_g}{R_1 + R_2 + R_4} = \frac{E + 2R I_g}{4R}$$

$$I_{K2} = \frac{E}{4R} + \frac{I_g}{2} = \frac{40}{40} + \frac{4}{2} = 3 A$$

$$I_1 = I_{K2} = 3 A$$

$$I_2 = I_1 = I_{K2} = 3 A$$

$$I_3 = I_g = 4 A$$

$$I_4 = I_{K1} - I_{K2} = 1 A$$

$$U_{oc} = R_4 I_4 + R_3 I_3 = 100 V$$

$$P_{I_g} = U_{oc} \cdot I_g = 400 W$$


$$U_{AC} = -R_2 I_2 + R_3 I_3 + R_4 I_4 = -10 \cdot 3 + 20 \cdot 4 + 20 \cdot 1$$

$$U_{AC} = 70 V \Rightarrow W_c = \frac{1}{2} C U_{AC}^2 = \frac{1}{2} \cdot 2 \cdot 10^{-9} \cdot 70^2$$

$$W_c = 4,9 \mu J$$

$$P_E = E \cdot I_1 = 120 W$$

③ a)

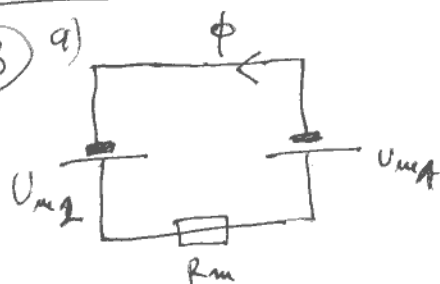

$$R_m = \frac{l}{\mu S}, U_{m1} = N_1 I_1, U_{m2} = N_2 I_2$$

$$\phi = \frac{U_{m2} - U_{m1}}{R_m} = \frac{N_2 I_2 - N_1 I_1}{\frac{l}{\mu S}} = \frac{500 \cdot 1 - 100 \cdot 3}{\frac{40 \cdot 10^{-2}}{2 \cdot 10^{-5} \cdot 10 \cdot 10^{-4}}}$$


$$\phi = 10^{-5} Wb = 10 \mu Wb$$

$$B = \frac{\phi}{S} = \frac{10 \cdot 10^{-6}}{10 \cdot 10^{-4}} = 10^{-2} T = 0,01 T$$

$$H = \frac{B}{\mu} = \frac{10^{-2}}{2 \cdot 10^{-5}} = 500 A/m$$

b)  $W_m = 0 \Rightarrow B, H = 0 \Rightarrow \phi = 0 \Rightarrow N_2 I_2' - N_1 I_1 = 0 \Rightarrow I_2' = \frac{N_1 I_1}{N_2} = \frac{3}{5} = 0,6 A$

4

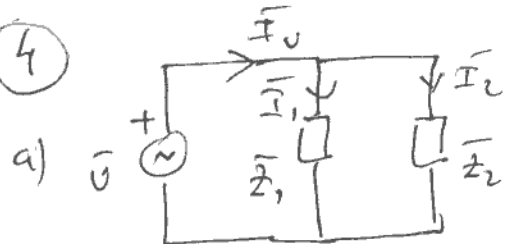

$$\bar{U} = 200 e^{j0} = 200 \text{ V}$$

$$\bar{Z}_L = j\omega L = j500 \cdot 100 \cdot 10^{-3} = j50 \Omega$$

$$\bar{Z}_2 = R + \bar{Z}_L = (50 + j50) \Omega = 50\sqrt{2} e^{j\pi/4} \Omega$$


$$\bar{Z}_C = -j \frac{1}{\omega C} = -j \frac{1}{500 \cdot 40 \cdot 10^{-6}} = -j50 \Omega$$

$$\bar{Z}_1 = R + \bar{Z}_C = (50 - j50) \Omega = 50\sqrt{2} e^{-j\pi/4} \Omega$$

$$\bar{I}_1 = \frac{\bar{U}}{\bar{Z}_1} = \frac{200}{50\sqrt{2} e^{-j\pi/4}} = \frac{4}{\sqrt{2}} e^{j\pi/4} = 2\sqrt{2} e^{j\pi/4} \text{ A} = (2 + j2) \text{ A}$$

$$\bar{I}_2 = \frac{\bar{U}}{\bar{Z}_2} = \frac{200}{50\sqrt{2} e^{j\pi/4}} = 2\sqrt{2} e^{-j\pi/4} \text{ A} = (2 - j2) \text{ A}$$
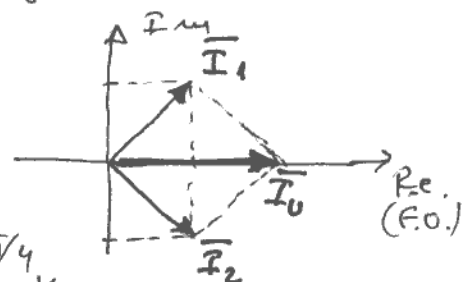
$$\bar{I}_U = \bar{I}_1 + \bar{I}_2 = 4 \text{ A}$$



$$b) \bar{U}_C = \bar{Z}_C \cdot \bar{I}_1 = 50 e^{-j\pi/2} \cdot 2\sqrt{2} e^{j\pi/4} = 100\sqrt{2} e^{-j\pi/4} \text{ V}$$

$$u_C(t) = 200 \cos(500t - \pi/4) \text{ V}$$

$$c) \bar{Z}_e = \frac{\bar{Z}_1 \cdot \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} = \frac{50\sqrt{2} e^{j\pi/4} \cdot 50\sqrt{2} e^{-j\pi/4}}{50 + j50 + 50 - j50} = \frac{2500 \cdot 2}{50 \cdot 2} = 50 \Omega$$

$$(or) \bar{Z}_e = \frac{\bar{U}}{\bar{I}_U} = \frac{200}{4} = 50 \Omega$$

$$d) \bar{S} = \bar{U} \bar{I}_U^* = \bar{Z}_e I_U^2 = 50 \cdot 16 = (800 + j0) \text{ VA}$$

$$P = 800 \text{ W}, Q = 0 \text{ VAR}, S = 800 \text{ VA}$$

5

$$\text{GEN } Y: U_L = E\sqrt{3} = 400\sqrt{3} \text{ V}$$

$$\text{POR } \Delta: U_F = U_L = 400\sqrt{3} \text{ V}$$

$$\cos \varphi = \sqrt{3}/2$$

$$\sin \varphi = -\sqrt{1 - \cos^2 \varphi} = -\sqrt{1 - \frac{3}{4}} = -\frac{1}{2}$$

KAPACITIVNI  
JER JE Q < 0

$$Q = 3U_F I_F \sin \varphi \Rightarrow I_F = \frac{Q}{3U_F \sin \varphi} = \frac{-12000}{3 \cdot 400\sqrt{3} \cdot (-1/2)} = \frac{20}{\sqrt{3}} \text{ A}$$

$$\boxed{I_L = I_F \sqrt{3} = 20 \text{ A}}$$

$$Z = \frac{U_F}{I_F} = \frac{400\sqrt{3}}{\frac{20}{\sqrt{3}}} = 60 \Omega$$

$$\bar{Z} = Z \cos \varphi + j Z \sin \varphi = Z e^{j\varphi}$$

$$\bar{Z} = (30\sqrt{3} - j30) \Omega$$